 


# CMOS Digital Integrated Circuits




## Chapter 13 Chip Input and Output (I/O) Circuits

S.M. Kang, Y. Leblebici, and  
C. Kim

# Introduction


- ◆ Critical factors of reliability, signal integrity, and inter-chip communication speed
  - Clock generation and distribution
    - External clock source -> on-chip internal clock generation
  - ESD protection
    - Protection for internal circuits from external hazards
  - I/O circuits
    - CMOS <-> TTL or ECL
  - On-chip noise prevention
    - From parasitic inductance in bonding wires
  - Latch-up prevention
    - From parasitic bipolar transistors

# ESD Protection

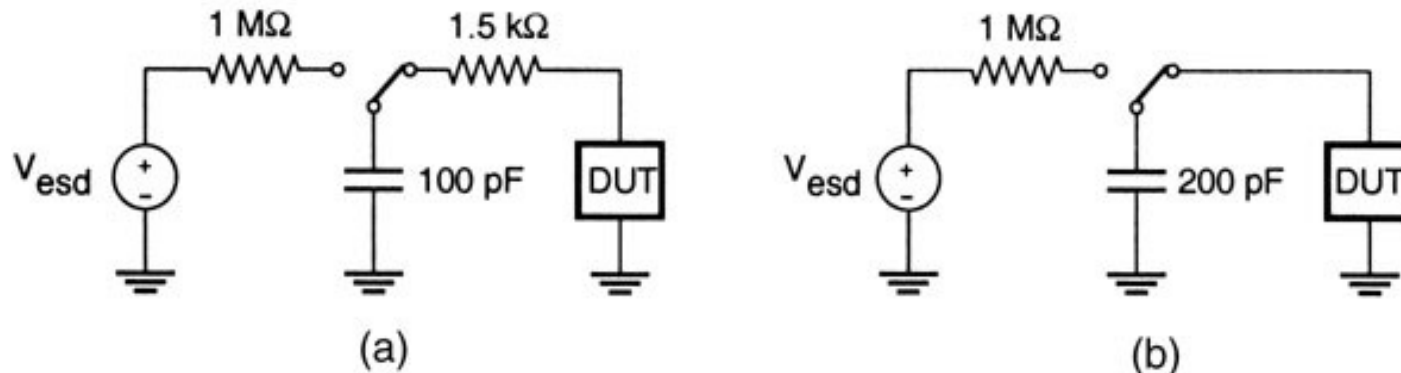


Human body model

Machine model

 

Charged device model, for ESD testing
 
# Simplified Lumped-Element Model of HBM-ESD and MM-ESD Testers



Component	HBM	MM
$C_C$ (pF)	100	200
$R_S$ ( $\Omega$ )	1500	25
$L_S$ ( $\mu$ H)	5	2.5
$C_S$ (pF)	1	0
$C_T$ (pF)	10	10

(b)

# Types of ESDs

## ◆ HBM(Human Body Model)

- Human body can induce 1.5kV
  - Condition
    - 80% relative humidity
    - Walking on synthetic carpet


## ◆ MM(Machine Model)

- Higher current than HBM

## ◆ CDM(Charged Device Model)

- Discharge of the packaged IC
  - Chip assembly or shipping -> Charge accumulation -> Discharge


# ESD Protection Network Examples

 

Basic ESD protection network: diodes clamp the signal level

$$-0.7V < V_A < V_{DD} + 0.7V$$

$I_D < \text{several tens of mA}$

 


Protection network with thick-oxide transistor: effective in excess of 3kV in HBM-ESD test

$M_1, M_2$ : thick oxide device w/  $V_T$  of 20~30V


$M_3$ : thin oxide device operating in SAT region

# ESD Failure

 


(a) Typical ESD failure modes

 (b) SEM photograph of a failed NMOS (from Diaz *et al.*, 1994)




# Input Series Transmission Gate

 

(a)

Schematic

 


(b)

Symbol




# Inverting Input Circuit with PN

 

- typical  $V_{IL}=0.3V_{DD}$ ,  $V_{IH}=0.7V_{DD}$  for 30% noise margin

# TTL to CMOS level shifting

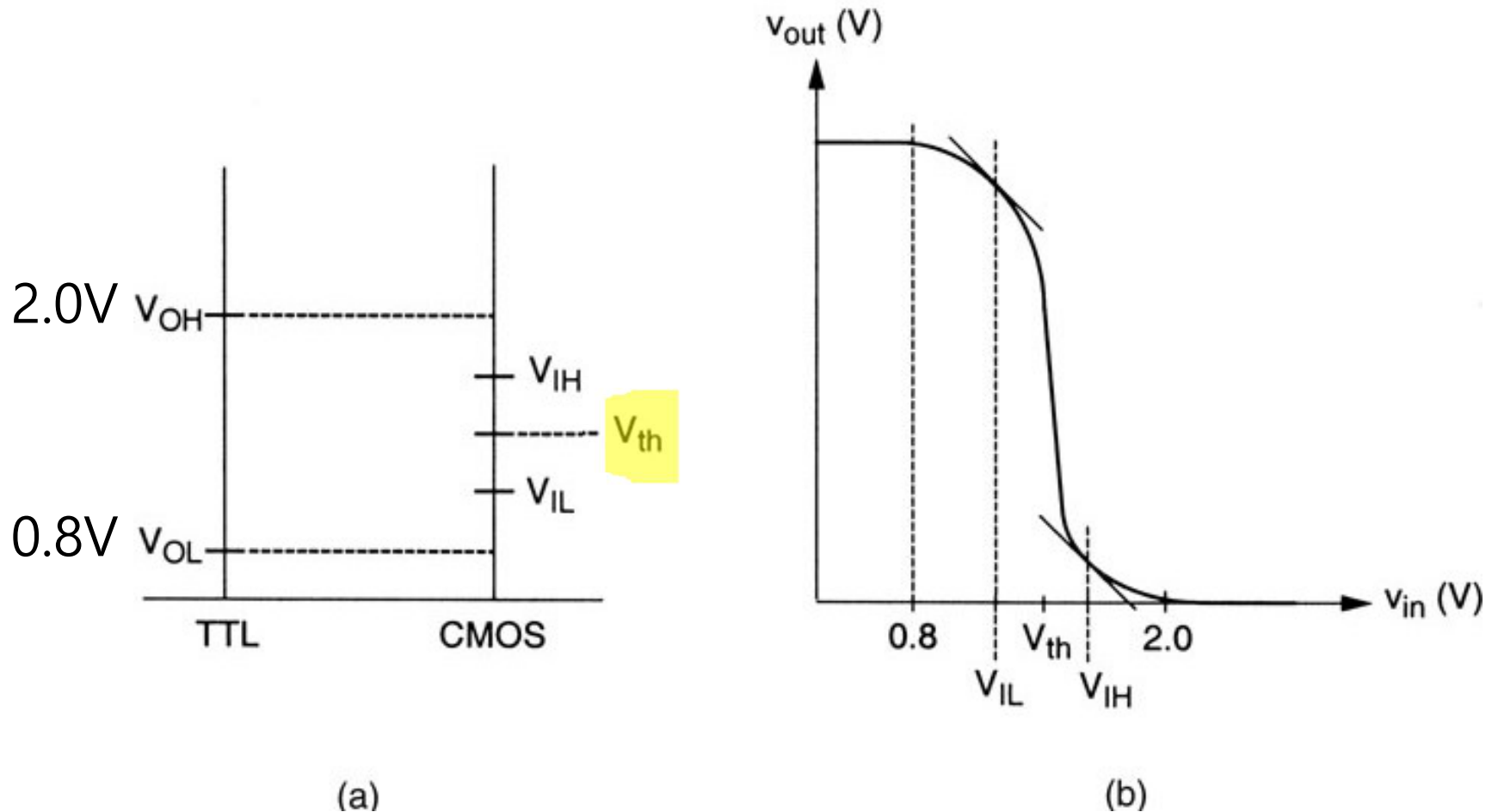

Voltage level of TTL and CMOS

The corresponding VTC

# Designing the Receiving Inverter Gate(1)

- ◆ Adjust the TR ratio such that the saturation voltage at which both transistors operate in saturation region is the **midpoint** between 0.8V and 2.0V
- ◆ Saturation voltage of the inverter gate is

$$V_{sat} = V_{th} = \frac{V_{DD} + V_{Tp} + rV_{Tn}}{1 + r}$$

$$r = \sqrt{\frac{\mu_n C_{ox} W_n / L_n}{\mu_p C_{ox} W_p / L_p}}$$

# Designing the Receiving Inverter Gate(2)

- ◆ From these two equations, we get

$$\frac{W_n / L_n}{W_p / L_p} = \frac{\mu_p}{\mu_n} \left[ \frac{V_{DD} + V_{Tp} - V_{sat}}{V_{sat} - V_{Tn}} \right]^2$$

- ◆ If  $\mu_n = 3\mu_p$  and  $V_{Tn} = -V_{Tp} = 1.0V$  and  $V_{DD} = 5V$ , then in order to achieve

$$V_{sat} = \frac{0.8 + 2.0}{2} = 1.4V$$

- ◆ The nMOS-to-pMOS ratio is

$$\frac{W_n / L_n}{W_p / L_p} = \frac{1}{3} \left[ \frac{5 - 1 - 1.4}{1.4 - 1} \right]^2 = \frac{169}{12}$$

# Designing the Receiving Inverter Gate(3)

- ◆ From the above, we get that  $r=6.5$  and

$$V_{IL} = \frac{2V_{out} - V_{DD} + r^2V_{Tn} + V_{Tp}}{r^2 + 1} = \frac{2V_{out} + 36.25}{43.25}$$

- ◆ where  $V_{out}$  satisfies the following:

$$\frac{r^2}{2}(V_{IL} - V_{Tn})^2 = (V_{DD} - V_{IL} + V_{Tp})(V_{DD} - V_{out}) - \frac{1}{2}(V_{DD} - V_{out})^2$$

- ◆ or

$$21.125(V_{IL} - 1)^2 = (4 - V_{IL})(5 - V_{out}) - \frac{1}{2}(5 - V_{out})^2$$

# Designing the Receiving Inverter Gate(4)

- ◆ Combining these two equations,

$$21.125 \left[ \frac{2V_{out} - 7}{43.25} \right]^2 = \left[ \frac{136.75 - 2V_{out}}{43.25} \right] (5 - V_{out}) - \frac{1}{2} (5 - V_{out})^2$$
$$V_{out} = 4.97V$$

- ◆ and, hence

$$V_{IL} = \frac{2 \times 4.97 + 36.25}{43.25} = 1.07V$$

- ◆ Likewise,

$$V_{IH} = \frac{r^2 (2V_{out} + V_{Tn}) + V_{DD} + V_{Tp}}{r^2 + 1} = \frac{84.5V_{out} + 47.25}{43.25}$$

# Designing the Receiving Inverter Gate(5)

- ◆ where  $V_{out}$  satisfies the following

$$\frac{1}{2}(V_{DD} - V_{IH} + V_{Tp})^2 = r^2 \left[ (V_{IH} - V_{Tn})V_{out} - \frac{1}{2}V_{out}^2 \right]$$

- ◆ or

$$\frac{1}{2}(4 - V_{IH})^2 = 6.5^2 \left[ (V_{IH} - 1)V_{out} - \frac{1}{2}V_{out}^2 \right]$$


- ◆ Combining these two equations, we obtain

$$\frac{1}{2} \left( 4 - \frac{84.5V_{out} + 47.25}{43.25} \right)^2 = 42.25 \left[ \left( \frac{84.5V_{out} + 4}{43.25} \right) V_{out} - \frac{1}{2}V_{out}^2 \right]$$

- ◆ Therefore,

$$V_{out} = 0.206V \quad \text{and} \quad V_{IH} = 1.47V$$

# Variation of the level-shifter VTC

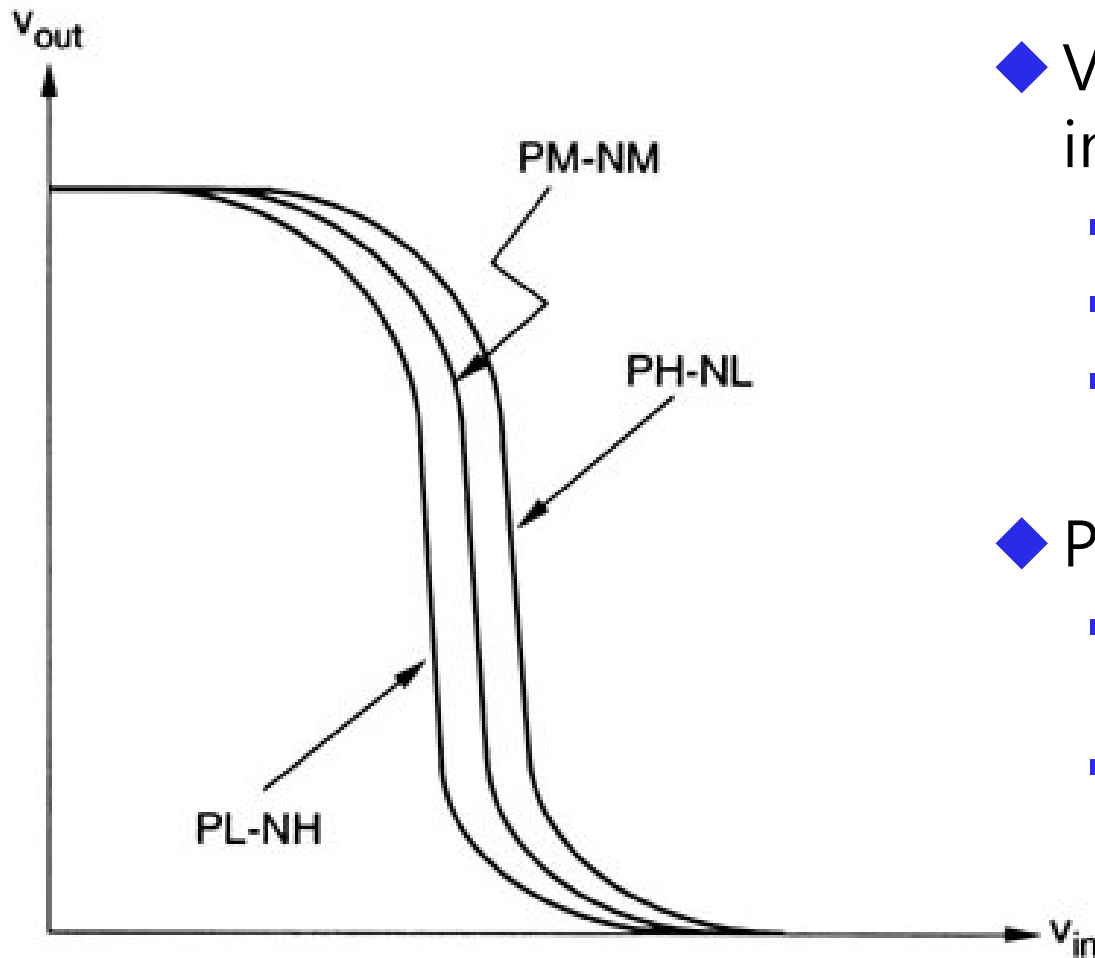

## ◆ Variations to consider in simulation


- Process
- Temperature
- Supply voltage

## ◆ Process variation

- Strong pMOS(PH) - Weak nMOS(NL)
- Weak pMOS(PL) - Strong nMOS(NH)



 
# Non-inverting TTL Level-shifting Circuit



(a)


Schematic

 

(b)


Symbol

# Input Pad Circuit with Schmitt Trigger

 

(a)

Schematic

 


(b)


Symbol

- ◆ Negative-going logic threshold voltage=1V
- ◆ Positive-going logic threshold voltage=4V

# Tristable Output Circuit

 


(a) Symbol

 

(b) Circuit 1

- ◆ 12 TRs
- ◆ Small area

 


(c) Circuit 2

- ◆ 4 TRs
- ◆ Large area

(Last stage TRs need to be large)
 
# Typical Output Circuit Current During Switching (1)



## ◆ Capacitor load

- Initially charged to  $V_{DD}=5V$
- Sink the current to GND @ Clock signal

$$I_{max} \frac{t_s}{2} = C_{load} V_{DD}$$

$$\left[ \frac{di}{dt} \right]_{max} \geq \frac{I_{max}}{t_s / 2} = \frac{2I_{max}}{t_s}$$

## ◆ Thus,

$$\left[ \frac{di}{dt} \right]_{max} \geq \frac{4C_{load} V_{DD}}{t_s^2}$$

# Typical Output Circuit Current During Switching (2)


- ◆ If  $C_{load} = 100\text{pF}$  and  $t_s = 5\text{ns}$ ,

$$\left[ \frac{di}{dt} \right]_{\max} \geq \frac{4 \times 100 \times 10^{-12} \times 5}{(5 \times 10^{-9})^2} = 80 \frac{\text{mA}}{\text{ns}}$$

- ◆ And for a bonding wire with  $L=2$ ,  $[nH]$


$$L \left[ \frac{di}{dt} \right]_{\max} \geq 160\text{mV}$$

# Circuit for Reducing ( $di/dt$ ) Noise

 


- ◆ At strobe signal( $ST$ ), the last driver TRs are precharged
- ◆ If  $r=1$  and  $ST=high$ , the gate voltages can be precharged to  $V_{DD}/2$  before  $CK$  goes to high
 
# Another Circuit for Reducing $(di/dt)$ Noise



- ◆ Transmits only differential signals


# Timing Diagram Of the Driver Circuit

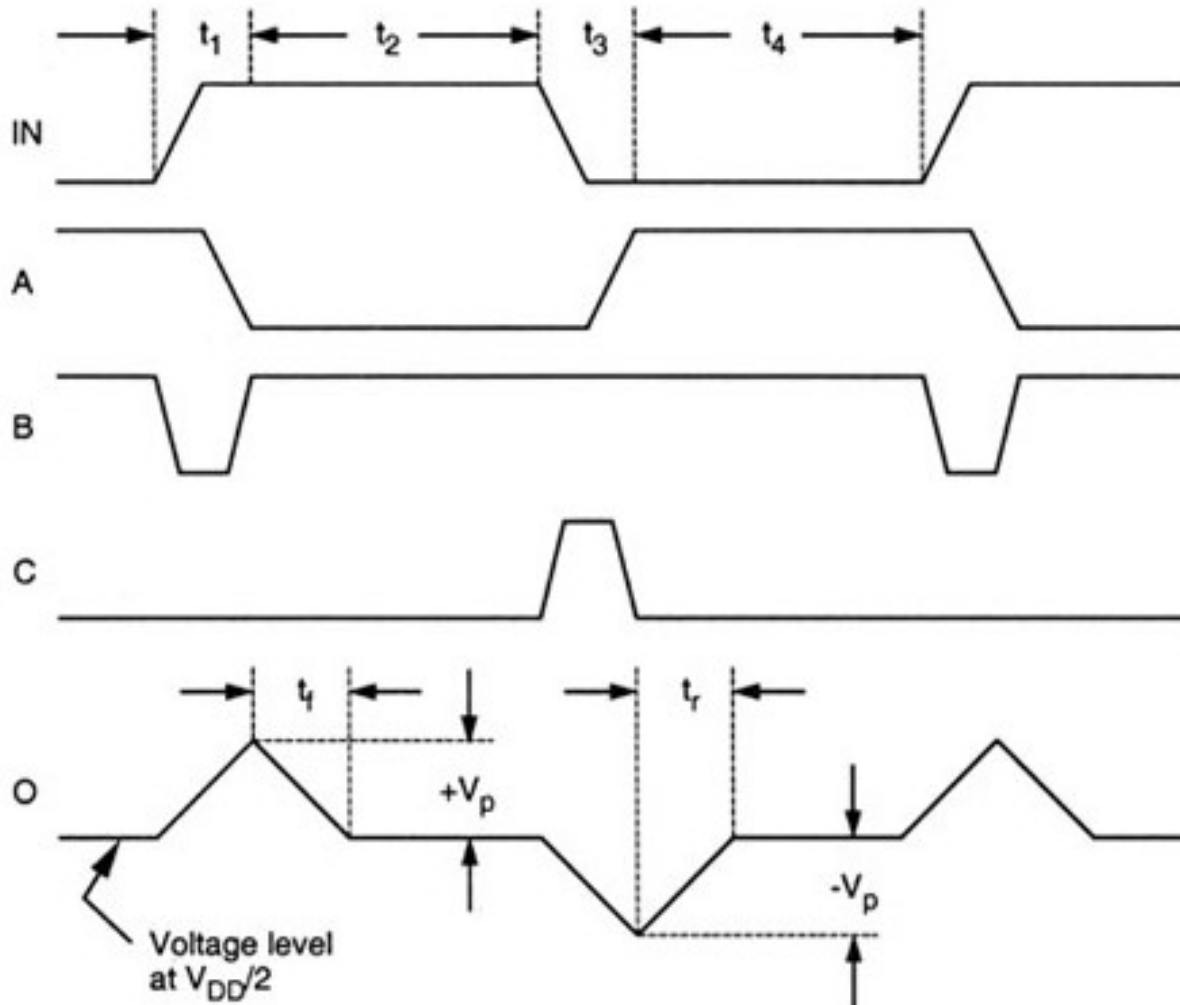


- ◆ The circuit produces pulses at nodes B and C only when input changes
- ◆ Output is at  $V_{DD}/2$  during the quiescent periods
- ◆ Phase splitter is used to generate differential pairs




# Receiver Circuit for Differential Data

 

# Bidirectional Buffer with TTL Input

 


(a) Schematic

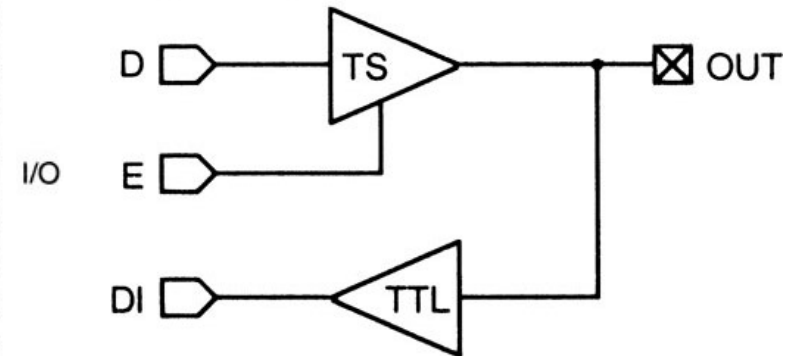

(b) Block diagram
 
# Layout of a Bidirectional I/O Pad Circuit




Courtesy of  
MOSIS


# On-Chip Clock Generation and Distribution

- ◆ Clock signal- heartbeats of digital systems
- ◆ Skew
  - **Spatial** clock uncertainty due to PVT variations of clock buffers and interconnect lines in clock distribution network
- ◆ Jitter
  - **Temporal** clock uncertainty from the clock generator and clock buffers
- ◆ About 10% of cycle time is expended to allow realistic clock jitter and skews in computer systems

# Clock jitter, skew

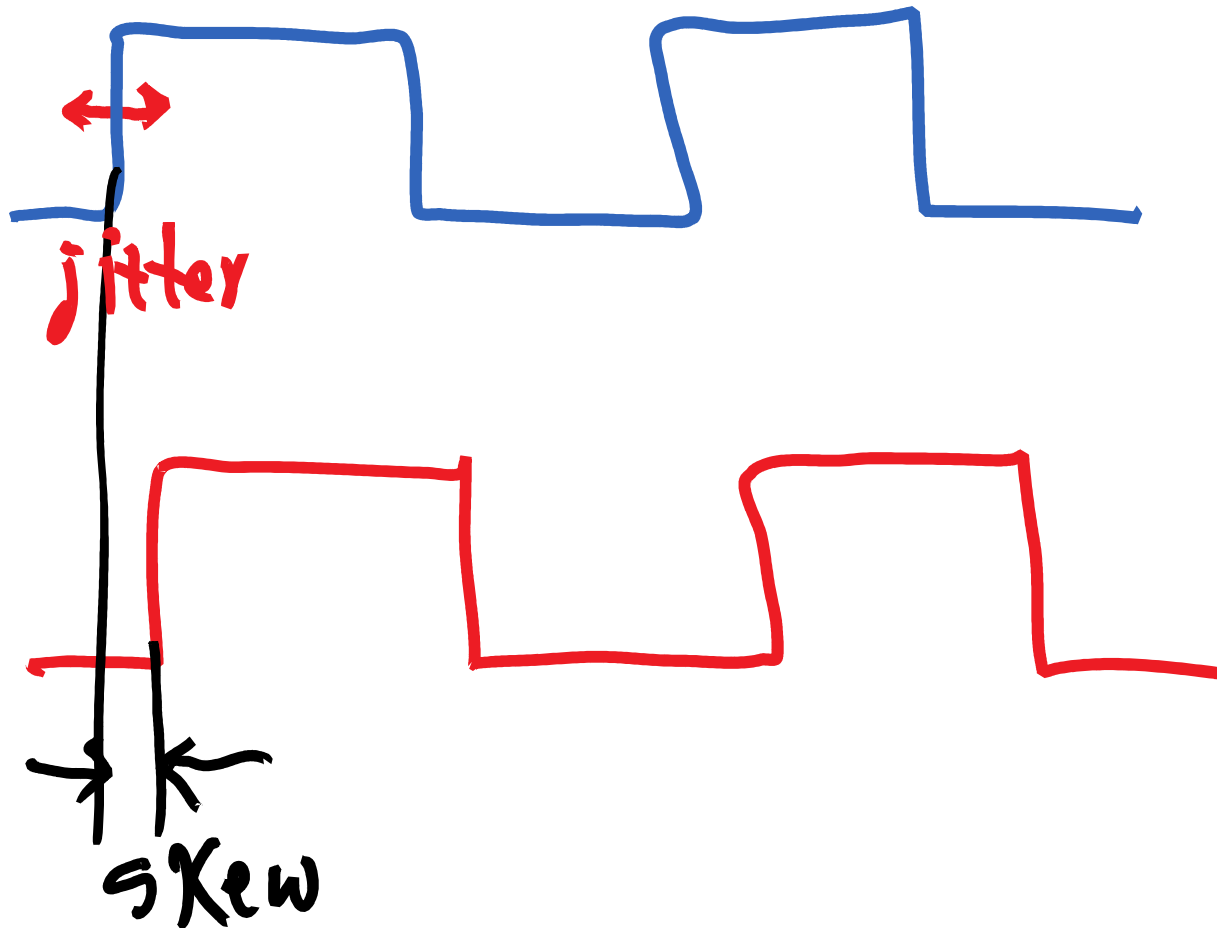


# Simple Clock Generator

 

- For low-end microprocessor chips
- Process-dependent
- Unstable



# Pierce Crystal Oscillator

 

- ◆ Good frequency stability
- ◆ Near series-resonant circuit
- ◆ Internal series resistance and external load
  - determines the frequency and stability
- ◆ Internal inverter
  - generates the voltage difference
- ◆ External inverter
  - amplify the clock signal

# Crystal Osc


## Quartz Crystal Equivalent Model

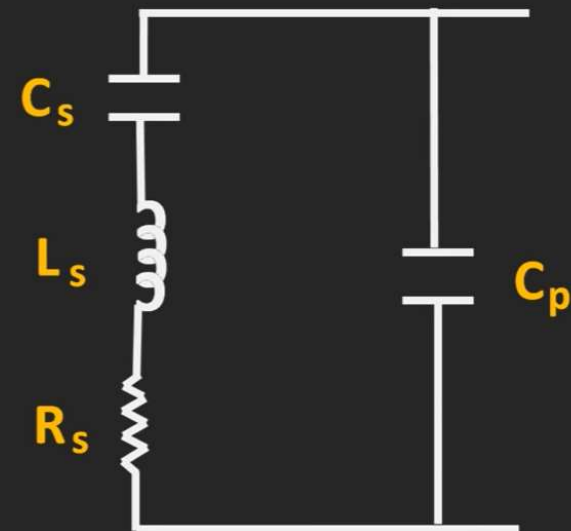 


$C_s$  - Motional Capacitance



# Feedback in Crystals Osc.

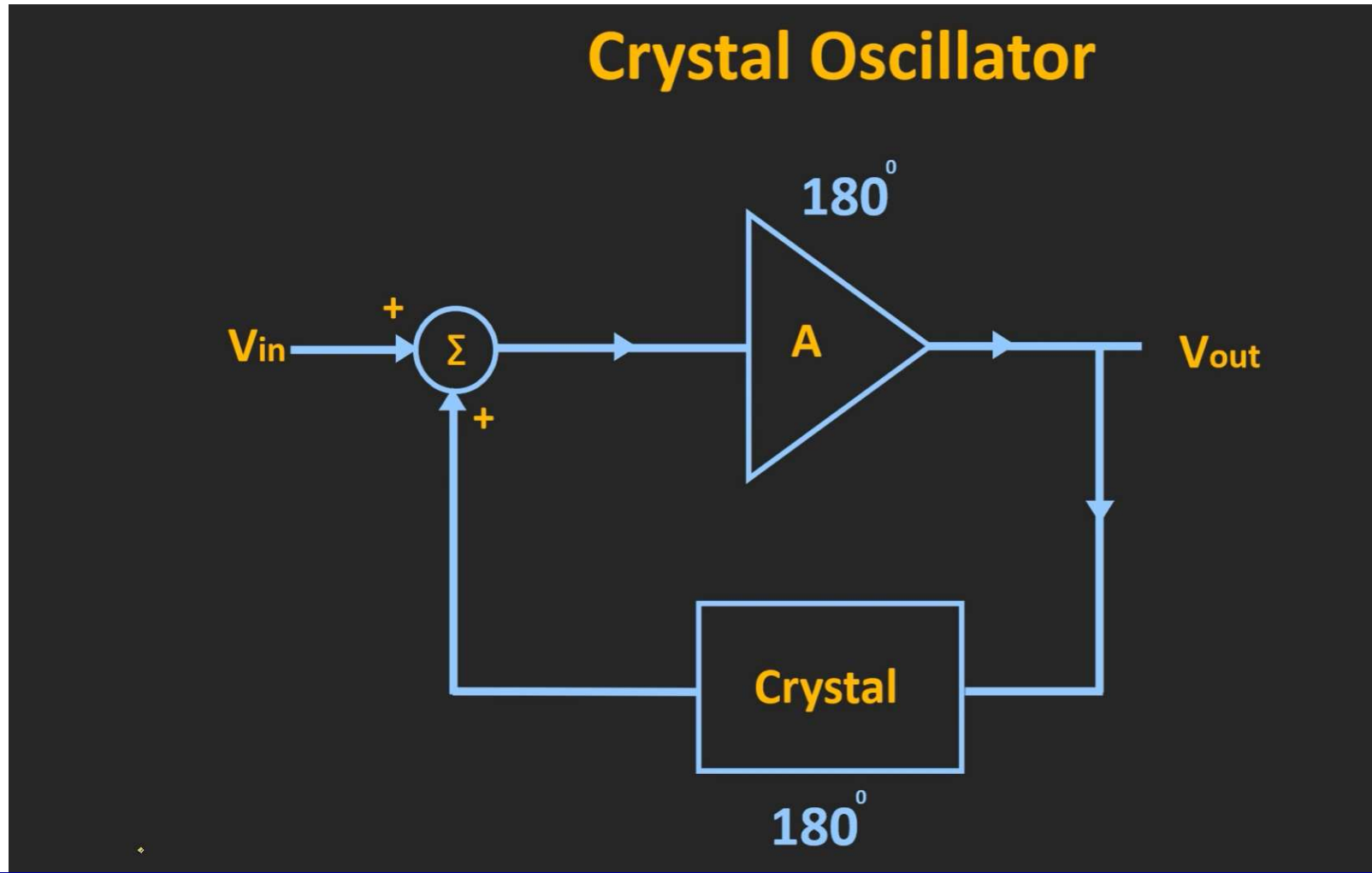

## Pierce Oscillator

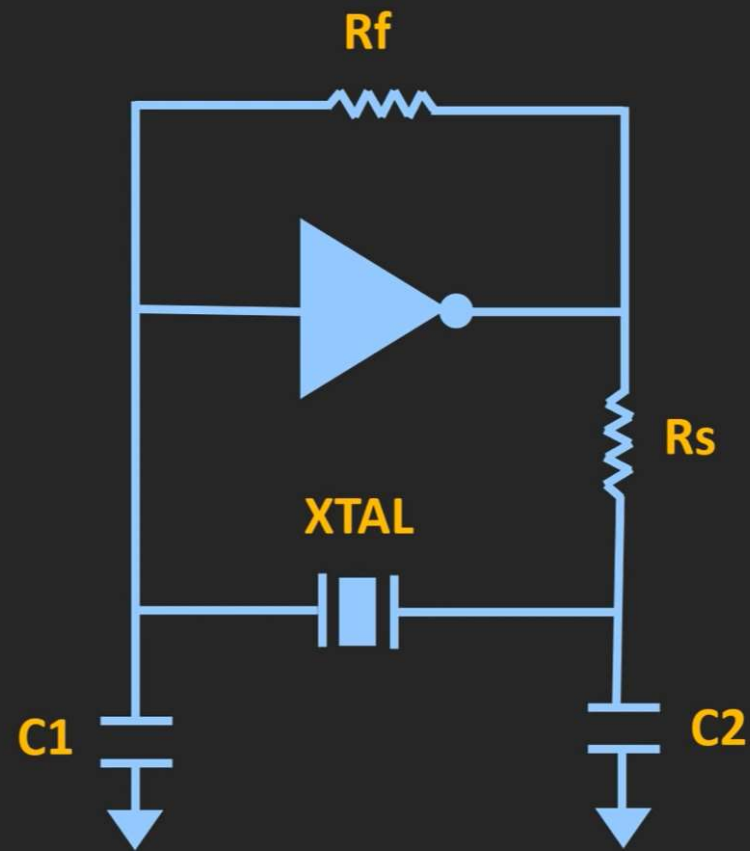

# Osc. Frequency

A quartz crystal can be modeled as an electrical network with a low-impedance (series) and a high-impedance (parallel) resonance points spaced closely together. Mathematically (using the Laplace transform), the impedance of this network can be written as:


$$Z(s) = \left( \frac{1}{s \cdot C_1} + s \cdot L_1 + R_1 \right) \parallel \left( \frac{1}{s \cdot C_0} \right),$$

or


$$Z(s) = \frac{s^2 + s \frac{R_1}{L_1} + \omega_s^2}{(s \cdot C_0) \left[ s^2 + s \frac{R_1}{L_1} + \omega_p^2 \right]}$$

$$\Rightarrow \omega_s = \frac{1}{\sqrt{L_1 \cdot C_1}}, \quad \omega_p = \sqrt{\frac{C_1 + C_0}{L_1 \cdot C_1 \cdot C_0}} = \omega_s \sqrt{1 + \frac{C_1}{C_0}} \approx \omega_s \left( 1 + \frac{C_1}{2C_0} \right) \quad (C_0 \gg C_1)$$

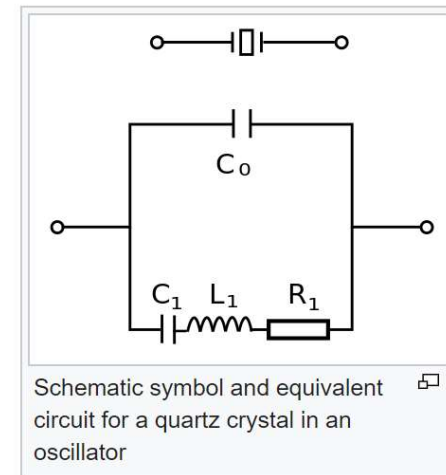where  $s$  is the complex frequency ( $s = j\omega$ ),  $\omega_s$  is the series resonant angular frequency, and  $\omega_p$  is the parallel resonant angular frequency.




# Phase-Locked Loop

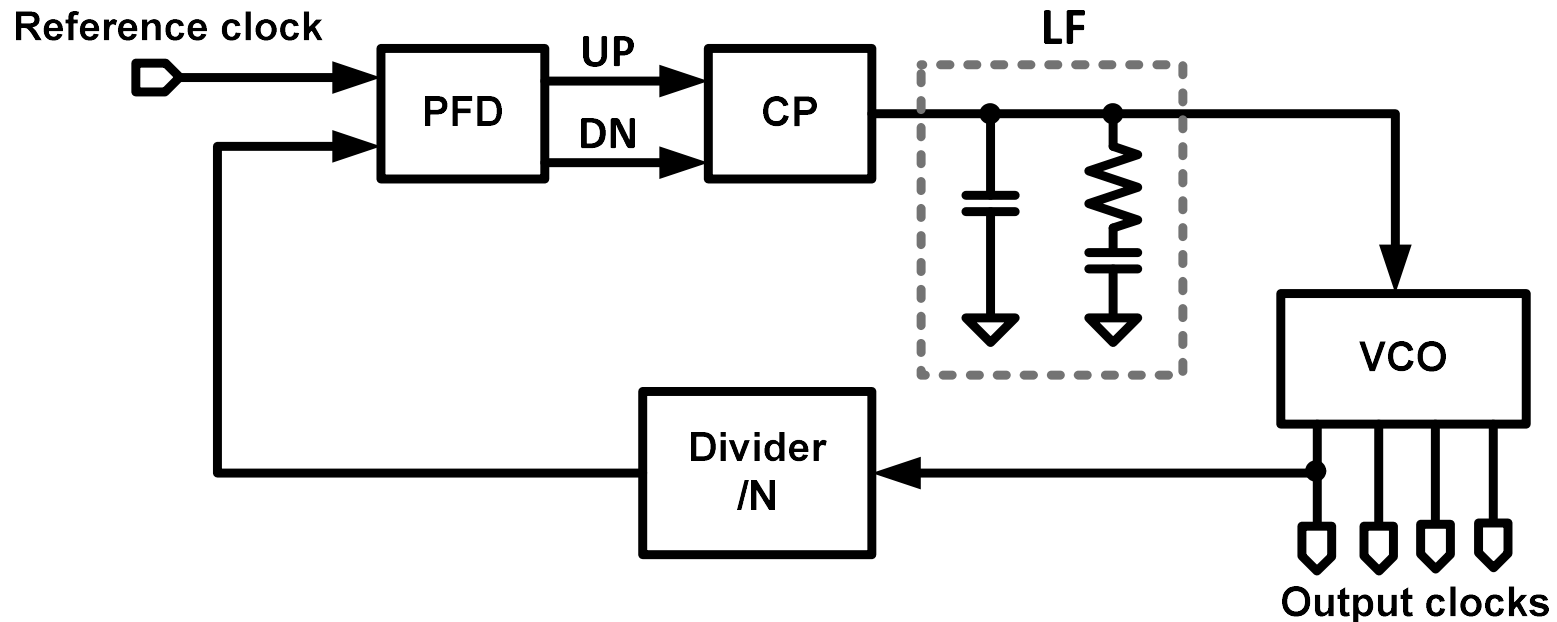


- ◆ The most common on-chip clock generator
- ◆ Easy multiplication of frequency
  - Frequency of VCO : N times as faster as the reference clock


# Phase Frequency Detector(PFD)

 

# Output Pulses of PFD

 

 - ◆ Reference clock comes faster than the divided VCO clock
  - UP



- ◆ The divided VCO clock comes earlier than the reference clock
  - DN

# Locked state of PLL


## ◆ Locked state of PLL

- Two clocks come very close

## ◆ Dead zone problem

- If the phase difference of two PFD inputs is as small as few pico seconds, the PFD cannot generate a proper pulse
- because it takes time for the PFD circuit to respond to the input signals
- In this case, the pulse width of PFD output would be too small to represent the exact amount of phase error
- It can be solved by inserting a buffer at the reset path to add some delay

# Input and Output Characteristic of PFD

 



# Oscillator

- ◆ Oscillator - unstable system that generates repetitive signals
  - Oscillation conditions
    - Loop gain  $> 1$
    - Total phase shift = 360
  - Barkhausen criterion
    - Loop gain, phase shift:  $|H(j\omega_0)| \geq 1, \angle H(j\omega_0) = 180^\circ$
    - Simple and intuitive
    - Bode plot
    - Necessary but not sufficient to stability
  - Nyquist stability criterion
    - Accurate
    - Root-locus plot

# Voltage Controlled Oscillator(VCO)

## ◆ VCO

- Oscillator whose frequency is controlled by the voltage
- Noise budget of the VCO
  - determines the jitter performance and loop bandwidth of PLL

$$\omega_{out} = \omega_0 + \int K_{VCO} V_{CTRL} dt$$

- $\omega_{out}$  : output frequency
- $\omega_0$  : initial VCO frequency
- $K_{VCO}$  : VCO gain
- $V_{CTRL}$  : VCO control voltage


# Factors to Consider in VCO (1)

- ◆ Free running frequency
  - VCO operating frequency in the absence of control voltage
- ◆ Tuning range
  - The range of frequency that VCO can generate
  - It determines the operating range of PLL
- ◆ Noise rejection ability
  - A measure of how much noise from external environment the VCO can filter out
  - Supply noise rejection / Common-mode noise rejection

# Factors to Consider in VCO (2)


- ◆ Power consumption
  - Critical to low-power applications
  - The more power, the better jitter performance
- ◆ Output signal purity
  - The most important factor
  - Clock jitter / phase noise

# Harmonic Oscillator

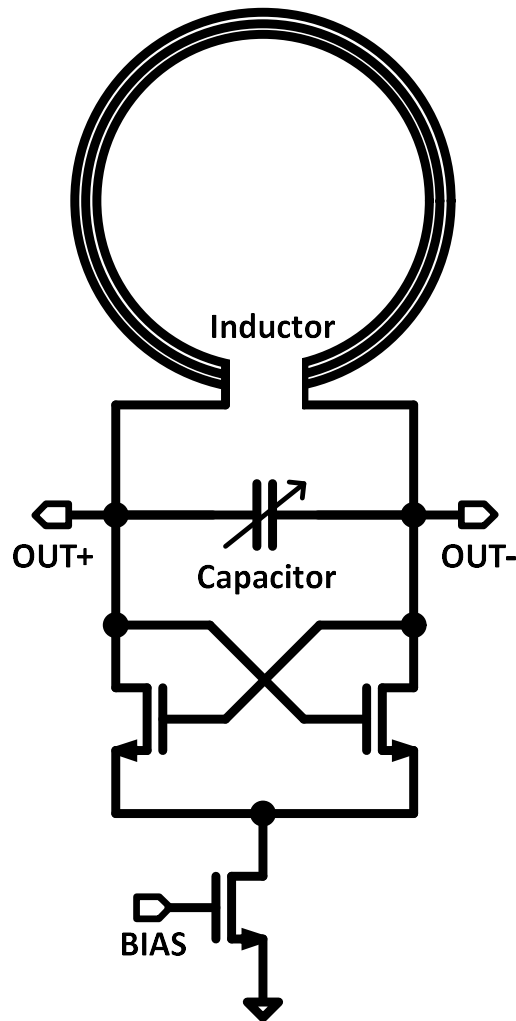


- ◆ Resonance of the energy components such as LC-tank
- ◆ Good signal purity
- ◆ But bulky (inductor and capacitor)
- ◆ Tuning range – narrow
- ◆ Not suitable for digital systems

# Relaxation Oscillator

 


- ◆ Chain of delay elements
- ◆ Easy to design
- ◆ Compact size
- ◆ Bad signal purity
- ◆ Typical example: ring oscillator

# VCO with Supply Noise Rejection

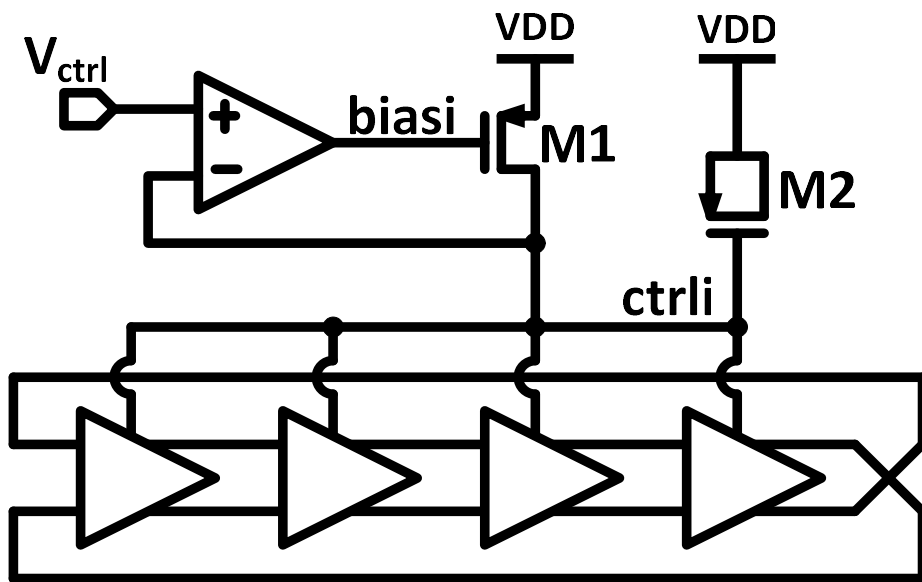

- ◆ Regulated voltage ctrli
  - robust to supply noise
- ◆ Opamp BW > PLL BW
- ◆ M1: large
  - Enough voltage headroom
  - Wide operating range of VCO
- ◆ M2: suppress ripples on ctrli
- ◆ Dominant pole on node ctrli
  - Compensation capacitor and resistor are needed between node biasi and ctrli


# Delay Cell

 


- ◆ Pseudo-differential type
- ◆ Back-to-back inverters are used
- ◆ ctrli controls the delay
- ◆ Body of PMOS is tied to the source
  - Linear change in frequency



# Charge Pump(CP)

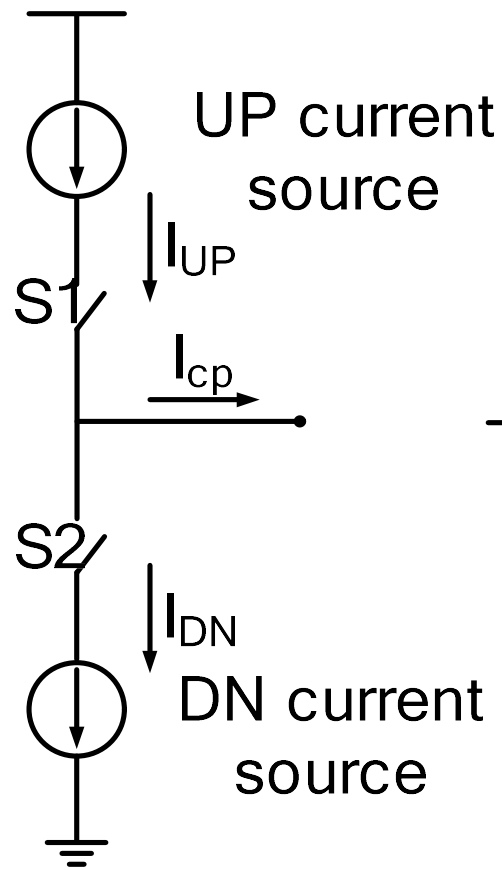


(a) Conceptual structure

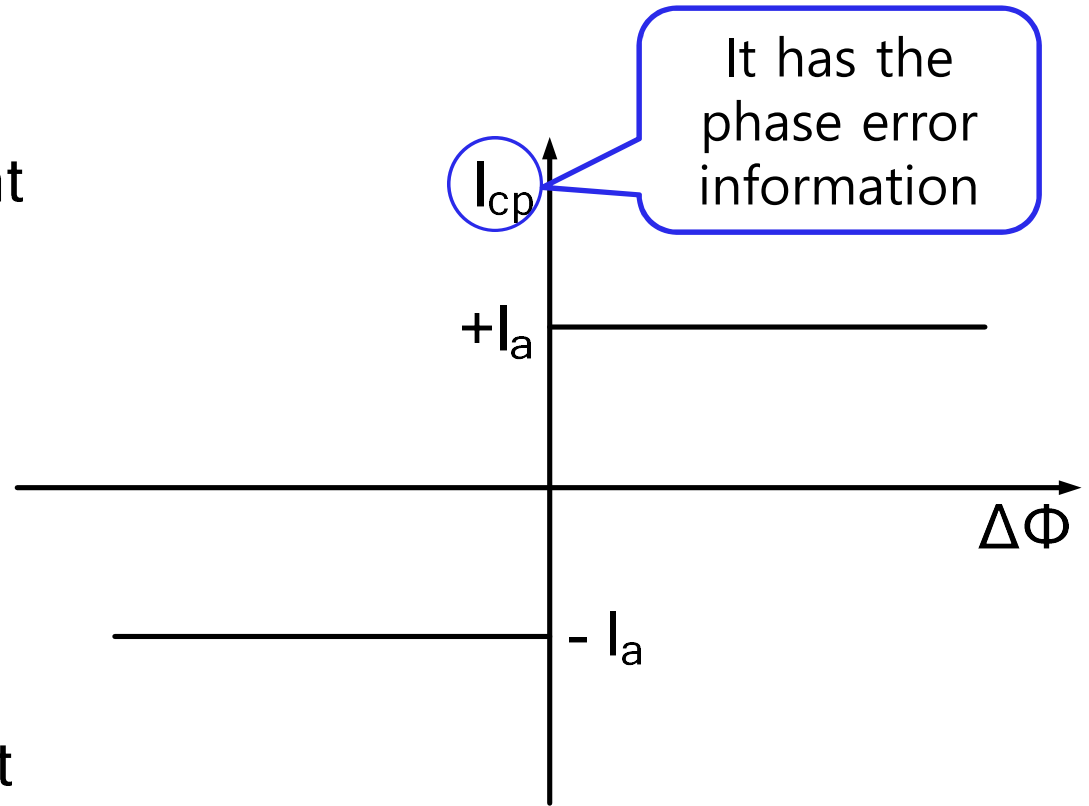


(b) Ideal output current of CP

# Loop Filter (1)

 

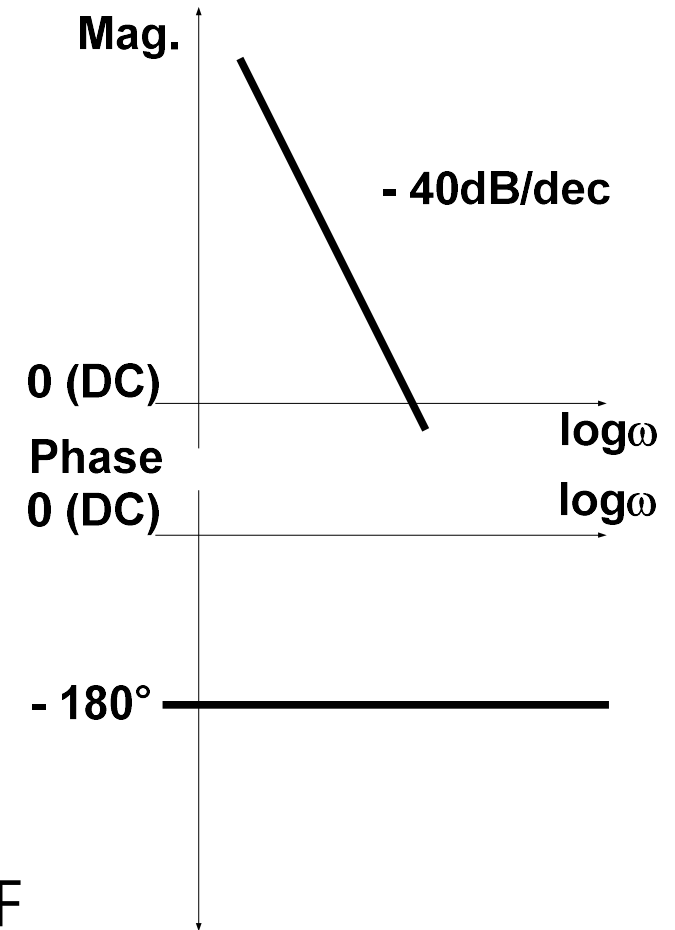
$$\frac{V_{ctrl}}{I_{cp}} = \frac{1}{sC}$$




- ◆ Loop Filter(LF) converts current from CP to voltage
- ◆ One pole at VCO, the other pole at LF
  - Two poles at DC -> Unstable

# Loop Filter (2)

 

 
$$\frac{V_{ctrl}}{I_{cp}} = R + \frac{1}{sC} = \frac{sRC + 1}{sC}$$




- ◆ Additional resistor introduces zero for larger phase margin

# Loop Filter (3)

 

$$\frac{V_{ctrl}}{I_{cp}} = \left( R + \frac{1}{sC_1} \right) \parallel \left( \frac{1}{sC_2} \right) = \frac{sRC_1}{s^2 RC_1 C_2 + s(C_1 + C_2)}$$

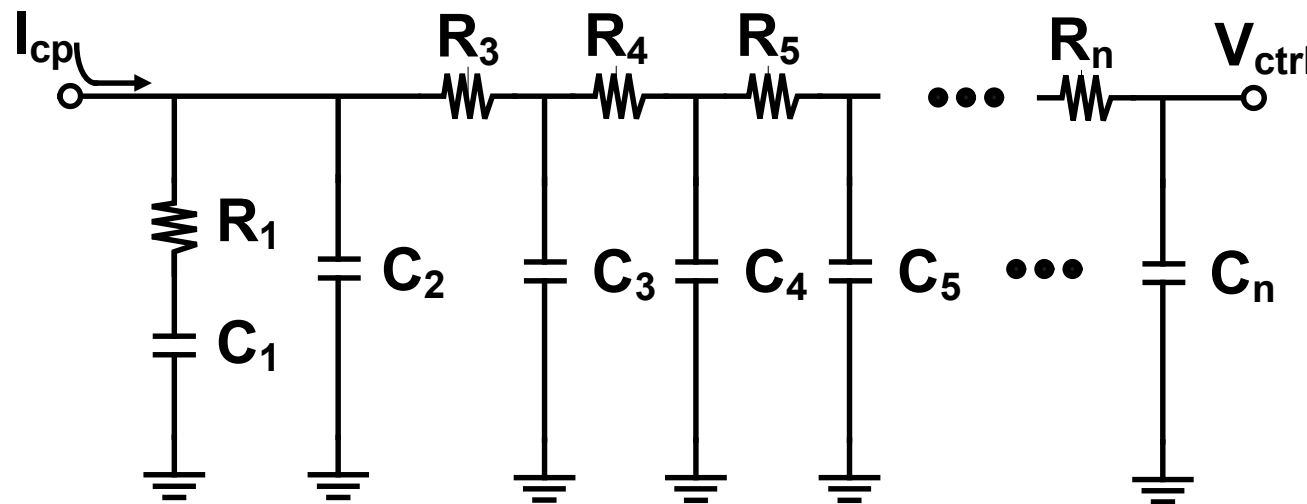◆  $C_2$  reduces fluctuation caused by the IR drop



◆ Higher order LF


- Filters out noise
- $V_{ctrl} < V_{cp}$   
=> Narrow range

# All-Digital PLL(ADPLL)
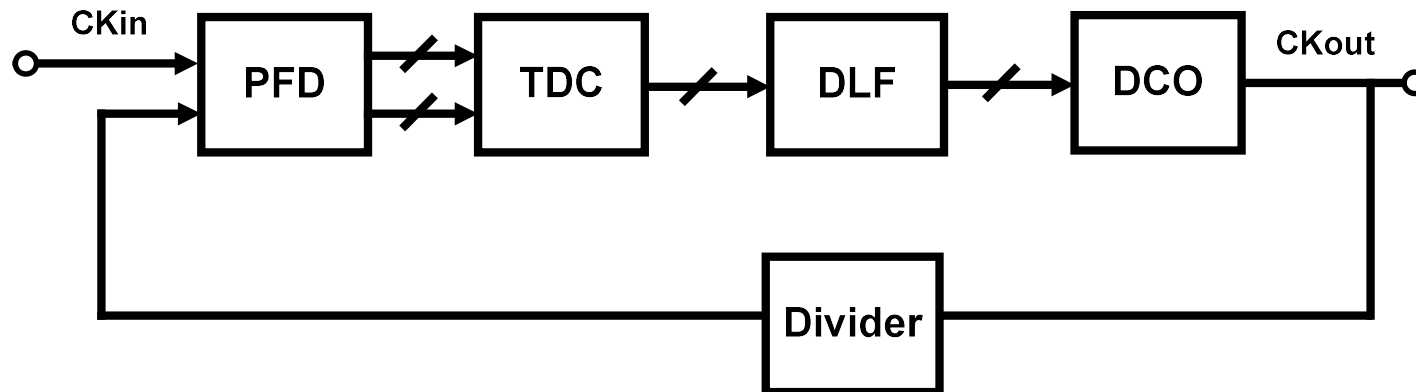
## ◆ Issues in analog PLL in deep-submicron process

- Leakage current in capacitors
- Steady-state power consumption
- Long-term jitter
- Small supply voltage
- High threshold voltage

Narrow PLL  
operating  
range, high  
PLL noise  
sensitivity



◆ ADPLL is introduced

# Components of ADPLL

- ◆ Phase-Frequency Detector(PFD)
- ◆ Time-to-digital converter(TDC)
  - converts phase difference to digital words
  - replaces CP
- ◆ Digital loop filter(DLF)
  - filters out digital input words
- ◆ Digitally controlled oscillator(DCO)
  - replaces a VCO

# Advantage/Disadvantage of ADPLL


## ◆ Advantage

- Excellent timing accuracy
- No analog circuits that suffer from small voltage headroom and relatively high threshold voltage
- Robust to PVT variation
  - Only TDC and DCO are sensitive
- Good for deep-submicron processes

## ◆ Disadvantage

- Limited resolution in phase detection by TDC
- Small resolution in frequency control by DCO
- Possibly more jitter than analog PLL


# Delay-Locked Loop(DLL)

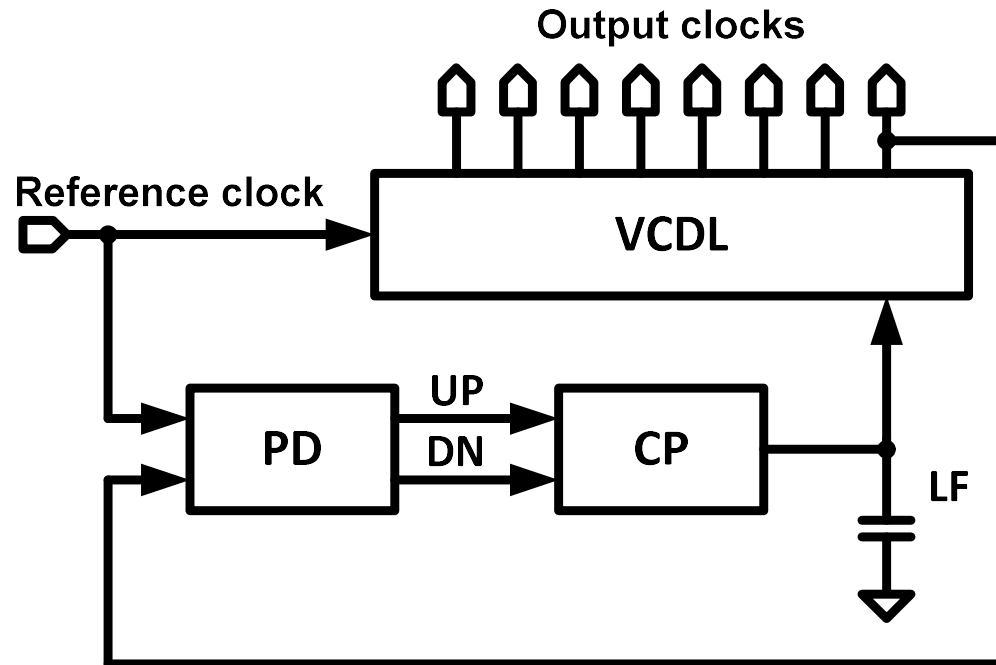

- ◆ VCDL adjusts the delay by a control voltage
  - ◆ DLL adjusts the phase of VCDL / PLL modifies the frequency
  - ◆ PLL has one more pole than DLL (2<sup>nd</sup>-order)
  - ◆ No stability issue in DLL
-



# Simulation of DLL Locking Process

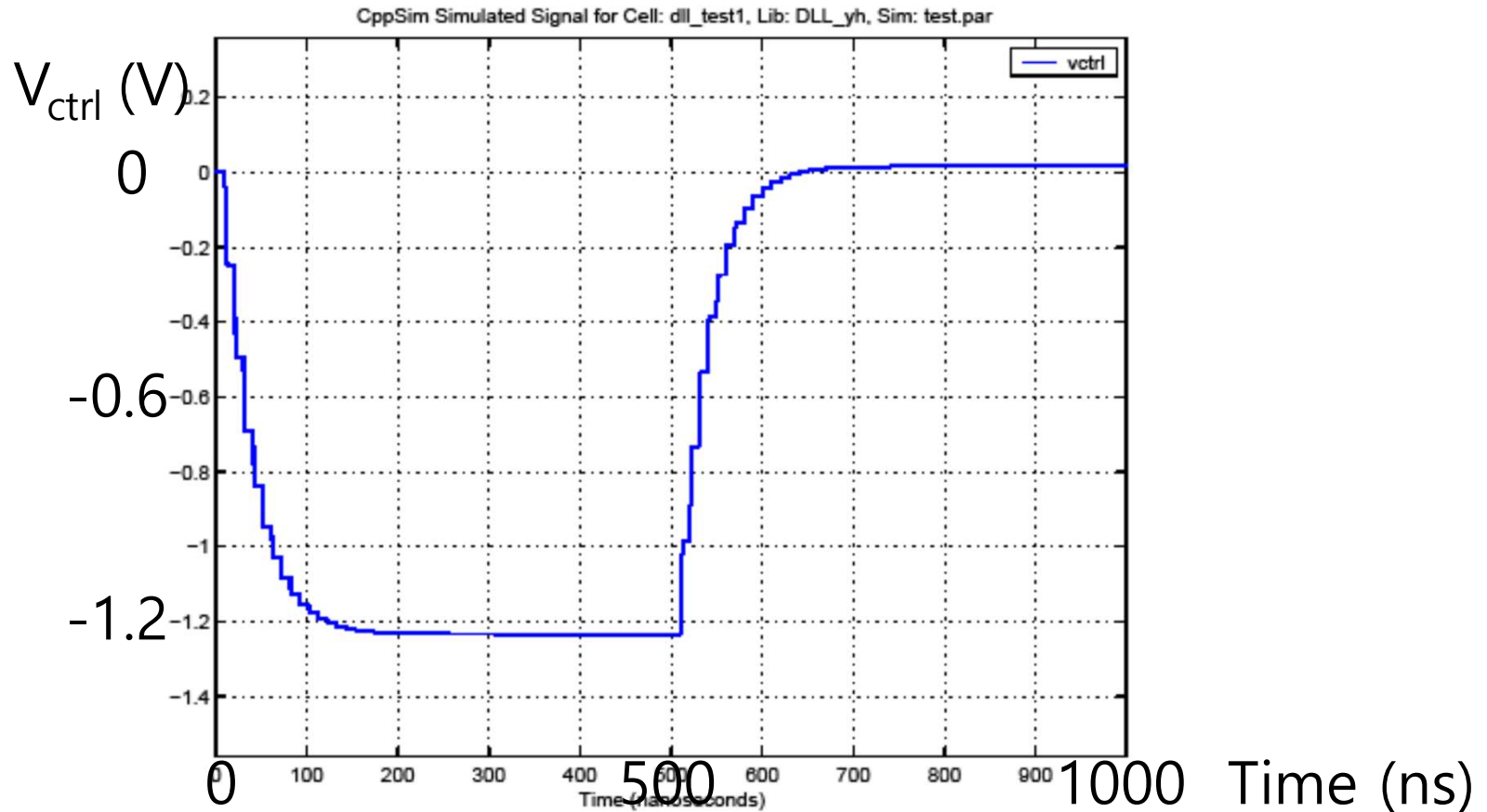


- ◆  $V_{ctrl}$  changes when abrupt phase shift occurs at 0ns and 500ns

# Comparison of PLL and DLL



PLL	DLL
VCO-Jitter accumulation	VCDL–No jitter accumulation
Higher-order system <ul style="list-style-type: none"> <li>- Can be unstable</li> <li>- Hard to design</li> </ul>	1 <sup>st</sup> -order system <ul style="list-style-type: none"> <li>- Always stable</li> <li>- Easier to design</li> </ul>
Costly to integrate LF	Easier to integrate LF
Less Ref. signal dependent	Ref. signal dependent
Easy Freq. multiplication	Difficult Freq. multiplication
No limited locking range	Limited locking range $T_{\text{Ref}} < \text{VCDL}_{\text{delay}} < 3T_{\text{Ref}}/2$
EMI problem	Less EMI Problem

# Non-overlapping Clock Generator

 


◆ Two phase clock generator

◆ Clock decoder waveform

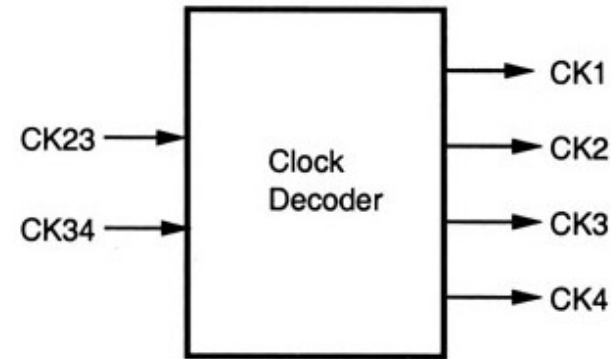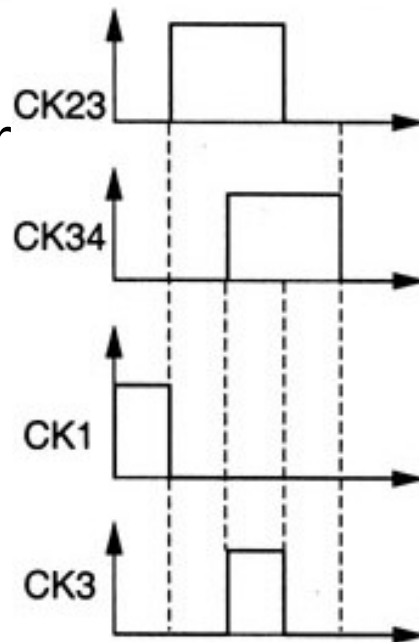


◆ Clock decoder symbol

 


◆ Clock decoder schematic

# Uniform Clock Distribution(H-tree)

 


- ◆ All clock signals are distributed with a uniform delay
- ◆ Difficult to achieve due to constraints of routing and fanout

# Zero-Skew Network By CAD

 


- ◆ An example of the zero-skew clock routing network, generated by a computer-aided design(CAD) tool

# Buffered Clock Distribution Network

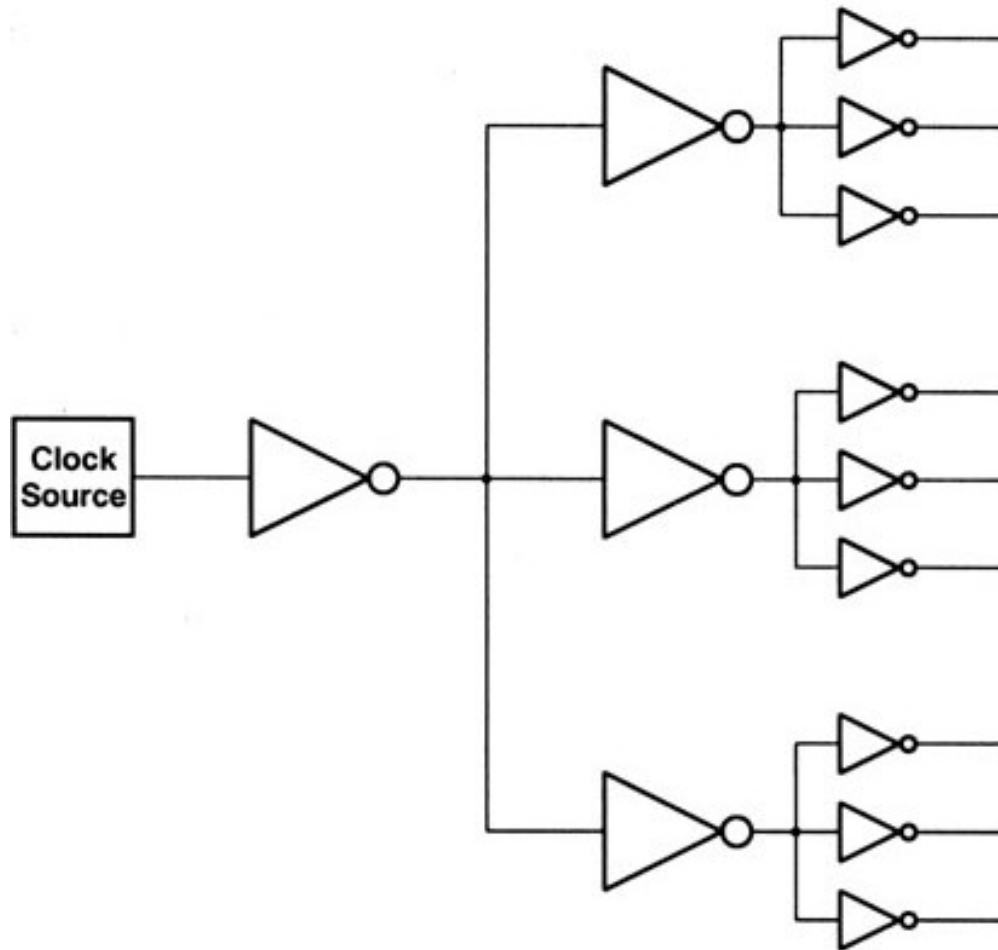

- ◆ Every stage has the same number of fan-outs
- ◆ Essential for the balanced clock delays
 
# Clock Distribution in the DEC Alpha Chip




- ◆ Mesh pattern of interconnect wires
- ◆ Clock signals are kept in phase across the entire chip
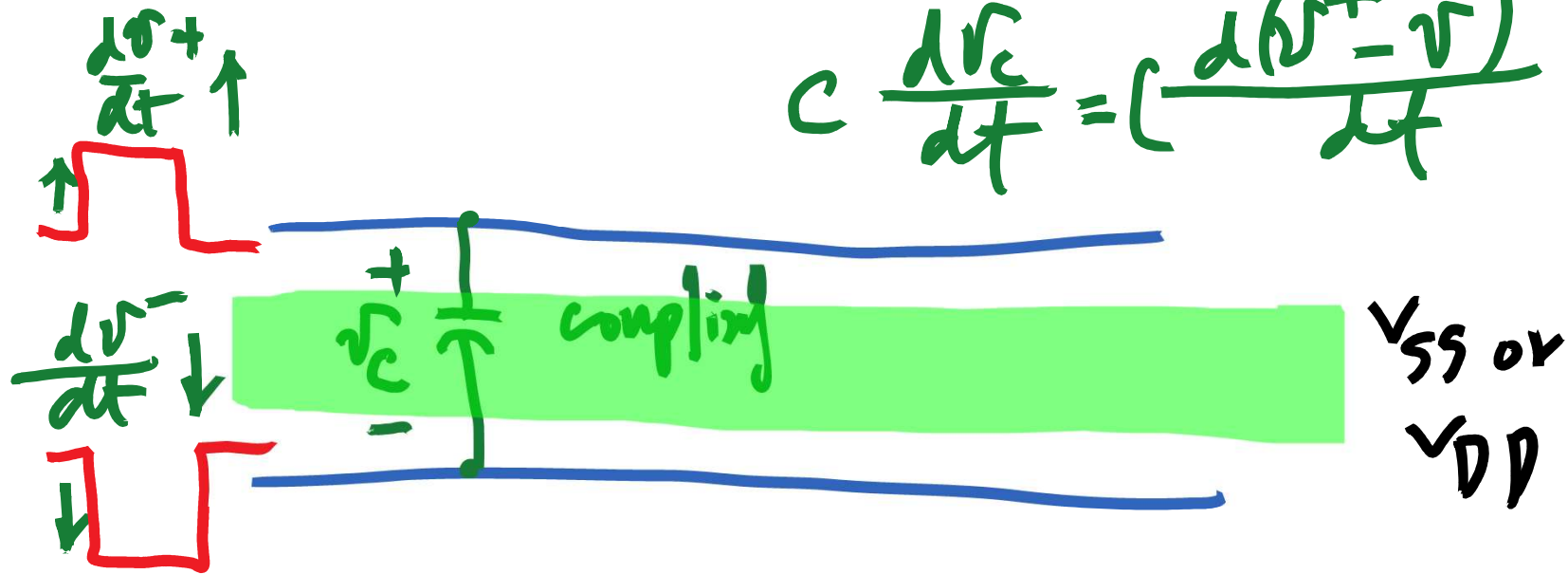
# Considerations For VLSI Design


- ◆ Ideal duty cycle of a clock = 50%
  - ◆ Feedback based on the voltage average improves the duty
  - ◆  $t_r$  and  $t_f$  should not be reduced excessively for prevention of reflection in the interconnection network
  - ◆ Small load cap reduces the fan-out, the interconnect lengths, and the gate capacitances
  - ◆ Small impedance of clock line by increasing the  $(w/h)$  ratios (the ratio of the line width to vertical separation distance of the line from the substrate)
  - ◆ Cross-talk prevention
    - Adequate separation between clock lines
    - Power or ground rail between high-speed lines
-



$$C \frac{dV_c}{dt} = C \frac{d(V^{+} - V^{-})}{dt}$$




# Latch-Up (1)

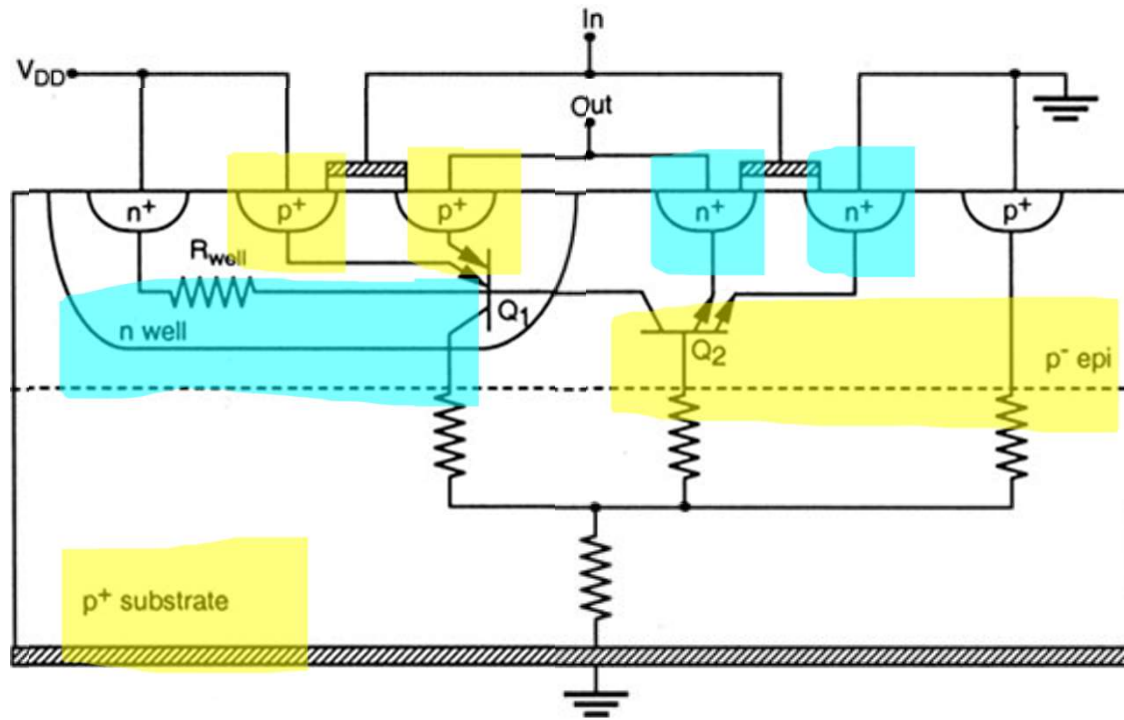

Cross-sectional view


- ◆ Silicon-controlled rectifier(SCR) with positive feedback
- ◆ Excessive current flow -> device damage
- ◆ Concerns of esp. I/O circuits

# Circuit Model of Latch-Up

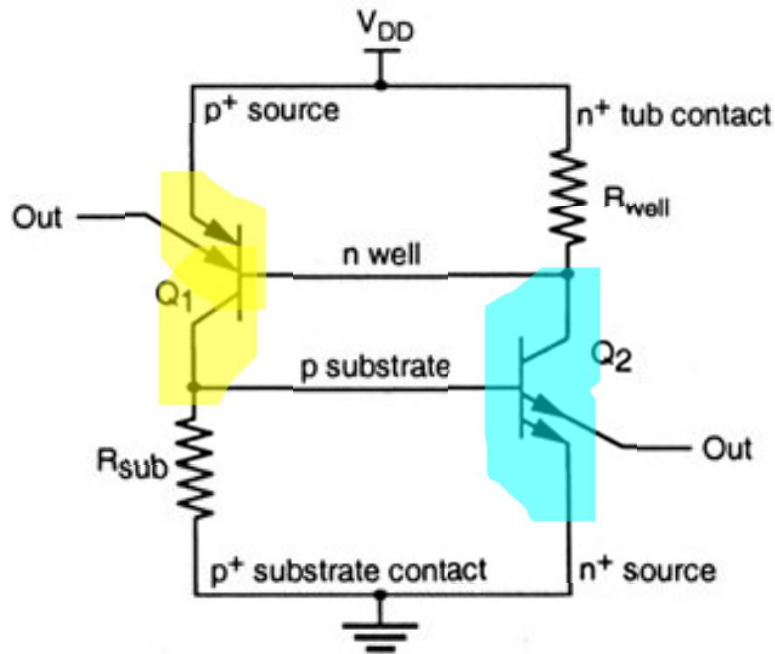

- ◆  $R_{\text{well}}$ :  $1\text{k}\Omega \sim 20\text{k}\Omega$
- ◆  $R_{\text{sub}}$ : a few  $\Omega \sim$  several hundred  $\Omega$
- ◆ Assumption
  - $R_{\text{well}}$  and  $R_{\text{sub}}$  are large enough to be neglected (open circuit)
- ◆ Initial condition
  - Current gain: very low
  - Only reverse leakage currents flows

# Latchup

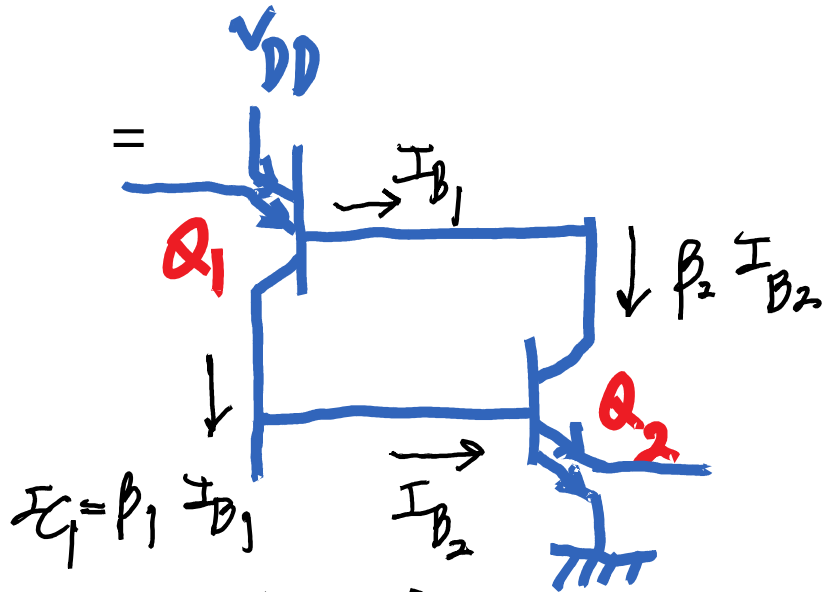


$$I_{C1} = \beta_1 I_{B1}$$
$$= \beta_1 (\beta_2 I_{B2})$$

$$= \beta_1 \beta_2 I_{B2}$$

For latch up

$$\beta_1 \beta_2 > 1$$

# Triggering the Latch-Up

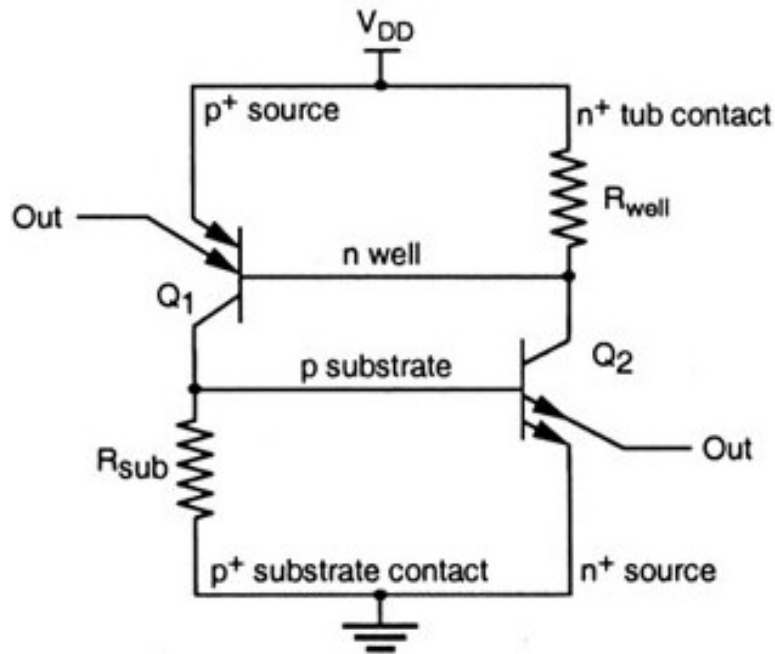

## ◆ Trigger process

- $I_C$  of one of BJTs is increased by an external disturbance
- Feedback loop multiplies it by  $(\beta_1 \cdot \beta_2)$  -> positive feedback
- Low-impedance path is formed

## ◆ Trigger condition

$$\beta_1 \cdot \beta_2 \geq 1$$

- Or


$$\frac{\alpha_1}{1 - \alpha_1} \cdot \frac{\alpha_2}{1 - \alpha_2} \geq 1 \quad \Rightarrow \quad \alpha_1 + \alpha_2 \geq 1$$

$$I_C = \beta I_B$$

$$I_E = (1 + \beta) I_B$$

$$I_C = \alpha I_E$$


# Latchup continued

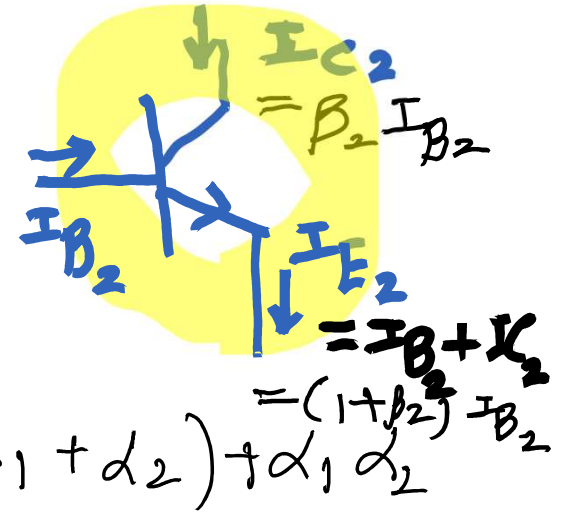

$$\beta_1 \beta_2 = \left( \frac{\alpha_1}{1 - \alpha_1} \right) \left( \frac{\alpha_2}{1 - \alpha_2} \right) > 1$$



$$\alpha_1 \alpha_2 > (1 - \alpha_1)(1 - \alpha_2) = 1 - (\alpha_1 + \alpha_2) + \alpha_1 \alpha_2$$
 
$$\Rightarrow \boxed{\alpha_1 + \alpha_2 > 1}$$



$$V_{DD} = R_T I + V_H$$

# Latch up continued

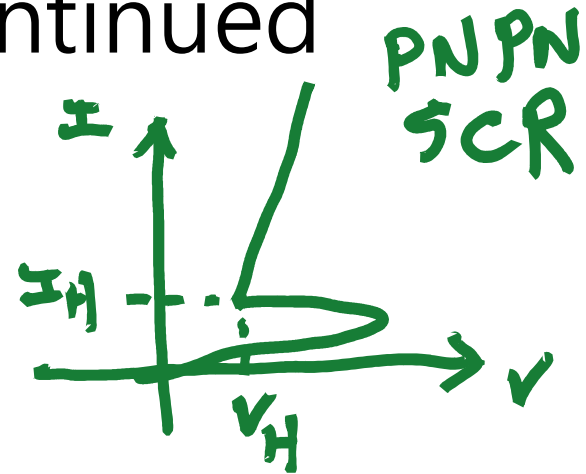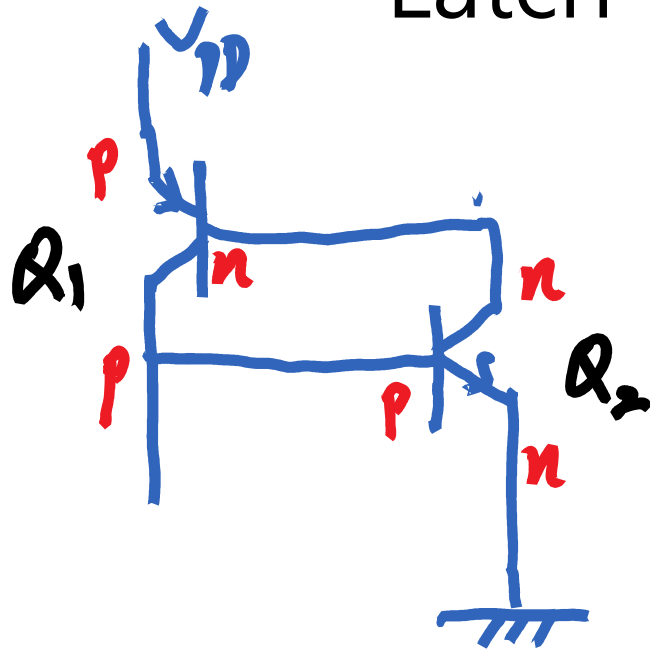

$$\begin{aligned}
 V_H &= V_{EC1}^{sat} + V_{BE2}^{sat} \\
 &= V_{EB1}^{sat} + V_{CE2}^{sat} \\
 &\approx 2V_D
 \end{aligned}$$

## Latchup continued

$$I = I_{C1} + I_{CBO1} + I_{C2} + I_{CBO2}$$

$$= I_{C1} + I_{C2} + I_{CBO}$$

$$\approx \alpha_1 I_E + \alpha_2 I_{E2} + I_{CBO}$$

$$= \alpha_1 (I - I_{RW}) + \alpha_2 (I - I_{RS}) + I_{CBO}$$

$$= (\alpha_1 + \alpha_2) I - \alpha_1 I_{RW} - \alpha_2 I_{RS} + I_{CBO}$$

$$\Rightarrow I = \frac{I_{CBO} - \alpha_1 I_{RW} - \alpha_2 I_{RS}}{1 - (\alpha_1 + \alpha_2)}$$

$$\Rightarrow I_H \left( = \frac{V_{DD} - 2V_D}{R_T} \right) \text{ for latchup}$$



## Catchup continued

$$I_{RW} = \frac{V_D}{R_W}, \quad I_{RS} = \frac{V_D}{R_S}, \quad I_H = I \Big|_{V_{BO}=0}$$


$$\alpha_1 + \alpha_2 - 1 \Rightarrow \frac{\alpha_1 I_{RS} + \alpha_2 I_{RW}}{\frac{V_{DD} - V_H}{R_T}}$$

$$= \frac{\frac{R_T}{R_S} \alpha_1 + \frac{R_T}{R_W} \alpha_2}{\frac{V_{DD} - 2V_D}{V_D}}$$

$$\alpha_1 + \alpha_2 \geq 1 + \frac{\frac{R_T}{R_S} \alpha_1 + \frac{R_T}{R_W} \alpha_2}{\frac{V_{DD} - 2V_D}{V_D}}$$
 
# Current-Voltage Characteristics of a SCR

- ◆ Voltage drop across the SCR in latch-up



$$V_H = V_{BE1,sat} + V_{CE2,sat}$$

$$= V_{BE2,sat} + V_{CE1,sat}$$


- $V_H$  : holding voltage
- $I_H$  : holding current
  - Low impedance state if  $I > I_H$

- ◆  $R_T$  : total parasitic R in the current path

# Causes for Latch-Up

- ◆ Large slew rate of VDD during initial start-up
    - Displacement currents
      - By well junction capacitance in the substrate and the well
    - *Dynamic recovery* if the slew rate is not very high
  - ◆ I/O signal swing much over VDD or far below VSS
    - By impedance mismatches in transmission lines
  - ◆ ESD stress
    - Minority carrier injection: clamping device → substrate or well
  - ◆ Sudden transients in buses
    - Due to simultaneous switching of many drivers
  - ◆ Leakage currents in well junctions
  - ◆ Radiation of X-rays, cosmic rays, or alpha particles
-

# Derivation of $I_H$ (1)

 

- ◆ From left figure,

$$I = I_{E1} + I_{RW}$$

$$I = I_{E2} + I_{RS}$$

- ◆ From relations of Q1 and Q2,

$$I_{C1} = \alpha_1 I_{E1} = \alpha_1^0 I$$

$$I_{C2} = \alpha_2 I_{E2} = \alpha_2^0 I$$

- ◆  $\alpha_1^0, \alpha_2^0$  : equivalent collector-to-emitter current gains absorbing the effects of parasitic R into TRs

- ◆ The SCR current  $I$ ,

$$I = I_{C1} + I_{C2} + (I_{CBO1} + I_{CBO2})$$

## Derivation of $I_H$ (2)

- ◆ From above equations,

$$I = \frac{I_{CBO} - (I_{RS}\alpha_1 + I_{RW}\alpha_2)}{1 - (\alpha_1 + \alpha_2)}$$

- ◆  $I_H$  is defined as the current with zero  $I_{CBO}$

$$I_H = \frac{I_{RS}\alpha_1 + I_{RW}\alpha_2}{\alpha_1 + \alpha_2 - 1}$$

- ◆ If  $\alpha_1 + \alpha_2$  is close to 1,  $I_H$  will be large
- ◆ The SCR current at the onset of latch-up,

$$I \geq I_H = (V_{DD} - V_H) / R_T$$

# Latch-Up Condition

- ◆ Both transistors are at the saturation boundary

$$V_H = 2V_{BE} \text{ with } V_{BE1} = V_{BE2} = V_{BE}$$


$$I_{RW} = V_{BE} / R_{well} \text{ and } I_{RS} = V_{RE} / R_{sub}$$

- ◆ Therefore, the condition for latch-up is


$$\alpha_1 + \alpha_2 \geq 1 + \left( \frac{\frac{R_T}{R_{well}} \alpha_1 + \frac{R_T}{R_{sub}} \alpha_2}{\frac{V_{DD}}{V_{BE}} - 2} \right)$$

- ◆ Above inequality shows that small  $R_{sub}$  and  $R_{well}$  help avoiding the latch-up

# Simulation of Latch-Up (Schematic)

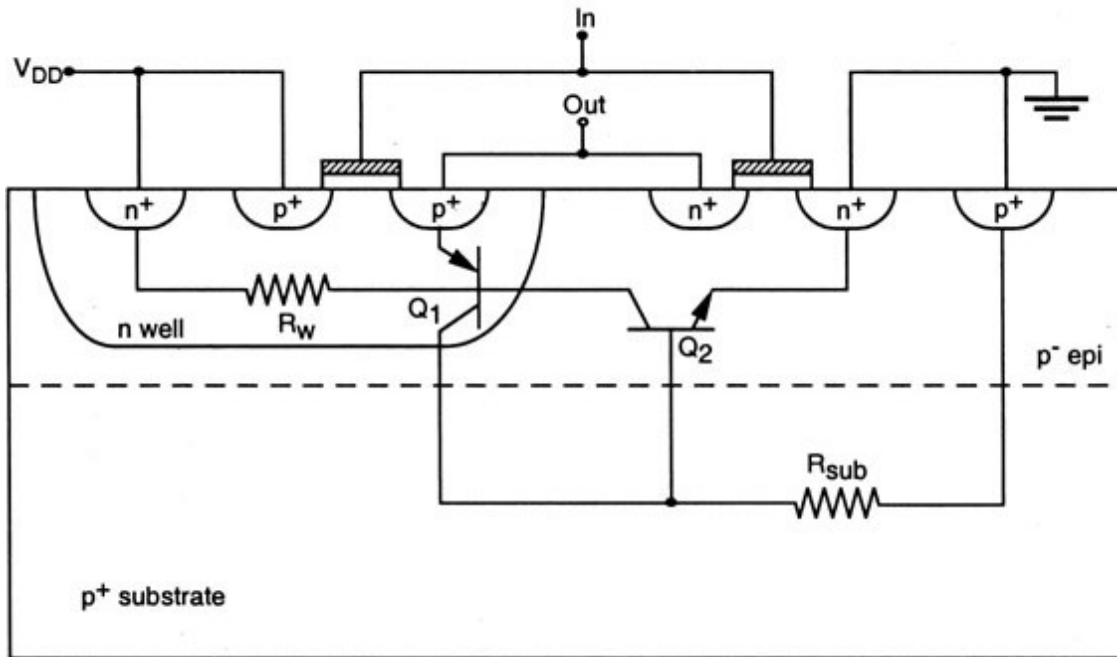


(a) CMOS inverter with parasitic BJTs

 


(b) Schematic of the simulation

# Simulation of Latch-Up (Waveform)

 

(a) Voltage

(b) Current

 



# Latch-Up Guidelines(1)

- ◆ Gold doping of the substrate
  - Reduce gains of BJTs by lowering the minority carrier lifetime
- ◆ Schottky source/drain contacts
  - Reduce the minority carrier injection efficiency of BJT emitters
- ◆ Guardband rings: capture the injected minority carriers
  - P+ guard rings connected to ground around nMOS
  - N+ guard rings connected to  $V_{DD}$  around pMOS
- ◆ Place substrate and well contacts as close as possible to the source of MOS transistors
  - Reduce  $R_w$  and  $R_{sub}$
- ◆ Minimum area p-wells (in case of twin-tub technology or n-type substrate)

# Latch-Up Guidelines(2)

- ◆ Source diffusion regions of pMOS transistors should be placed.
    - Ensure the same potential between  $V_{DD}$  and p-wells
  - ◆ In some n-well I/O circuits, wells can be eliminated by using only nMOS
  - ◆ Avoid the forward biasing of source/drain junctions
    - Prevents injecting high current
  - ◆ Lightly doped epitaxial layer on top of a heavily doped substrate
    - Shunts lateral currents from the vertical transistor
  - ◆ Place nMOS close to  $V_{SS}$  and pMOS near  $V_{DD}$
  - ◆ Maintain sufficient space between pMOS and nMOS
-

# I/O Cell Layout With Latch-Up Guidelines

