 


CMOS Digital Integrated Circuits



Chapter 10 Semiconductor Memories

S.M. Kang, Y. Leblebici, and
C. Kim


10.1 Introduction

◆ Design issue

- Area efficiency → cost per bit
- Access time → speed
- Power consumption → low-power

10.1 Introduction


◆ Semiconductor memory types

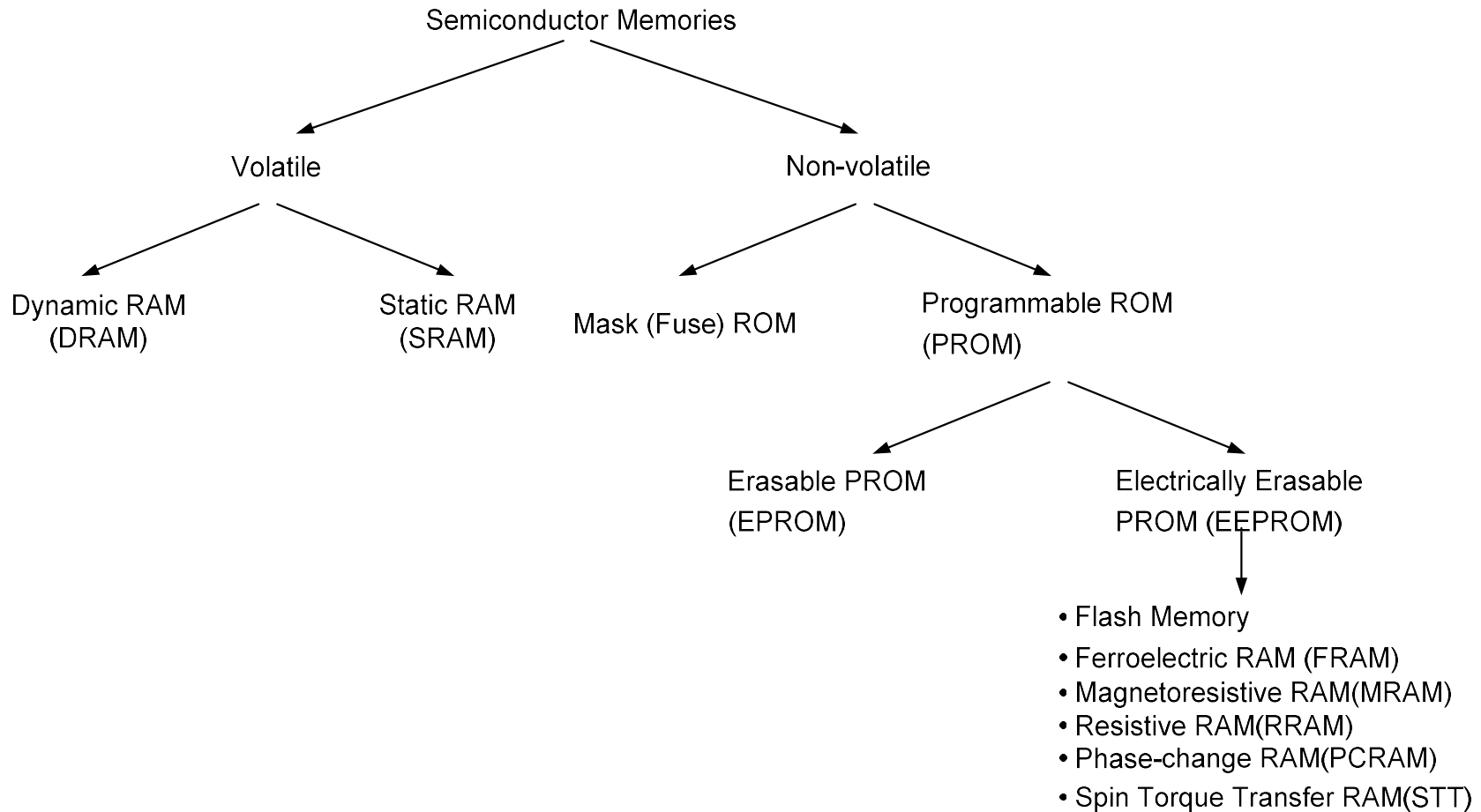


Characteristic Summary of Memory Devices

	Memory type					
	DRAM	SRAM	UV EPROM	EEPROM	Flash	FRAM
Data volatility	Yes	Yes	No	No	No	No
Data refresh operation	Required	No	No	No	No	No
Cell structure	1T-1C	6T	1T	2T	1T	1T-1C
Cell size(F ²) (F: min. feature size)	6~8	80~100			4~5(NAND) 9~10(NOR)	
Cell density	High	Low	High	Low	High	High
Power consumption	High	High/low	Low	Low	Low	High
Read speed (latency)	~50 ns	~10/70 ns	~50 ns	~50 ns	~50 ns	~100 ns
Write speed	~40 ns	~5/40 ns	~10 μs	~5 ms	~(10 μs-1 ms)	~100 ns
Endurance	High	High	High	Low	High	High
Cost	Low	High	Low	High	Low	Low
In-system writability	Yes	Yes	No	Yes	Yes	Yes
Power supply	Single	Single	Single	Multiple	Single	Single
Application example	Main memory	Cache/PDAs	Game machines	ID card	Memory card solid-state disk	Smart card, digital camera

Equivalent Circuits of Memory Cells(1)

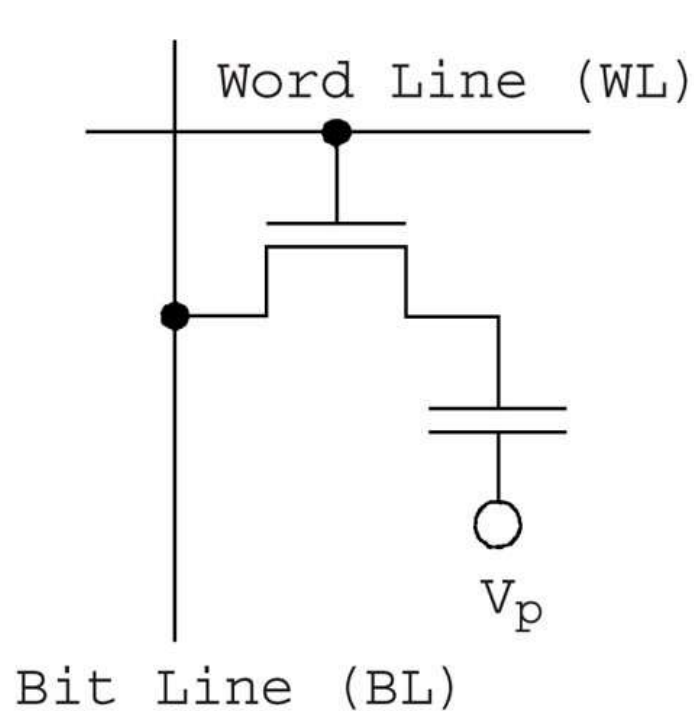


(a) DRAM

 


(b) SRAM


Equivalent Circuits of Memory Cells(2)

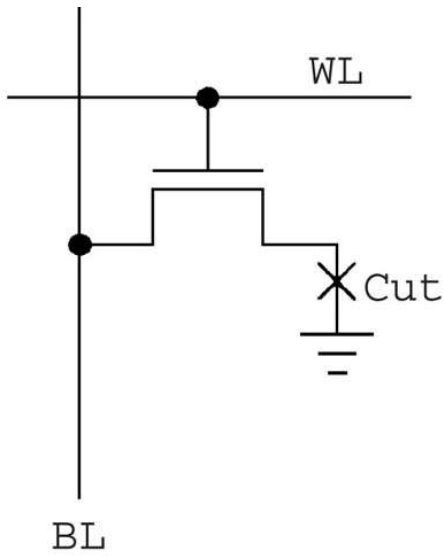

(c) Mask ROM

 


(d) EPROM

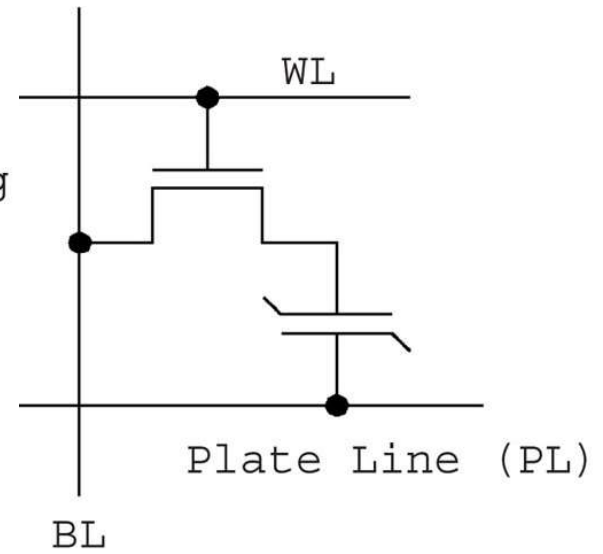

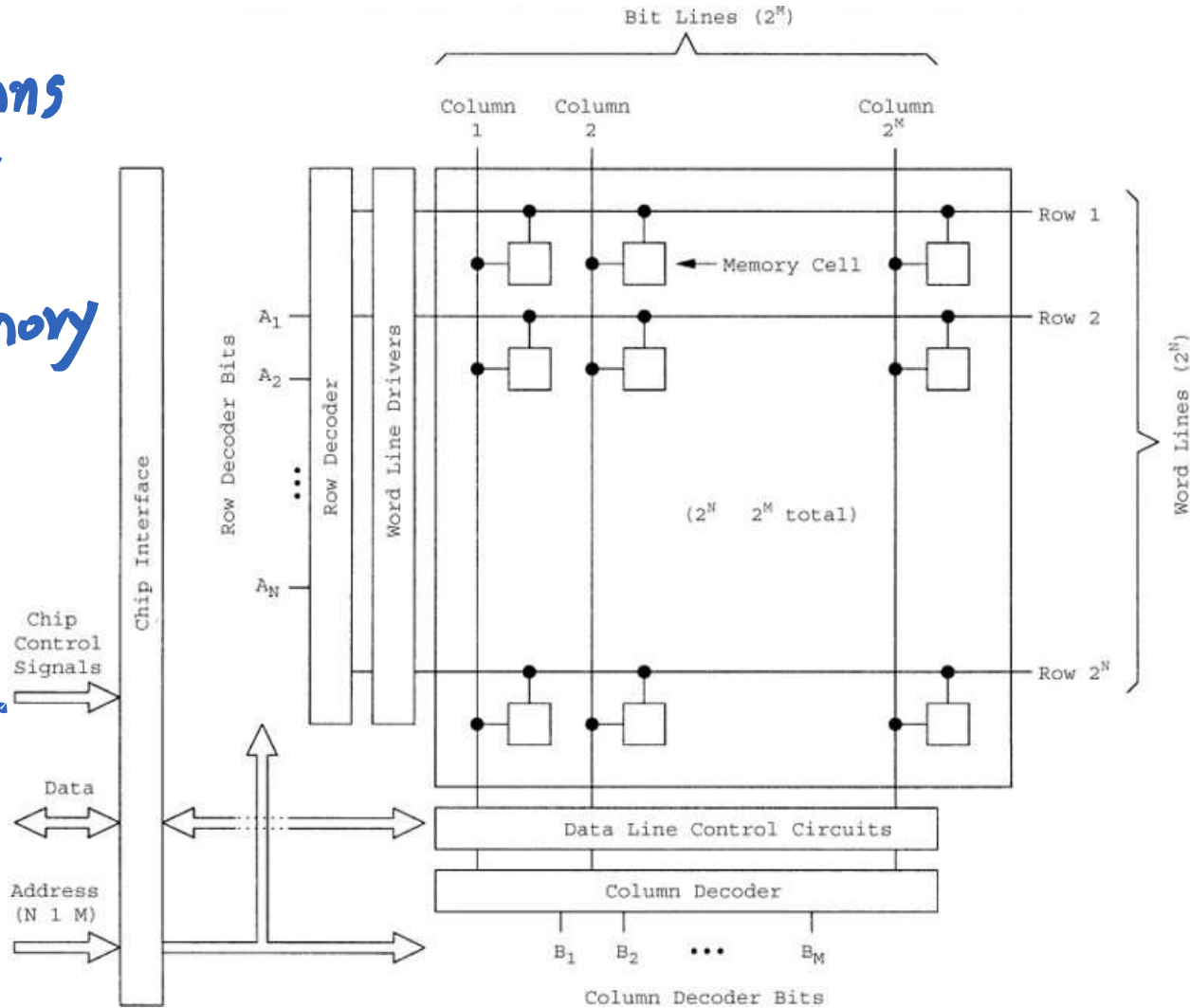
(e) FRAM

Conceptual RAM Array Organization

M columns
 N rows
 1 Kb memory
 = 1024b
 = 2^{10}
 $M = 5 \quad 6 \quad 4$
 $N = 5 \quad 4 \quad 6$




10.2 Dynamic Random Access Memory

 

Typical configuration of DRAM chip
 (1.6Gbps 4Gb 30nm LPDDR3 w/ 8 banks)
 chip size ↔ performance

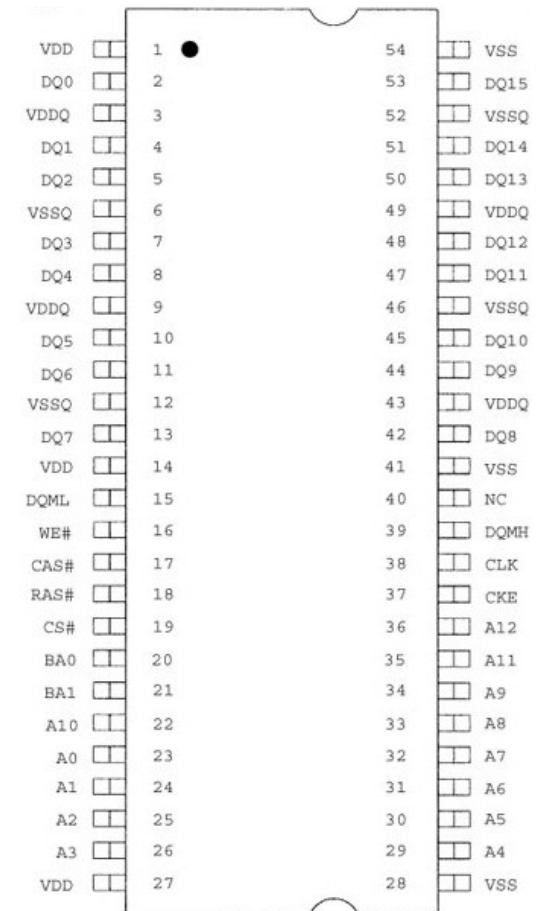➔ The number of cells per word and bit lines




Pin assignment

Definition and Function of DRAM Pins


Pin name	Definition	Function
CLK	Clock input	Reference system clock for the operation and data communication
CKE	Clock Enable	Control the clock input
\overline{CS}	Chip Select	Activate the DRAM device from a memory cluster
\overline{RAS}	Row Address Strobe	Latch row address and start the cell core operation
\overline{CAS}	Column Address Strobe	Latch column address and start the data communication operation
\overline{WE}	Write Enable	Activate the write operation
A0 to A14	Address input	Select a data bit
DQ0 to DQ15	Data input and output	Communicate data with external devices
DQMU/DQML	DQ Mask for Upper (Lower) Byte	Mask byte data from the operations
V_{DD}/V_{SS}	Power pins	Power for DRAM core and peripheral circuits
V_{DDQ}/V_{SSQ}	Power pins	Power for DQ circuits
NC	No connection	

Historical Evolution of DRAM Cell(1)

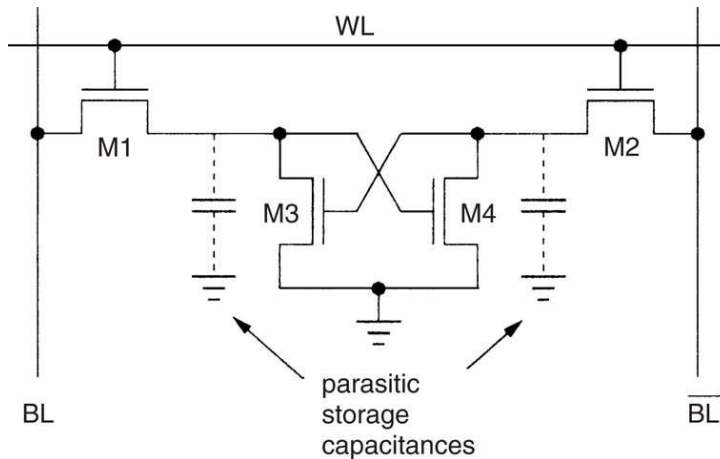

◆ Four-transistor DRAM cell

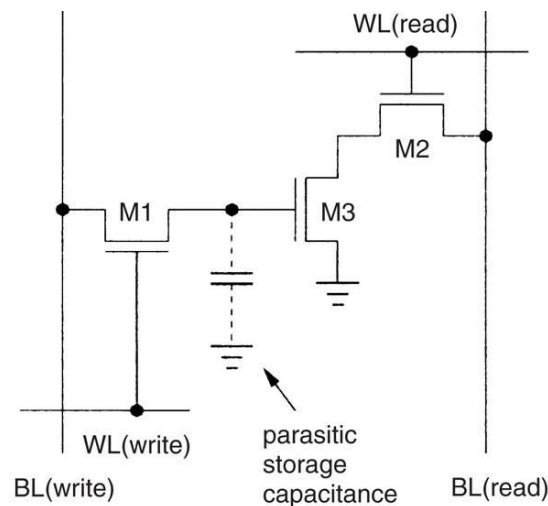
- Operations are similar to SRAM cell
- Two storage nodes
- Periodically refresh is required
- Non-destructive read operation



◆ Three-transistor DRAM cell


- One storage node
- One Tr. each for "read" and "write"
- Non-destructive read operation
- Two bit lines and two word lines
(additional contacts → increase area)

Historical Evolution of DRAM Cell(2)

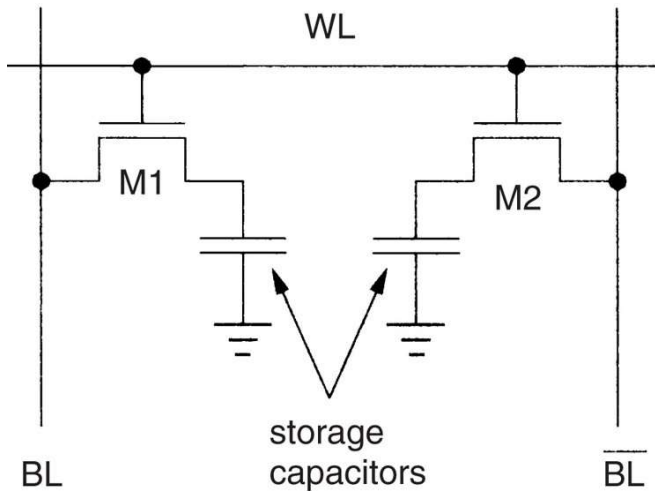

◆ Two-transistor DRAM cell

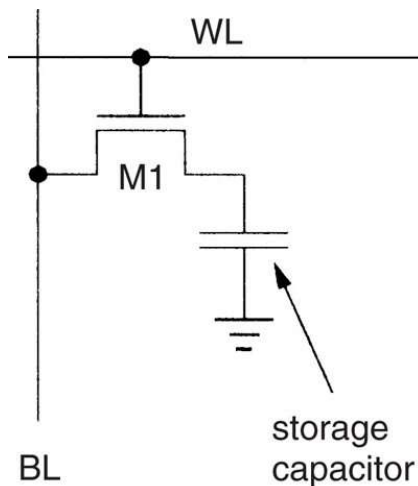- Explicit storage cap.
- Destructive read operation (share with the bit line)
- Two bit lines and one word line




◆ One-transistor DRAM cell


- Industry-standard DRAM cell
- Destructive read operation (share with the bit line)
- Charge restoring operation required

DRAM Cell Types

 - ◆ With only one transistor and one capacitor
 - Smallest area of the all DRAM cells.
 - Destructive “read” operation
 - ➔ major effort : large cap. cell with minimized area




(a) DRAM cell with a stacked cap.

 

 
(b) DRAM cell with a trench cap.

Operation of Three-Transistor DRAM Cell

◆ Typical 3-T DRAM cell and voltage waveforms



Precharge Events

 

◆ Base on two-phase non-overlapping clock scheme

Φ_1 : precharge phase

Φ_2 : active phase

Precharge signal PC goes up




MP1 and MP2 are activated



C_2 and C_3 are charged up
(Steady-state values)

Write "1" and Read "1" Operations

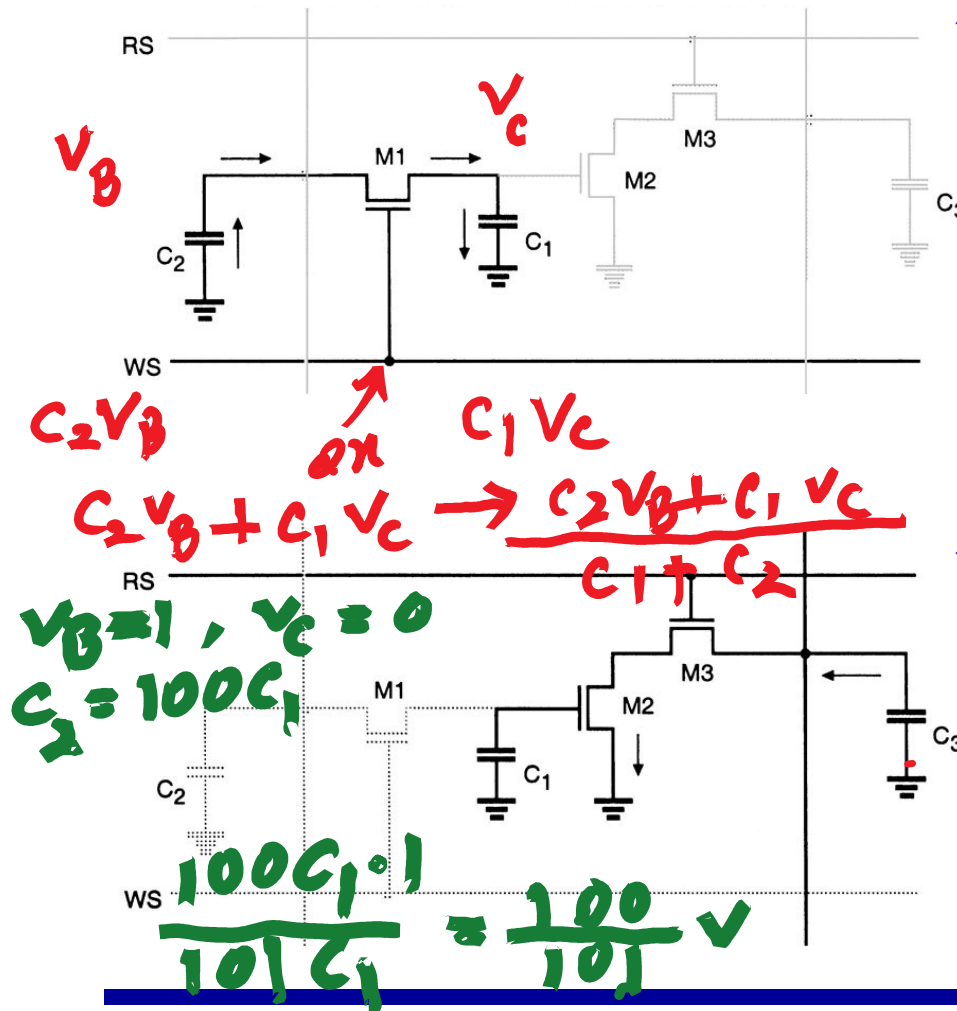

Write "1"


- DATA is low \rightarrow D_{in} remains high
- M1 turns on (WS is high) \rightarrow C_2 shared with C_1
- C_1 charge up to high (M2 is conducting)

Read "1"

- RS is high \rightarrow M3 turns on
- M2 and M3 create conducting path from C_3 to GND
- C_3 discharges
- Non-destructive read operation


Read
 $\frac{1}{2} V_{DD} = 0.5$
 $\frac{0.5 \times 100 C_1 + 0.990 C_1}{101 C_1}$
 $= 0.5 \frac{100}{101}$
 $+ \frac{0.99}{101}$
 $= 0.505$
 $\Delta = 5 mV$

Write "0" and Read "0" Operations

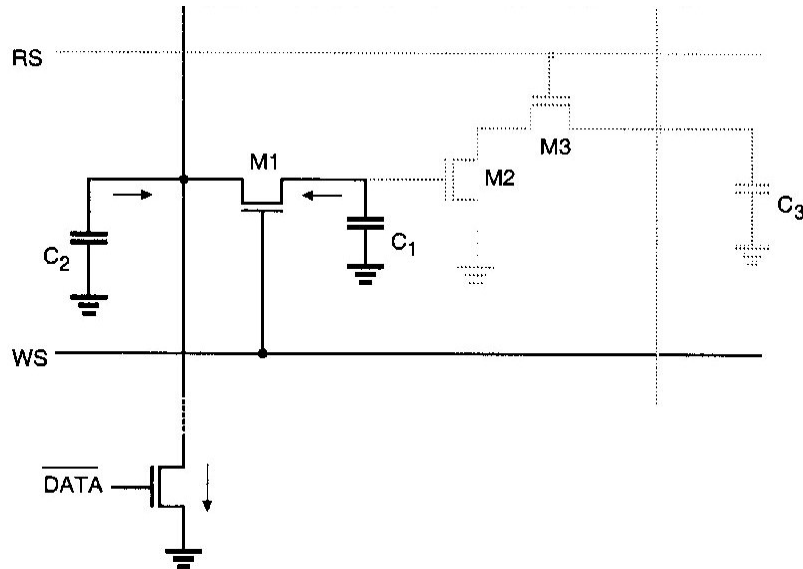

◆ Write "0"

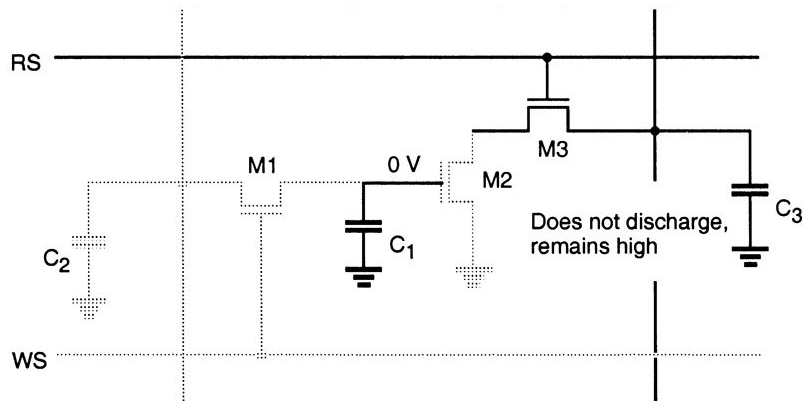- $\overline{\text{DATA}}$ is high \rightarrow D_{in} goes low
- M1 turns on (WS is high)
- C_1 discharges (M2 turns off)




◆ Read "0"

- RS is high \rightarrow M3 turns on
- No conducting path
- C_3 does not discharge


Operation of One-Transistor DRAM Cell

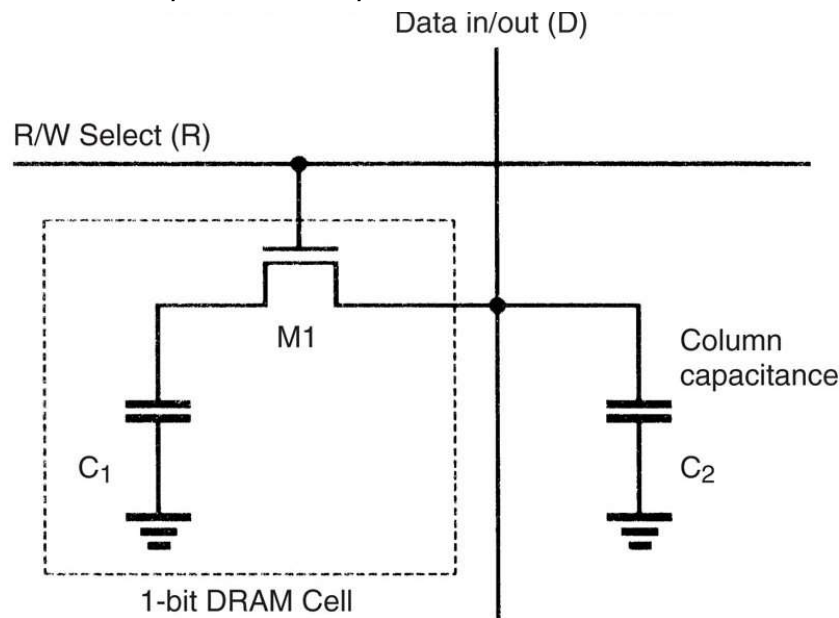- ◆ One explicit storage cap. and one access transistor
 - The most widely used storage structure
 - Bit lines are folded and precharged to half- V_{DD}
 - ➔ improve noise-immunity & reduce power consumption
 - Operation : "read", "write", "refresh"




1-T DRAM Structure

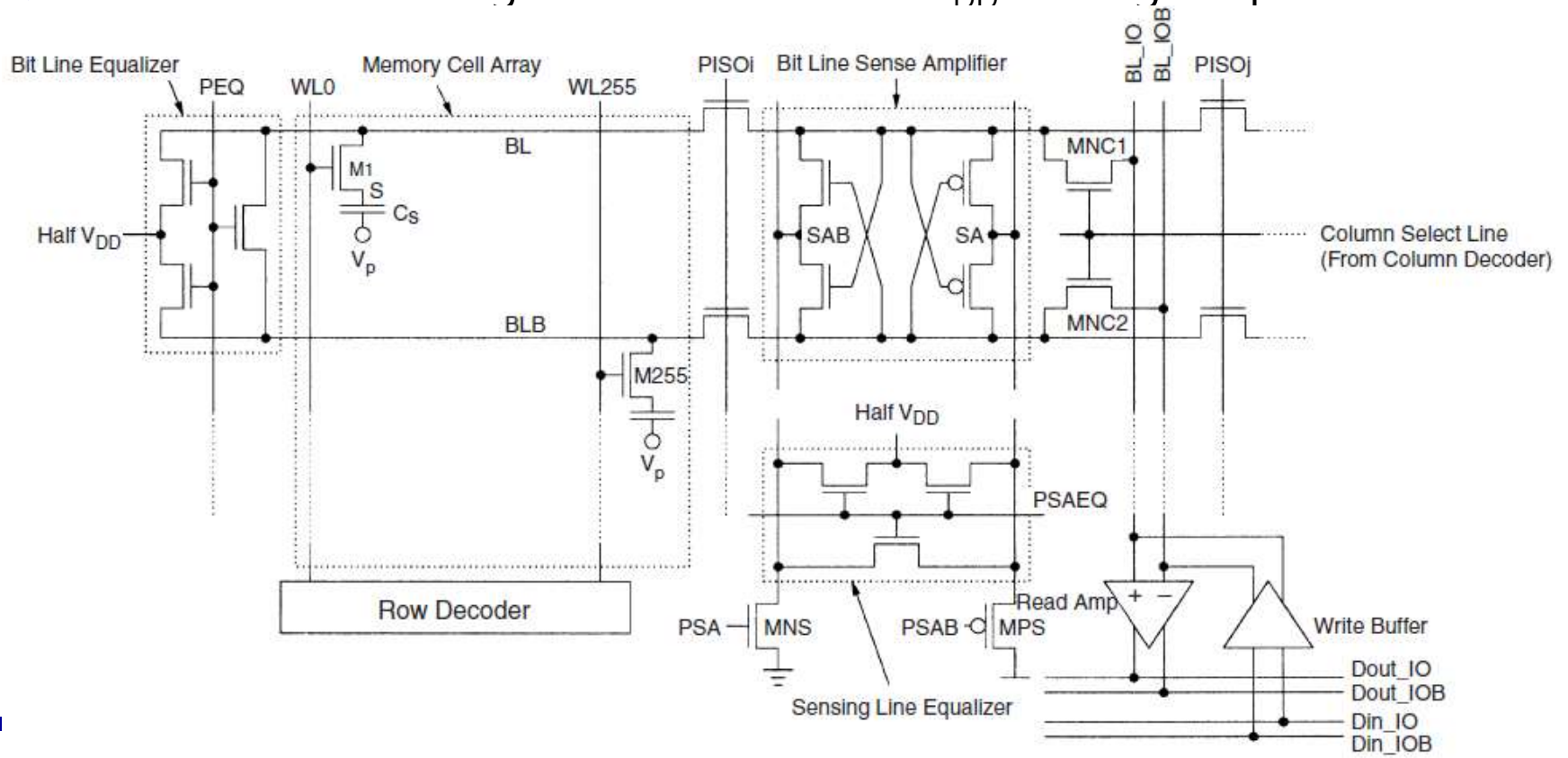- ◆ DRAM cell array with control circuits
- ◆ Latch amplifier to sense the small signal difference
- ◆ Bit lines and sensing nodes set to half- V_{DD} through equalizer



DRAM Read Operation

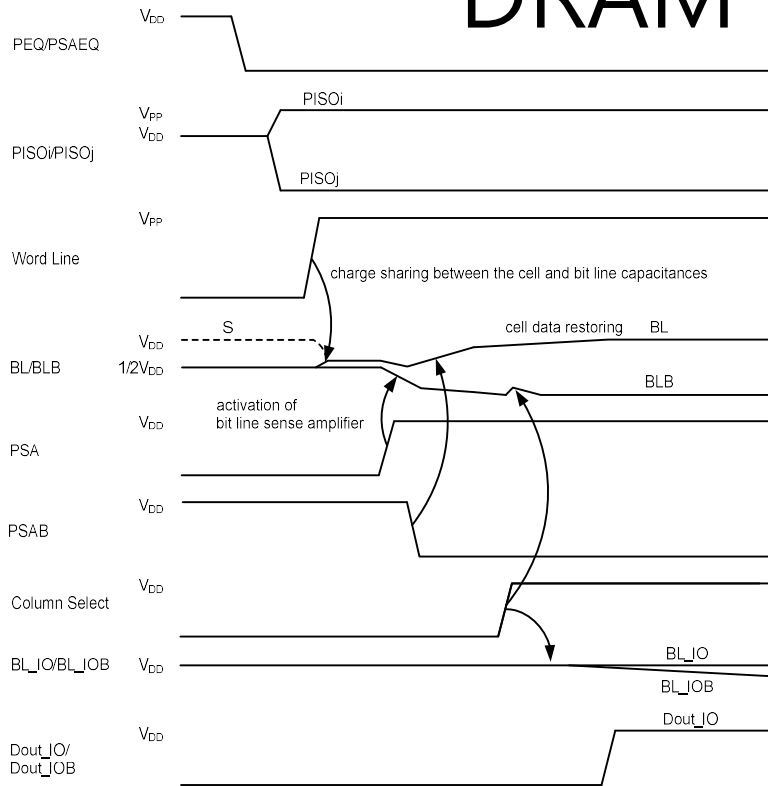

◆ C_S shared with C_{BL} (=initially half V_{DD})

$$\Delta V = \frac{C_S}{C_{BL} + C_S} \frac{V_{DD}}{2}$$

◆ $C_S : V_{DD} \rightarrow \frac{1}{2}V_{DD} + \Delta V$ (destructive)

◆ BL and BLB voltage difference amplified

◆ BLB \rightarrow GND, BL \rightarrow V_{DD}


storage node is recovered (restoring)

◆ Column switch is enabled by column decoder (BL \rightarrow BL_IO, BLB \rightarrow BL_IOB)


◆ Read Amp. amplifies the voltage difference

❖ $V_{PP} = V_{DD} + V_{th}$ for full charge restoration

 ❖ PSA and PSAB are sequentially activated to reduce charge injection and short circuit current




DRAM Write Operation

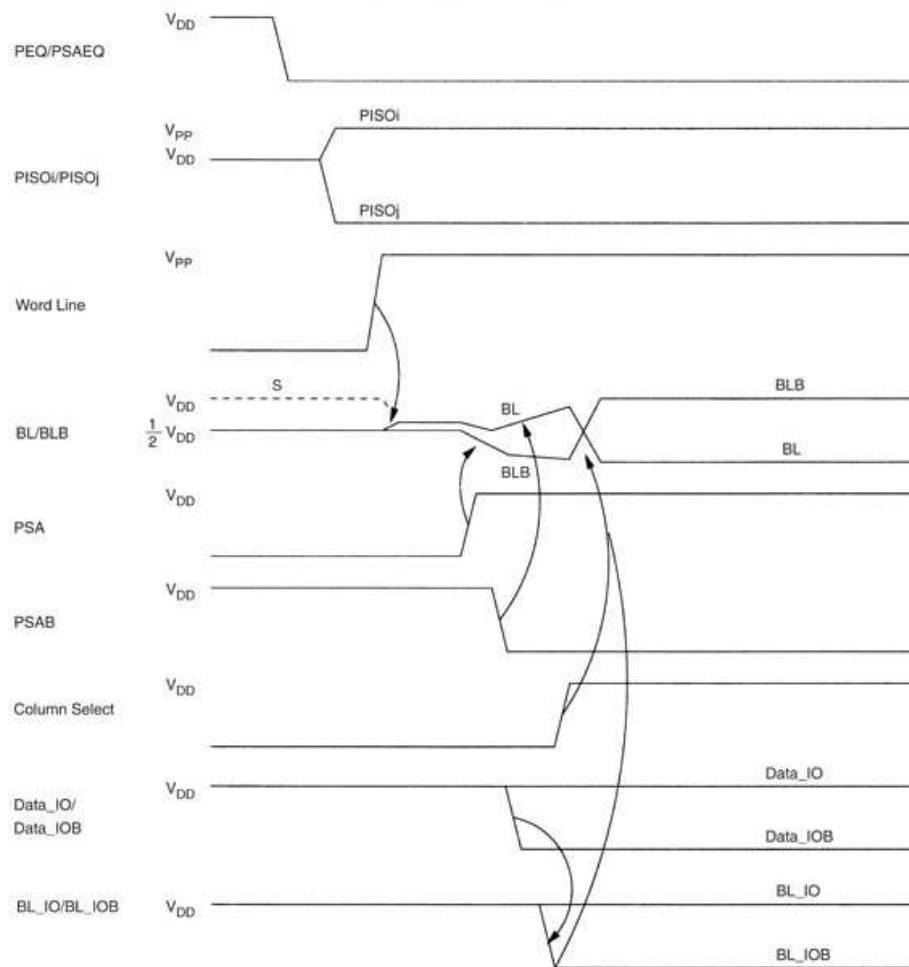


- ◆ Identical sequence to normal read operation
- ◆ Strong write driver (buffer) to drive BL_IO, BL_IOB line cap.
 - ➔ faster than read operation
- ◆ Column switch is selected by column decoder
- ◆ Bit line and cell data changed

Asynchronous DRAM Mode(1)

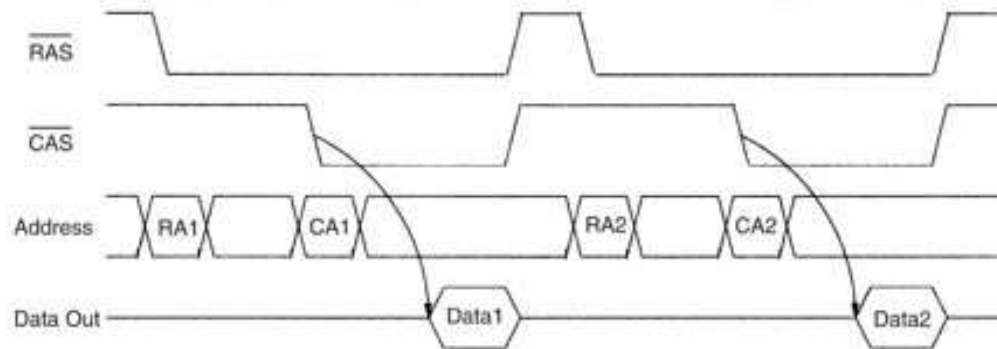


- ◆ single bit access (different row and column addresses)
- ◆ Operation uses address multiplexing scheme ($\overline{\text{RAS}}$ and $\overline{\text{CAS}}$)
 - ➔ reduce the chip package size
- ◆ $\overline{\text{RAS}}$ pull down ➔ operation start
- ◆ Falling edge of $\overline{\text{CAS}}$ ➔ data (from same word line) selected
- ◆ $\overline{\text{RAS}}$, $\overline{\text{CAS}}$ precharge before new data access
- ◆ t_{RAC} : memory read latency, time to read data from falling of $\overline{\text{RAS}}$
- ◆ Length of word line is determined by **refresh** cycle constraint

Asynchronous DRAM Mode(2)

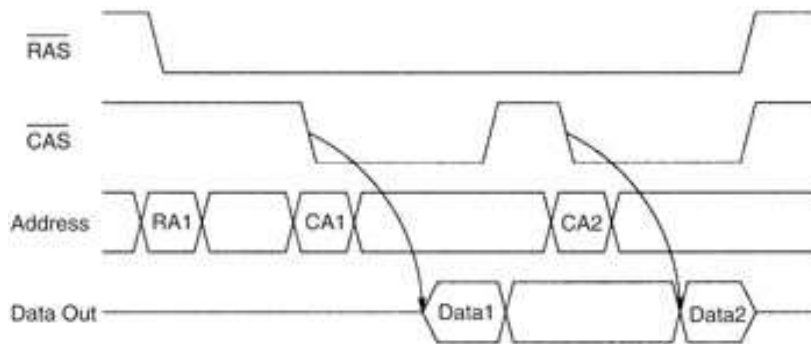

◆ page access

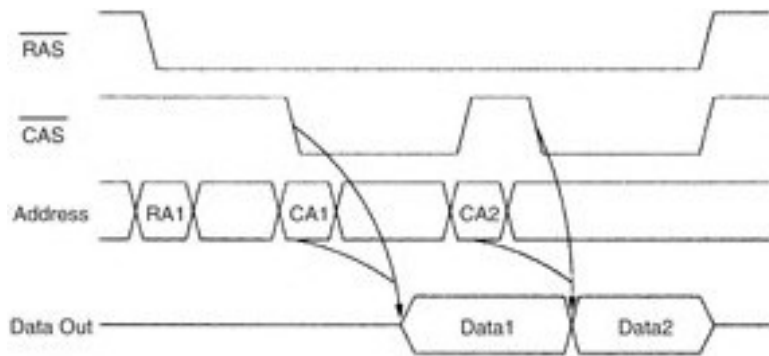
- keep the row address
- read cell of same row address
- faster read operation



◆ extended data-out(EDO)


- new column address is captured at rising edge of CAS
- Read data maintain during precharge time
- Fastest read operation

Synchronous DRAM Mode

 

◆ Four bit burst read

 
- Read frequency improve with use of the system clock
- At falling edge, control signal and addresses become active
- Pipelined based on clock to improve throughput
- Use both of edges to improve bandwidth (Dual Data Rate)



◆ Serial mode read

- Use small signal swing and clock recovery scheme to maximize the frequency
- Send control input as packet
- Send out data in a serial form

Leakage Currents in DRAM Cells

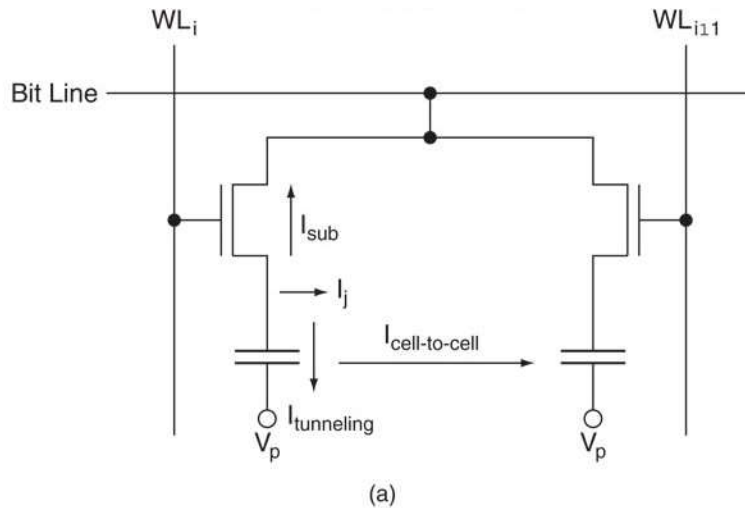

- ◆ Contact and bit line share by two adjacent cells


$$I_{leakage} = I_{sub} + I_{tunneling} + I_j + I_{cell-to-cell}$$

I_{sub} : leakage through cell transistor

$I_{tunneling}$: tunneling through thin dielectric


I_j : junction leakage at storage node

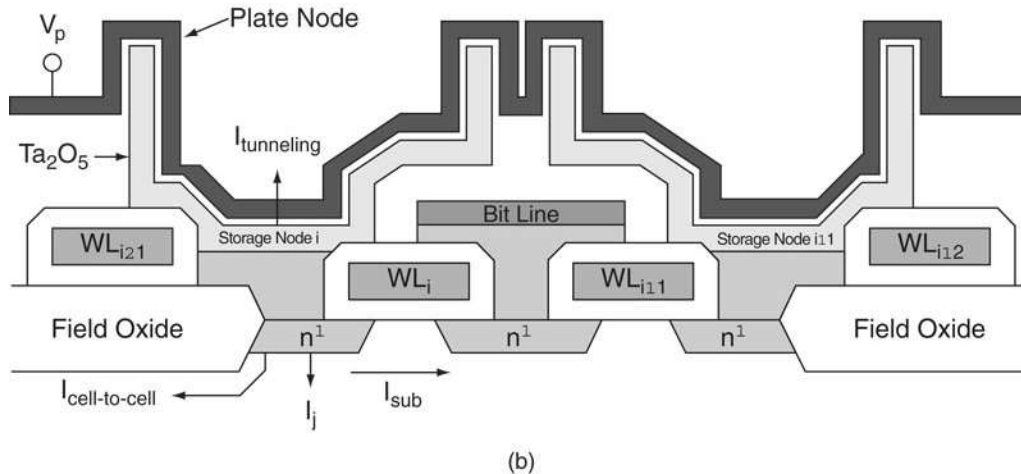$I_{cell-to-cell}$: leakage across the field oxide




- ◆ I_{sub} depend on V_{th}
increase V_{SB} to reduce I_{sub}
- ◆ $I_{tunneling}$ is a serious issue
because thickness of dielectric is reduced to increase cell cap.


Refresh Operation

 

ROR refresh mode

 

CBR refresh mode

 

Self refresh mode

◆ ROR(RAS-only refresh) refresh

- Read and restore operation
- Does not send data out
- similar to normal read operation

◆ CBR(CAS-before-RAS) refresh


- row address generated by on-chip counter
- performed periodically

◆ Self refresh


- period set according to operating condition
- row address and control signal generated by internal circuit

DRAM Input/Output Circuits(1)

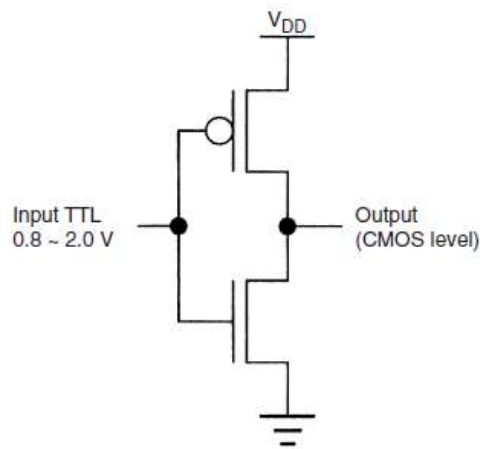
- ◆ Logic level of system board and memory chip are different
➔ required to convert logic levels ➔ input/output buffers
- ◆ Input buffers



inverter type

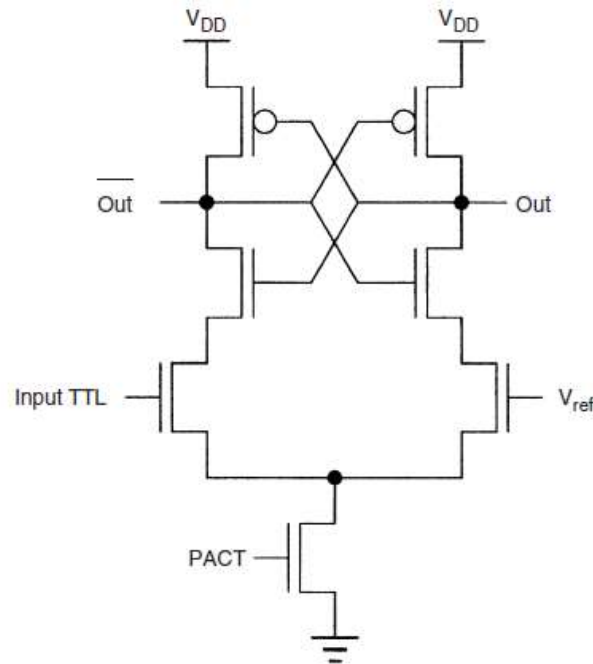

latch type

 

differential amp type


Characteristic Comparison of Input Buffers

	Buffer type		
	Inverter	Latch	Differential
Logic threshold determination (V_{IH} and V_{IL})	By W_P/W_N ratio	By V_{ref}	By V_{ref}
Speed	Slow	Fastest	Fast
Standby current	Small	Smallest	Large
Sensitivity to V_{DD} and temperature	Large	Small	Small
Noise immunity	Bad	Good	Good
Constraint	None	Precharge and activation signals needed	None


DRAM Input/Output Circuits(2)

◆ Memory output buffers

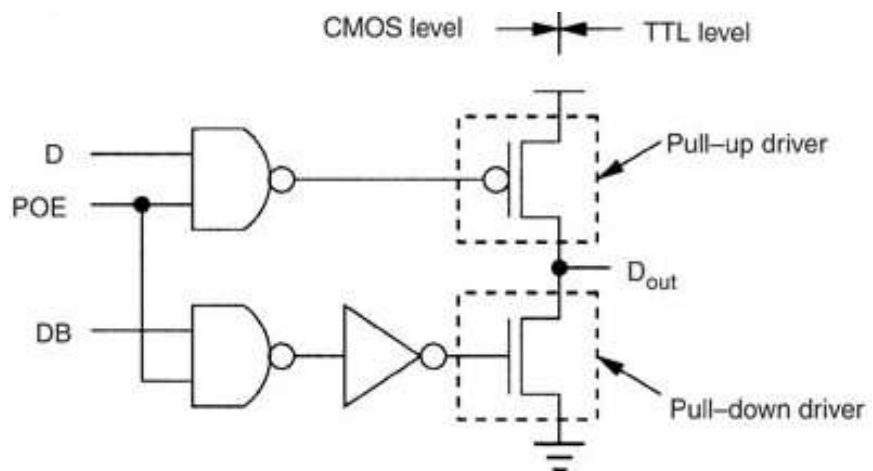- Need to drive large cap.
- Keep a high-impedance when chip is not selected
 - ➔ to prevent interference of output




PMOS pull-up structure

 


NMOS pull-up structure

DRAM Decoder(1)

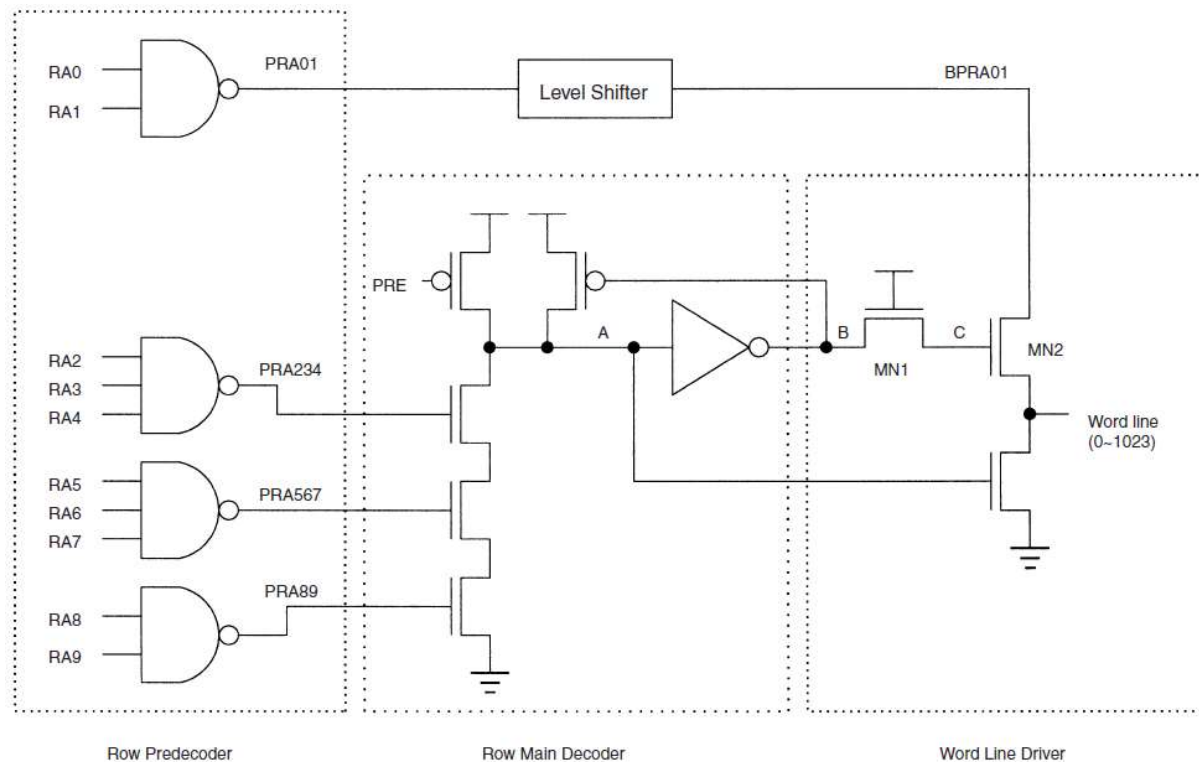- ◆ To select cell from 2^{2M} memory array, M address bits are needed
- ◆ Practically, M transistors in series is impossible
- ➔ decoding scheme is composed of pre and main decoder



DRAM Decoder(2)

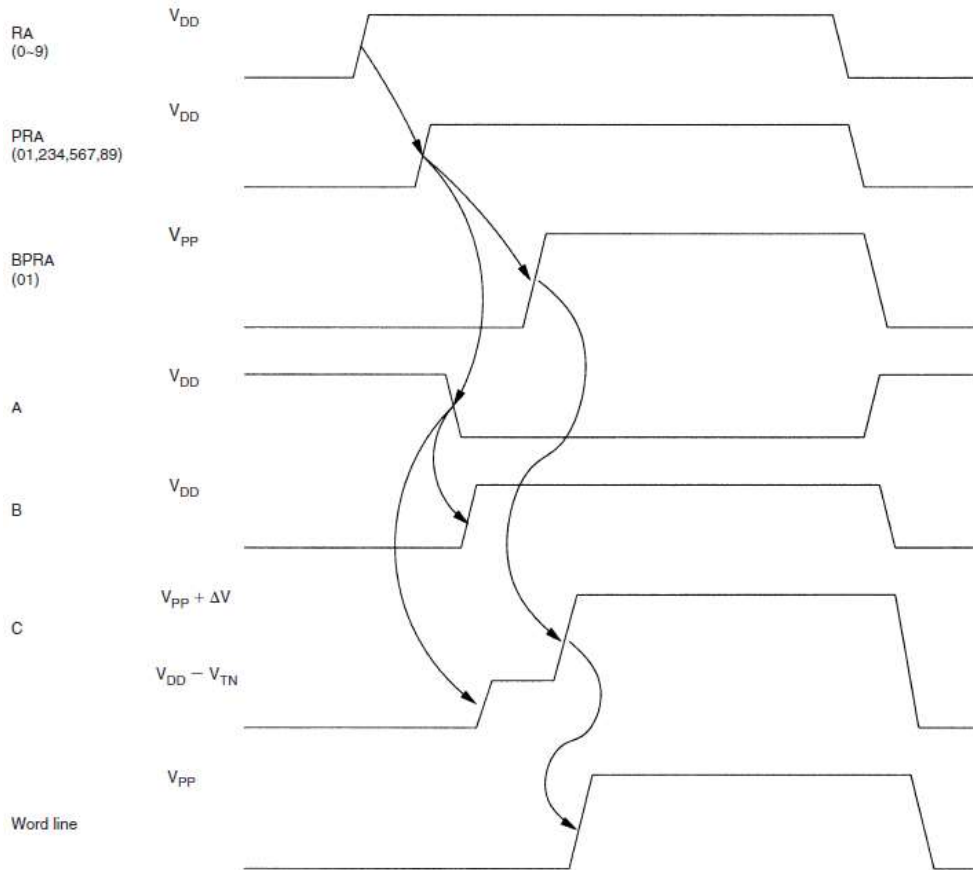


- ◆ V_{PP} for full restoration
- ◆ Output of predecoder boosted by level shifter
- ◆ Self-bootstrapped driver for transferring to highly cap. without signal degradation

- ◆ Voltage of C when main decoder is selected

$$V_C = V_{PP} + \Delta V = V_{DD} - V_{TN} + \frac{C_{MN2}}{C_{MN2} + C_{Cparasitic}} V_{PP}$$


Voltage Sense Amplifiers

 ◆ To detect signal difference on data lines




◆ Current-mirror differential

 - Popular and good common-mode rejection ratio
- Large area and large power consumption



◆ Full CMOS latch type

 - High speed, small area and low power
- Precharge signal required
- operation cannot be reversed




◆ Semilatch type

- Between current-mirror type and full CMOS latch type



Internal Voltage Regulator Circuit

 - ◆ Lowering voltage to reduce power consumption
- ◆ V_{INT} (internal voltage generator)
 - ➔ reduce operating current




Half V_{DD} Voltage Generator

 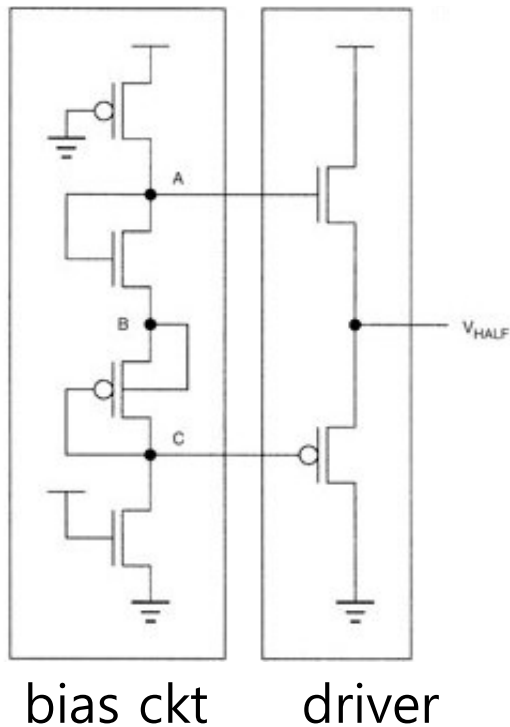- ◆ Folded bit line structure with half V_{DD} sensing scheme
 - Improve noise immunity and low power consumption
 - Reduce electric field across thin dielectric




Negative Substrate Bias Voltage Generator(1)

 - ◆ Subthreshold current is major source of charge decay
 - Negative voltage substrate → increase threshold voltage
 - reduce load cap. of bit line




$$\frac{\Delta V_T}{\Delta V_{SB}} \propto \sqrt{V_{SB}}$$

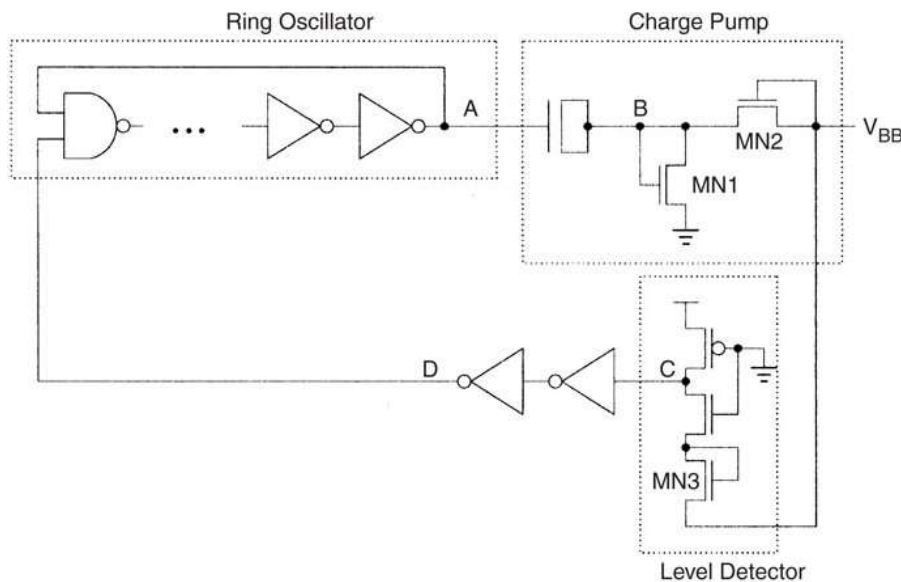
Negative Substrate Bias Voltage Generator(2)



Circuit diagram

 


Timing diagram

 


Simulated waveforms

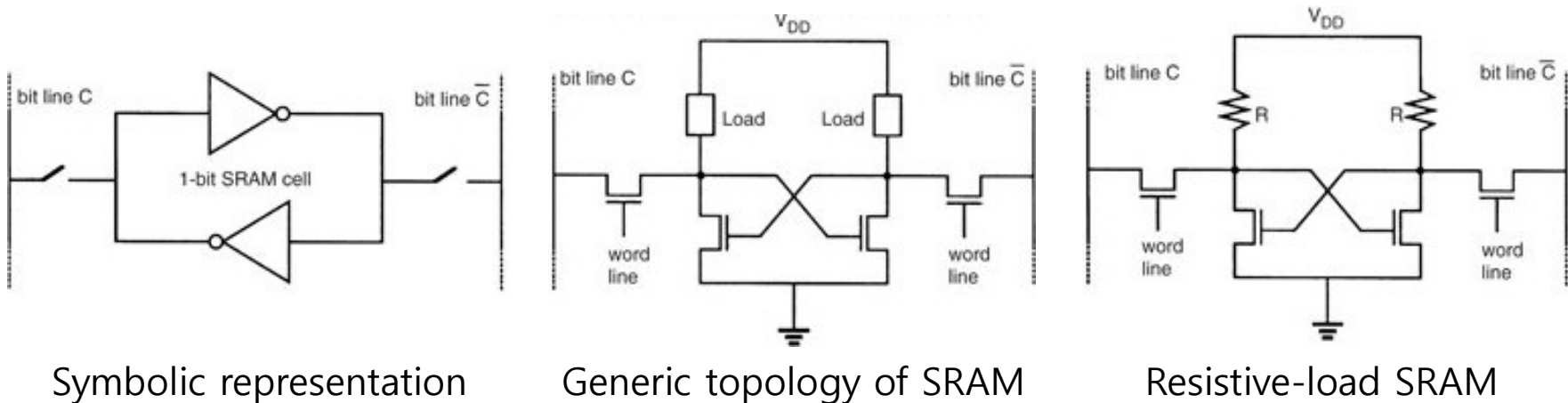10.3 Static Random Access Memory(1)

- ◆ Stored data can be retained indefinitely
- ◆ Simple latch with two stable operating points
- ◆ Two access switches to connect 1-bit SRAM
- ◆ Poly resistor load inverter structure is more compact cell size (resistor stack on top of cell)
- ◆ Load R trade off : low power \longleftrightarrow wider noise margin, high speed




10.3 Static Random Access Memory(2)

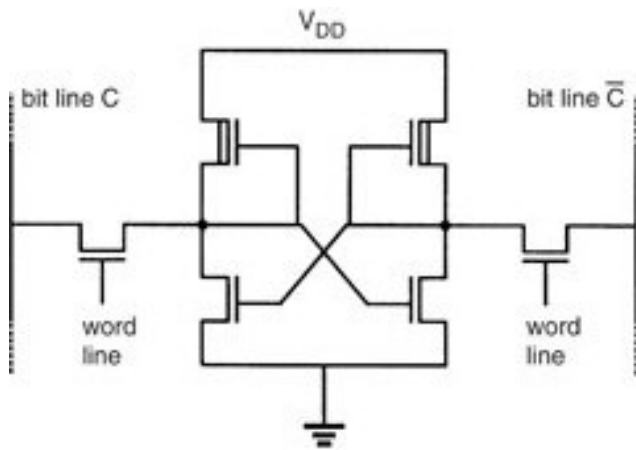

◆ Depletion-load NMOS SRAM

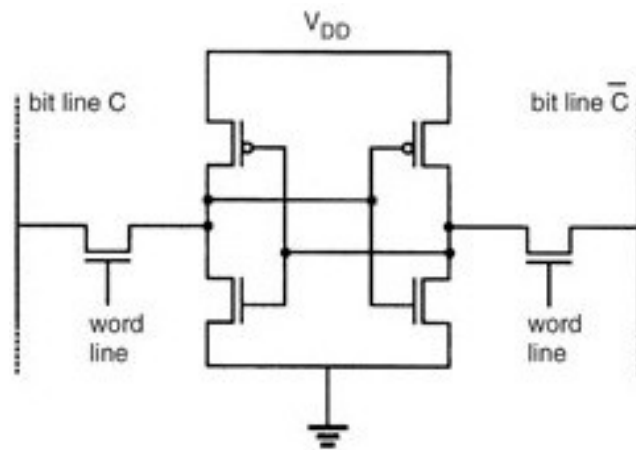- Six-transistor
(one poly and one metal layer)
- Cell size relatively small
- Static characteristics and noise margins better than resistive-load cell
- Static power consumption




◆ Full CMOS SRAM


- Most popular
- Lowest static power
- Superior noise margins and switching speed

Full CMOS SRAM Cell(1)

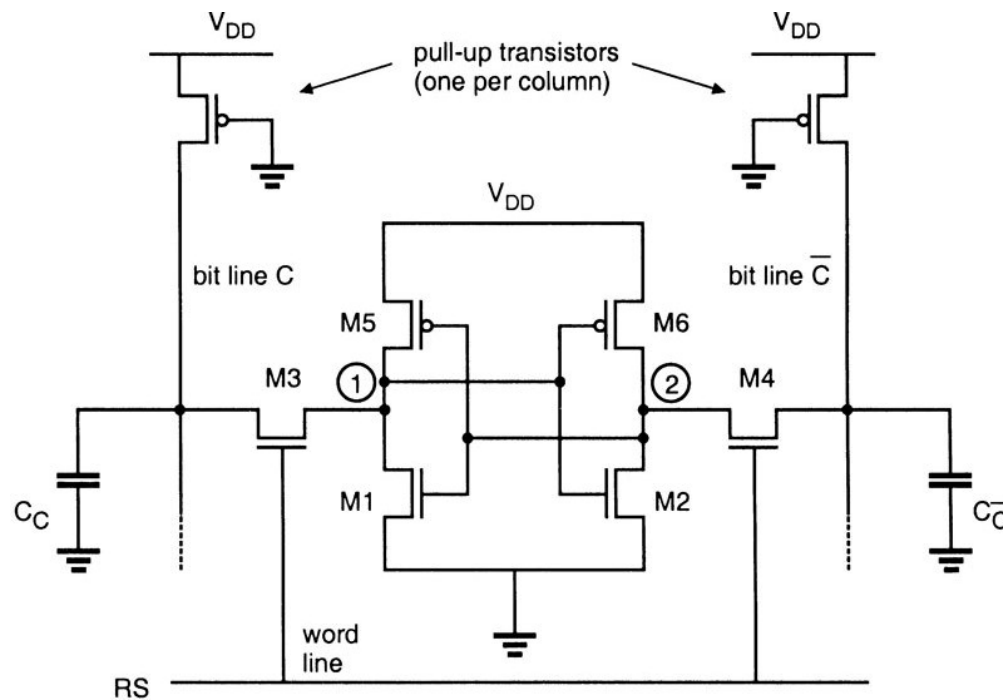
- ◆ Very small static power dissipation (limited by leakage current)
- ◆ High noise immunity (large noise margin)
- ◆ Ability to operate at lower supply
- ◆ Disadvantage : cell area slightly larger, latch-up phenomena



Full CMOS SRAM Cell(2)

 


Layout of CMOS SRAM cell

 

Layout of a 4-bit X 4bit SRAM array, consisting of 16 CMOS SRAM cells

CMOS SRAM Cell Design Strategy(1)

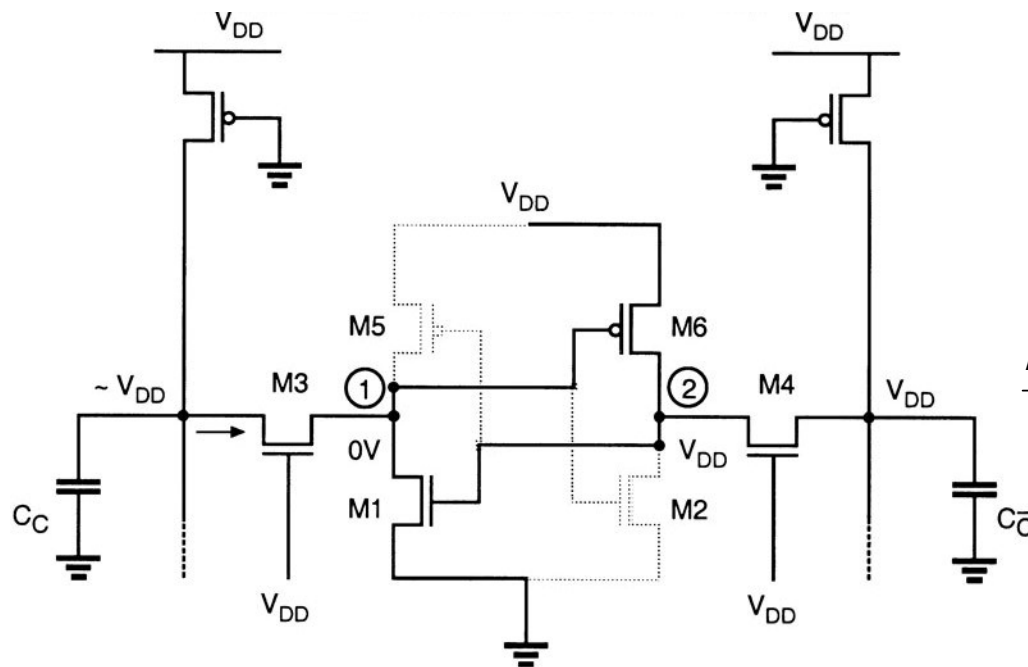- ◆ Two basic requirements which dictate W/L ratio
 - Non-destructive data read operation
 - Modify stored data during write phase




◆ Read Operation (0 stored)

- M3 and M1 conduct some current
- V_{C_C} drops slightly and V_1 increases
- $V_{1,max} \leq V_{T,2}$ not to turn on M2
- M3 in Saturation and M1 in linear

$$\frac{k_{n,3}}{2} (V_{DD} - V_1 - V_{T,n})^2 = \frac{k_{n,1}}{2} (2(V_{DD} - V_{T,n})V_1 - V_1^2)$$

$$\frac{k_{n,3}}{k_{n,1}} = \frac{\left(\frac{W}{L}\right)_3}{\left(\frac{W}{L}\right)_1} < \frac{2(V_{DD} - 1.5V_{T,n})V_{T,n}}{(V_{DD} - 2V_{T,n})^2}$$

CMOS SRAM Cell Design Strategy(2)

 


◆ Write 0 operation (initially, 1 was stored at node 1)

- V_1 must be reduced below $V_{T,2}$ → M2 turns off, V2 rises and V1 falls
- When $V_1 = V_{T,n}$, M3 in linear & M5 in saturation

$$\frac{k_{p,5}}{2} (0 - V_{DD} - V_{T,p})^2 = \frac{k_{n,3}}{2} (2(V_{DD} - V_{T,n})V_{T,n} - V_{T,n}^2)$$


$$\frac{k_{p,5}}{k_{n,3}} < \frac{2(V_{DD} - 1.5V_{T,n})V_{T,n}}{(V_{DD} + V_{T,p})^2} \quad \rightarrow \quad \left(\frac{W}{L}\right)_5 < \frac{\mu_n}{\mu_p} \cdot \frac{2(V_{DD} - 1.5V_{T,n})V_{T,n}}{(V_{DD} + V_{T,p})^2}$$

Memory Structure of SRAM

 

- ◆ Word line selected by row address
- ◆ Cell data kept during read operation
- ◆ Boosted voltage not required
- ◆ Address multiplexing scheme is not used (fast access time than DRAM)
- ◆ Depend on applications
 - ultra low power : load transistor turns off during read operation
 - high speed : remains on

Operation of SRAM

 

◆ Read operation


- Word line enable
- One bit line discharge (voltage change of bit line is very small)
- Sense amp. detect the voltage difference on bit line
- Multi-stage amp. is used to improve read speed

◆ Write operation

- Word line selected by row address
- Write buffer write data into cell
- Write buffer has larger current driving capability than cell
- Write is faster than read

SRAM Read Operation

 
- ◆ TTL level converts into CMOS level signal
- ◆ Internal voltage regulator to reduce power dissipation to improve reliability



Leakage Currents in SRAM Cells

- ◆ Major portion of standby current
- ◆ Standby power is key parameter for low power design
- ◆ High threshold

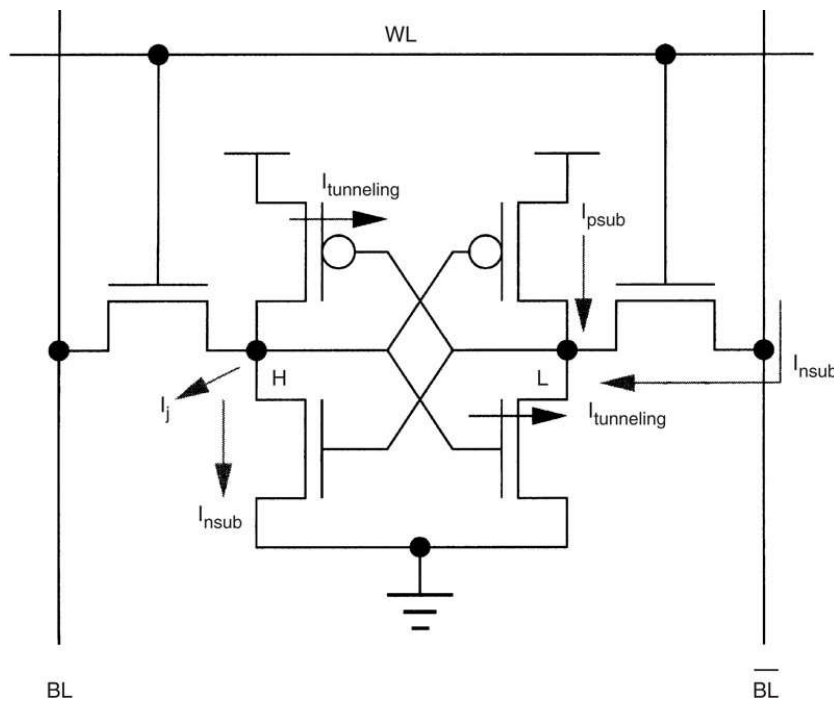reduction of leakage \longleftrightarrow degradation of performance



I_j : junction current

data "1" to substrate


I_{sub} and I_{psub} : subthreshold leakage

turn off NMOS and PMOS

$I_{\text{tunneling}}$: tunneling current

cross thin gate oxide

SRAM Read/Write Circuits

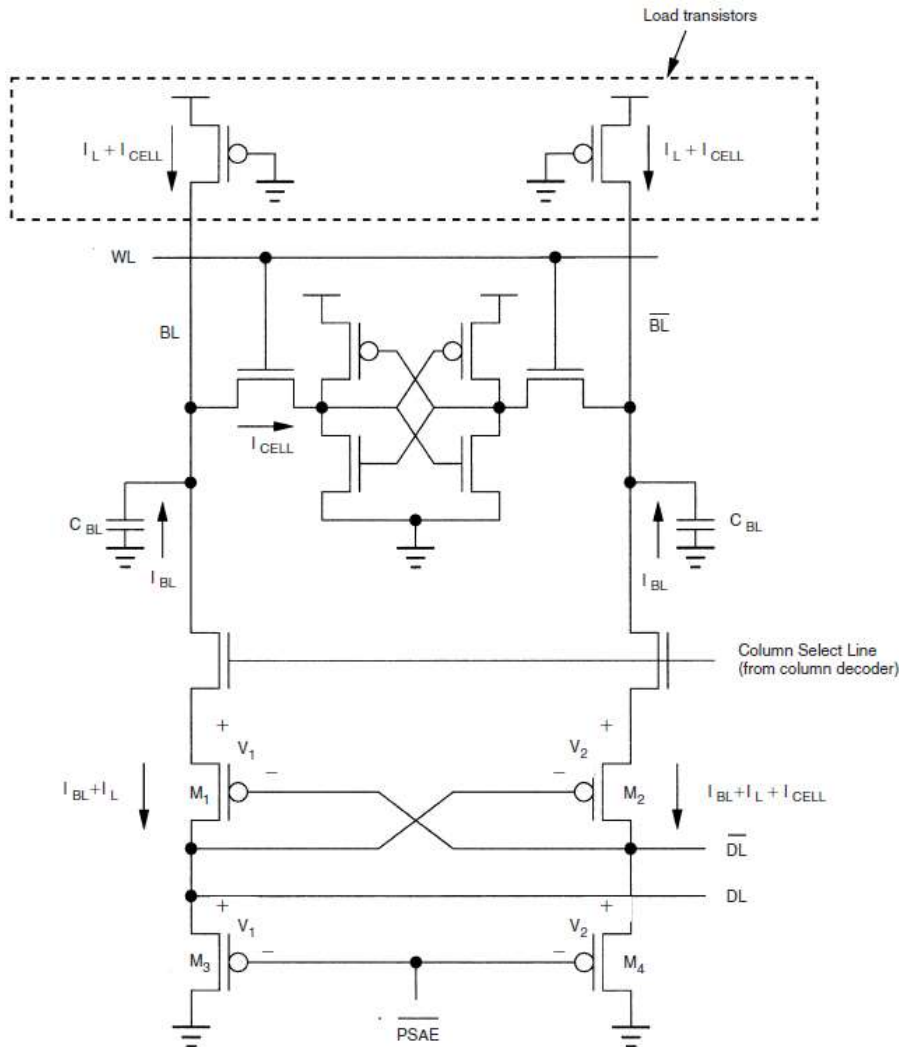

- ◆ Current-mode sense amp widely used in SRAM
- ➔ improve signal sensing speed independent of bit line cap.
- ◆ Signal line connect to source of latch transistor
- ◆ Current difference appears on DL and \overline{DL}
- ◆ Open-loop gain


$$Gain_{open-loop} = \frac{g_m(m3) \times g_m(m4)}{g_m(m1) \times g_m(m2)}$$
- ◆ Current-mode sense amp:
Drawback- larger power consumption

SRAM Cell at Low Supply Voltage

- ◆ SRAM cell susceptible to variabilities
 - Due to minimum device size to a minimize area
 - Threshold voltage variation covered in Ch. 3 plus layout induced threshold voltage variation
 - PMOS pair (M5, M6) in SRAM cell- different V_T due to NBTI
 - NMOS pair (M1, M2) in SRAM cell- different V_T due to PBTI

- ◆ Static noise margin (SNM)

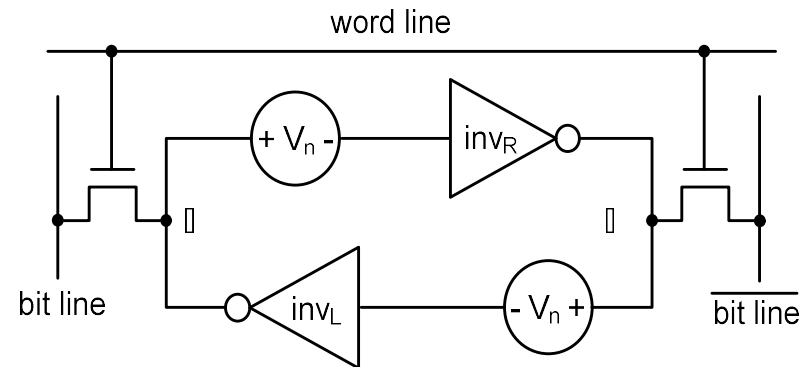
- A noise tolerant voltage before the stored data flip
- Equivalent ckt to measure SNM
- 6-T SRAM cell at low supply voltage degrades SNM



V_n : DC noise, SNM: min. DC noise which flips the state of SRAM cell during read operation

SNM Variation due to DC Noise

◆ How to measure SNM graphically

 

- SNM: The length of side of the smaller nested square in the two openings of butterfly curve
- Before two V_n s are fed: $SNM = V_S$
- After V_n s are fed: stable point A and unstable point B meets at D
- More V_n s are applied: one common point C & the stored bits are flipped



SRAM Cell Writability

◆ Write-trip point



- A metric for writability
- Max. bit line voltage to flip the state of the SRAM cell
- Primarily determined by the pull-up ratio of SRAM cell (Ex: $(W/L)_5/(W/L)_3$)

◆ Variability tolerant 6T SRAM cell

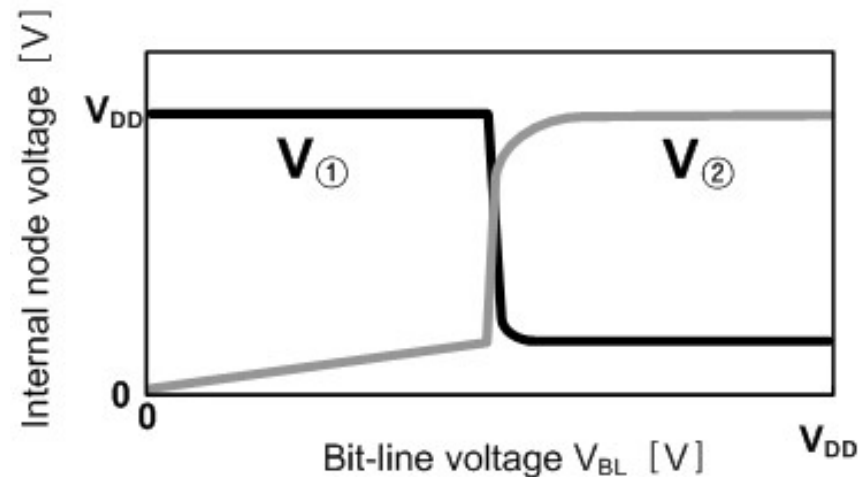 - Trade off bw. read stability and writability
- M_3 & M_4 \uparrow :
SNM \uparrow , writability \downarrow




8T SRAM Cell

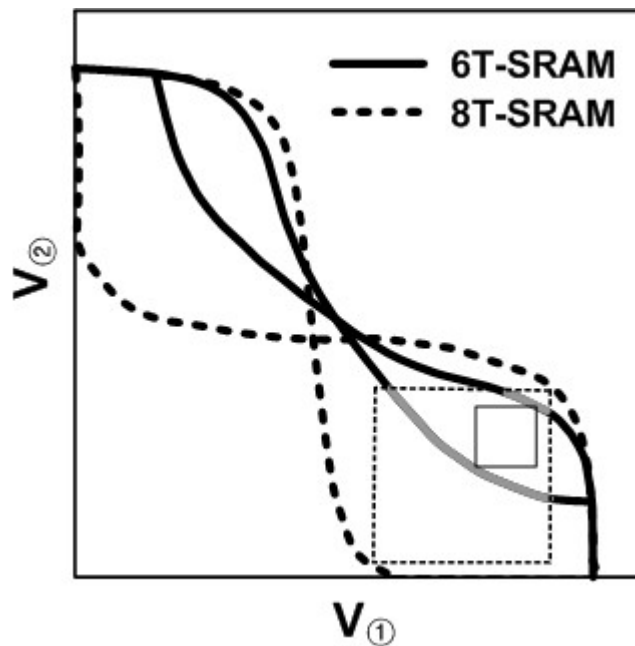 

- No secondary power supplies
- Decouples the SRAM cell nodes from the bit line which enables balancing the read & write modes
- Read operation doesn't affect the stored data
- 6T cell has the worst SNM in read operation where the pass gate transistor increases the voltage at the '0' stored

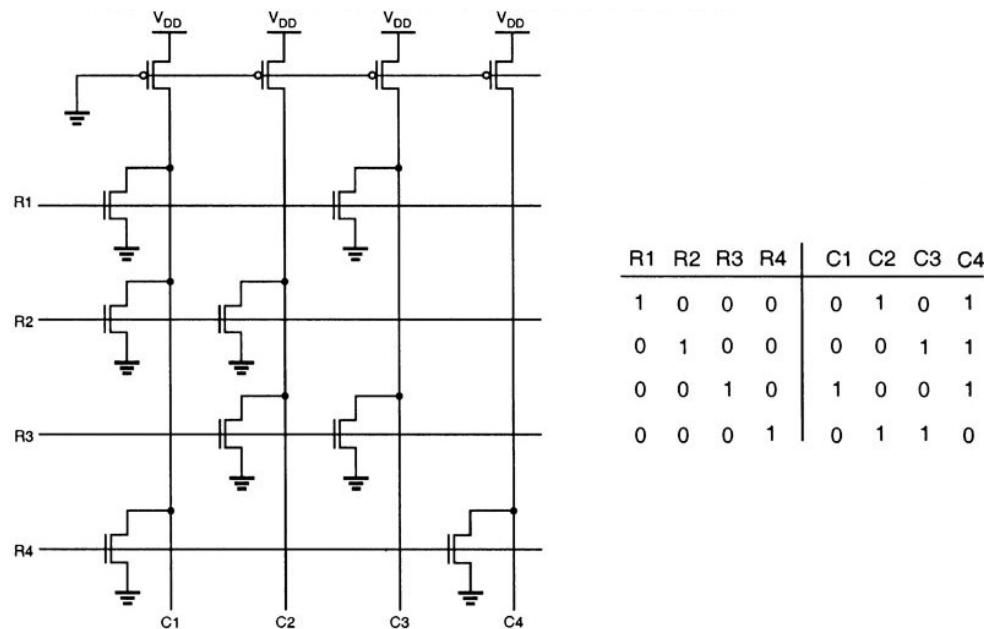
10.4 Nonvolatile Memory

- ◆ Simple combinational Boolean network
- ◆ Only one word line selected at a time
- ◆ Active transistors exist at cross point
- ◆ Dynamic ROM
 - use periodic precharge signal to reduce static power



Layout of NOR ROM Array(1)

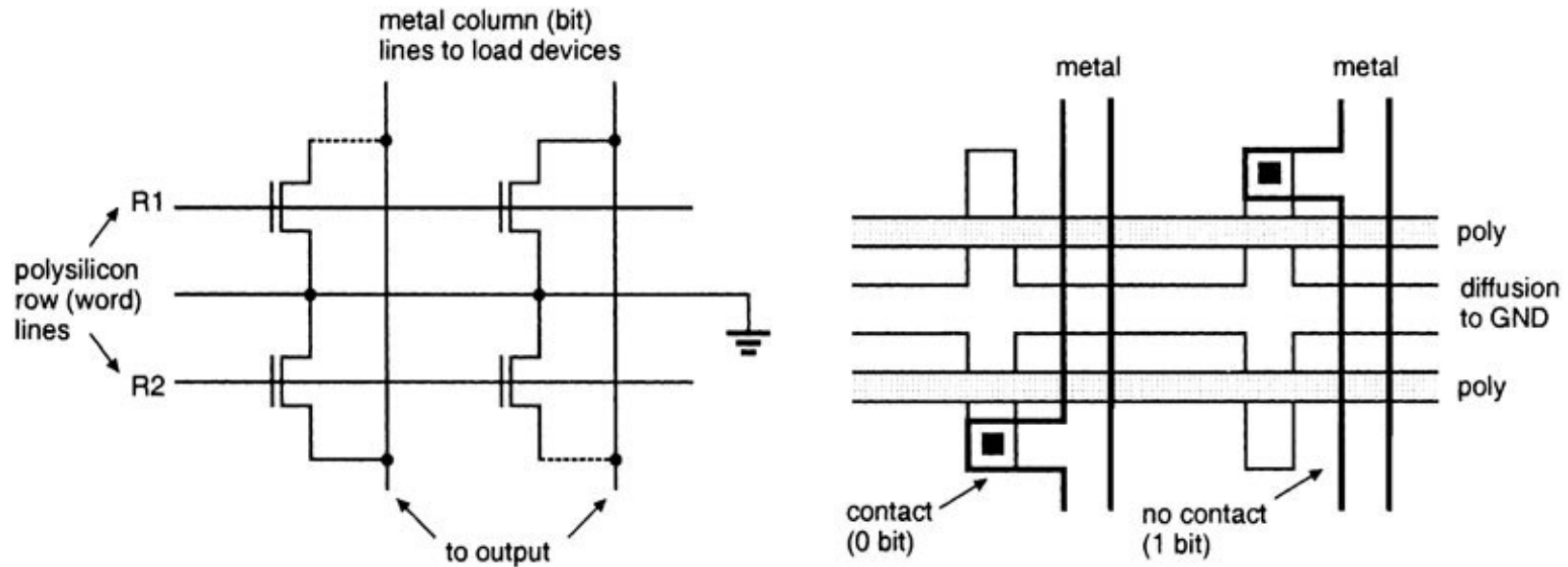
- ◆ Initially, NMOS at every row-column intersection
- ◆ '1'-bits are realized by omitting drain or source connection or gate electrode of corresponding NMOS



Layout example of a NOR ROM array

Layout of NOR ROM Array(2)

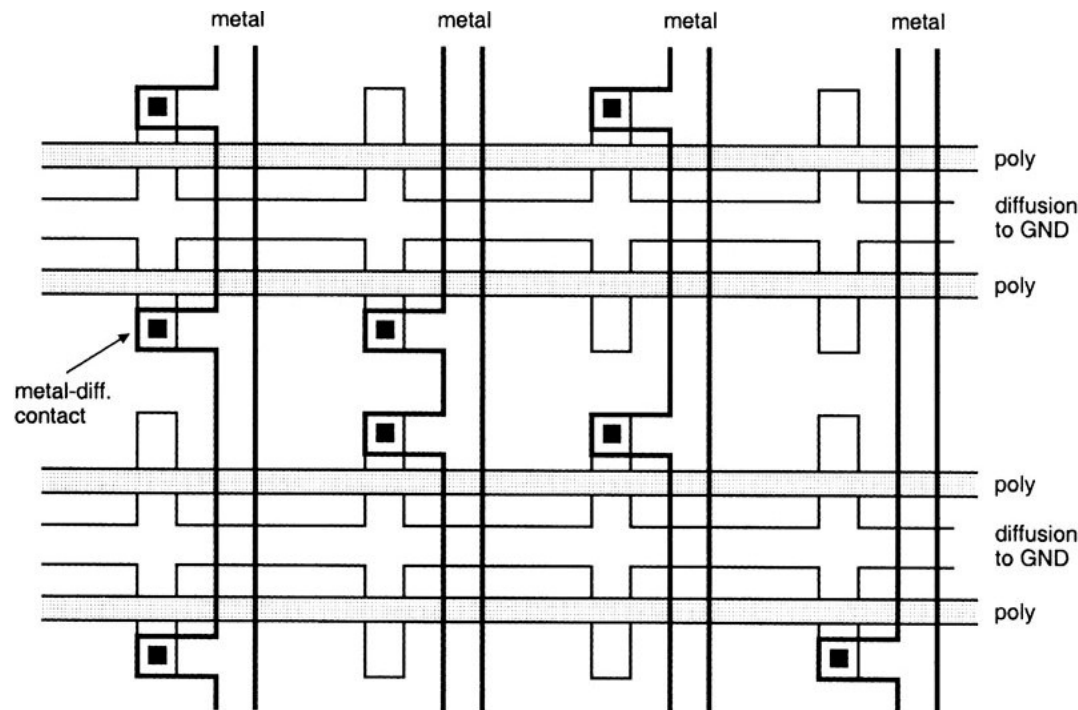
- ◆ In reality, metal column lines laid out directly on top of diffusion column to reduce horizontal dimension



Layout of the 4-bit X 4-bit NOR ROM array (pp. 46)


Implant-mask Programmable NOR ROM

 - ◆ Every two rows share a common ground connection
- ◆ Every metal to diffusion contact shared by two adjacent devices




4-bit x 4-bit NOR ROM Array

 - ◆ Based on implant-mask programming
- ◆ Raised threshold voltage $> V_{OH}$ \rightarrow "1"-bit
- ◆ Non-implanted \rightarrow "0"-bit
- ◆ higher core density (smaller silicon area per stored bit)



4-bit x 4-bit NAND ROM Array

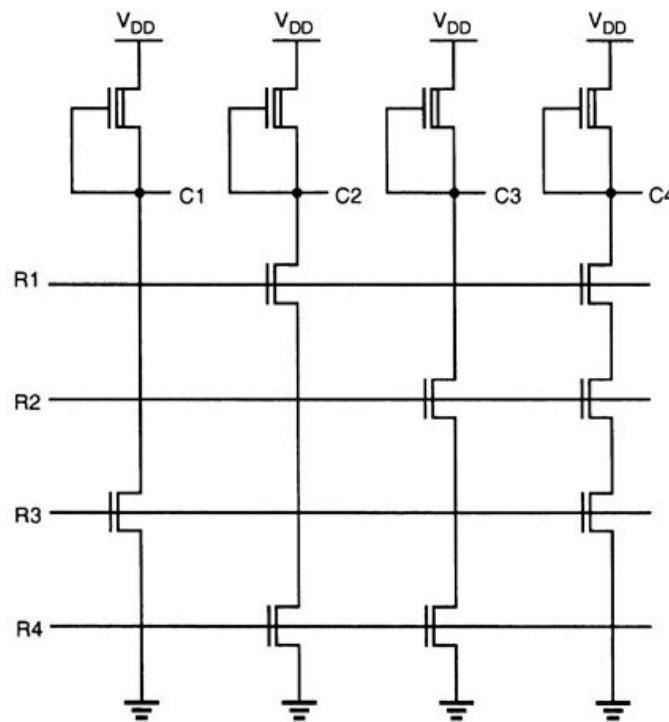
- ◆ Bit line : depletion-load NAND gate
- ◆ Deactivated transistor → "1"-bit
- ◆ Shorted or on transistor → "0"-bit



R1	R2	R3	R4	C1	C2	C3	C4
0	1	1	1	0	1	0	1
1	0	1	1	0	0	1	1
1	1	0	1	1	0	0	1
1	1	1	0	0	1	1	0


Implant-mask layout of NAND ROM

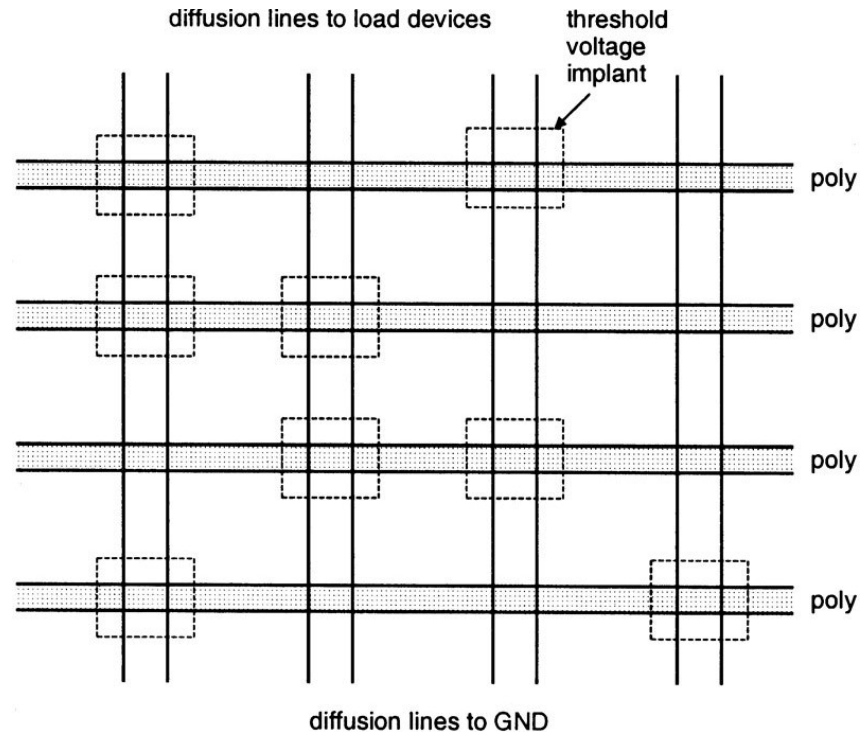- ◆ Lowered threshold voltage $< 0V \rightarrow$ "0"-bit
- ◆ Much more compact than NOR ROM
- ◆ Access time is slower than NOR ROM




Design of Row and Column Decoders(1)

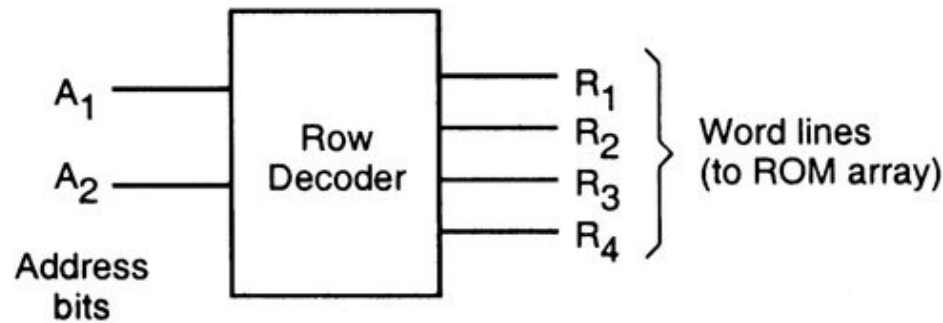- ◆ Select a particular memory location in array
- ◆ Row address decoder example




A ₁	A ₂	R ₁	R ₂	R ₃	R ₄
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

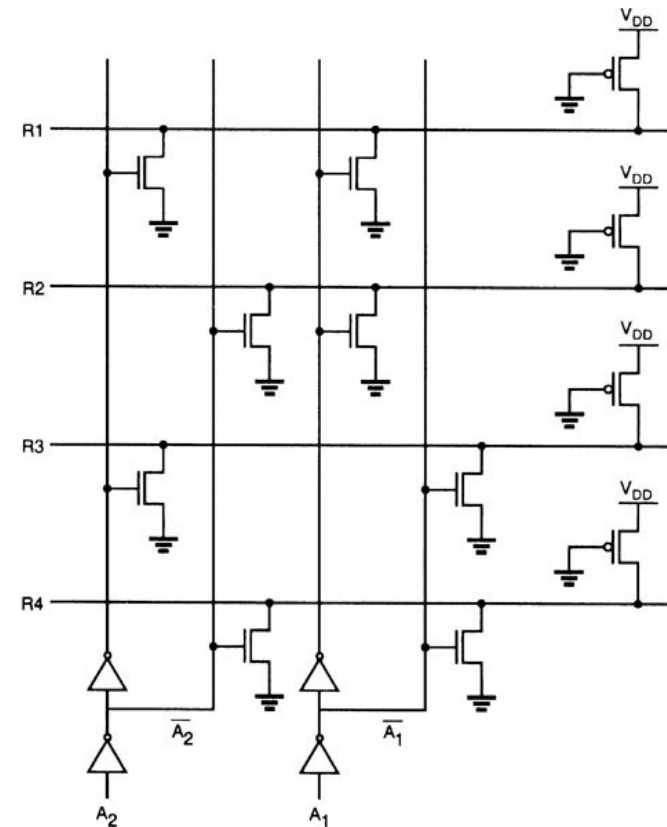


Design of Row and Column Decoders(2)

 - ◆ ROM array and row decoder (two adjacent NOR arrays)




Row Decoder for NAND ROM

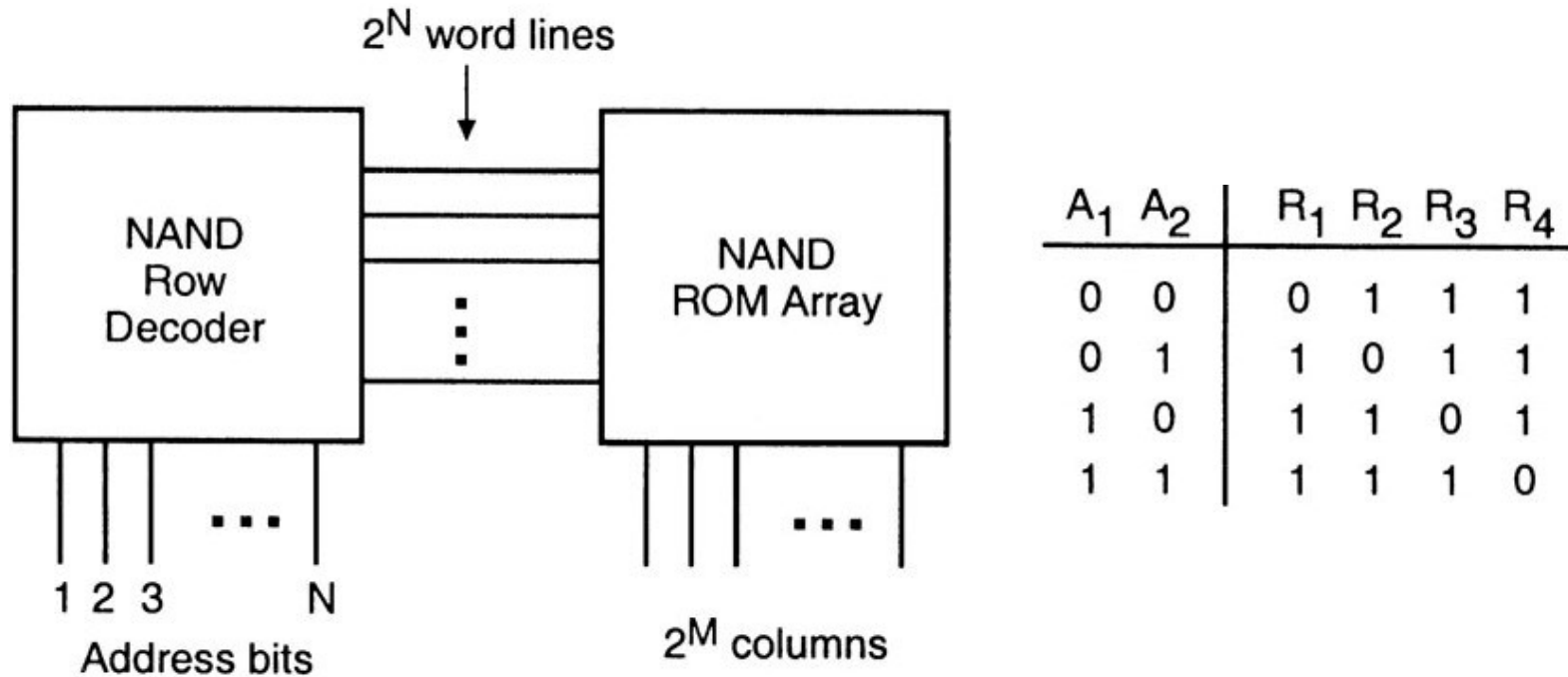- ◆ Lower voltage for logic "0"
- ◆ Realized using same layout strategy as memory array




Column Decoder(1)

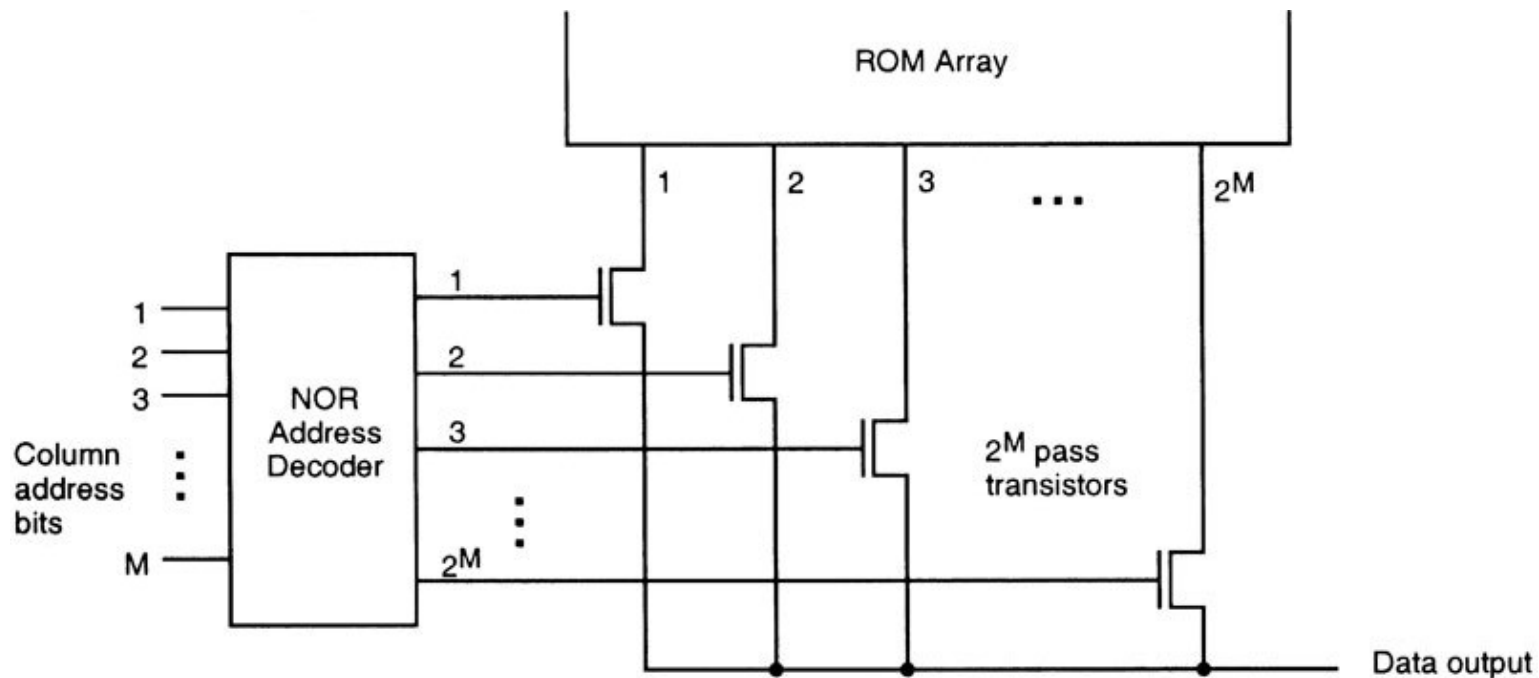- ◆ Using NOR address decoder and NMOS pass transistor
- ◆ Only one pass transistor turned on at a time
- ◆ $2^M(M+1)$ transistors required




Column Decoder(2)

- ◆ Binary selection tree decoder
- ◆ NOR address decoder not needed
 - ➔ Reduce the number of transistors significantly
- ◆ But, long data access time

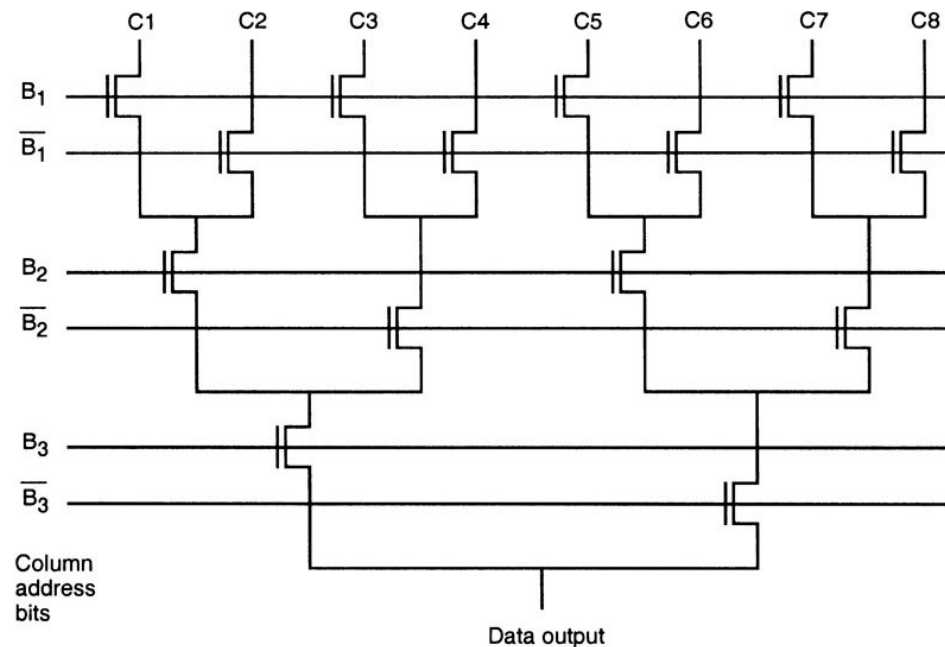

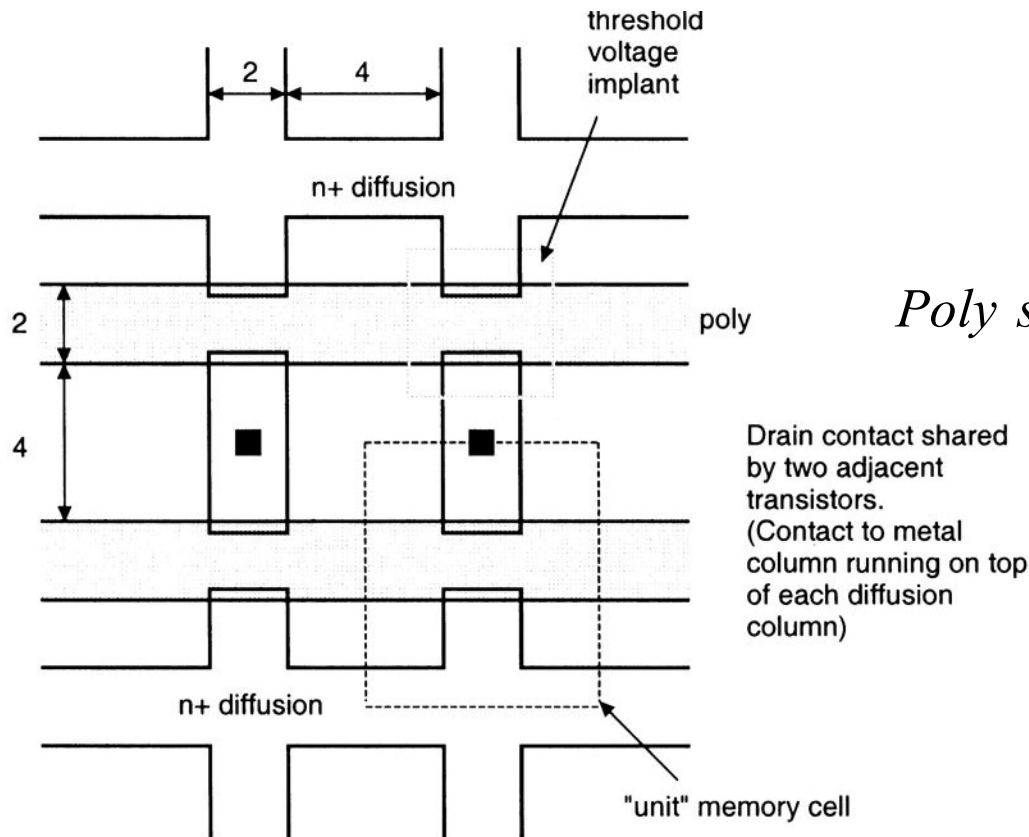Example 10.1(1)

- ◆ Analyze the access time of a 32-kbit NOR ROM array




$$\mu_n C_{ox} = 20 \mu A / V^2$$

$$C_{ox} = 3.47 \mu F / cm^2$$

Poly sheet resistance = 20Ω / square

 Example 10.1(2)

- Assume 7 row address bits and 8 column address bits (128 rows and 256 columns)
- Calculate row resistance and capacitance



$$C_{row} = C_{ox} \cdot W \cdot L = 10.4 \text{ fF / bit}$$


$$R_{row} = (\# \text{ of squares}) \times (\text{Poly sheet resistance}) = 60 \Omega / \text{bit}$$

- Calculate row access time

$$t_{row} \approx 0.38 \cdot R_T \cdot C_T = 15.53 \text{ ns}$$

$$R_T = \sum_{\text{all columns}} R_i = 15.36 \text{ k}\Omega$$

$$C_T = \sum_{\text{all columns}} C_i = 2.66 \text{ pF}$$

 

Example 10.1(3)

- A more accurate delay: Elmore time constant for RC ladder circuits


$$t_{row} = \sum_{k=1}^{256} R_{jk} C_k = 20.52ns \quad \text{where} \quad R_{jk} = \sum_{j=1}^k R_j$$

- Calculate column access time

$$C_{column} = 128 \times (C_{gd,driver} + C_{db,driver})$$


$$\approx 1.5pF$$

where $C_{gd,driver} + C_{db,driver} = 0.0118pF / \text{word line}$

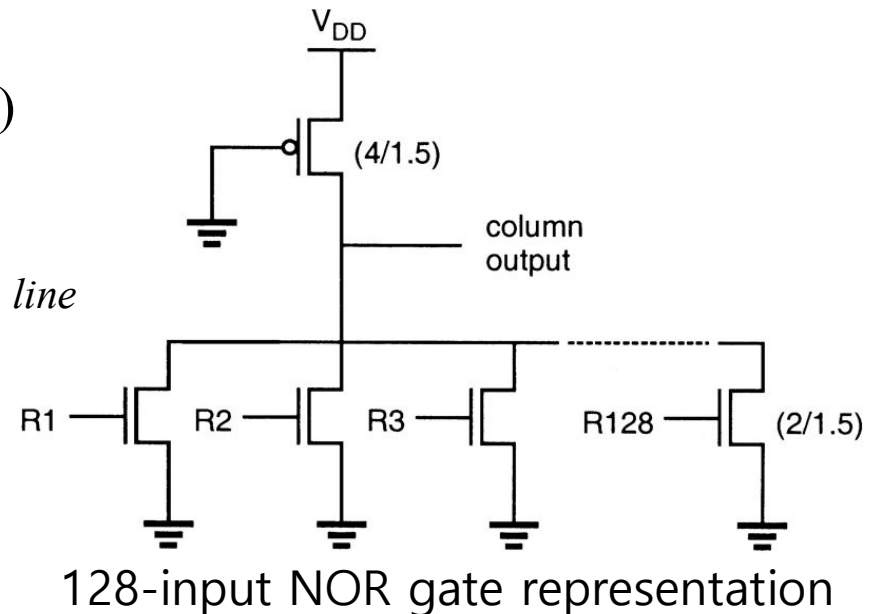

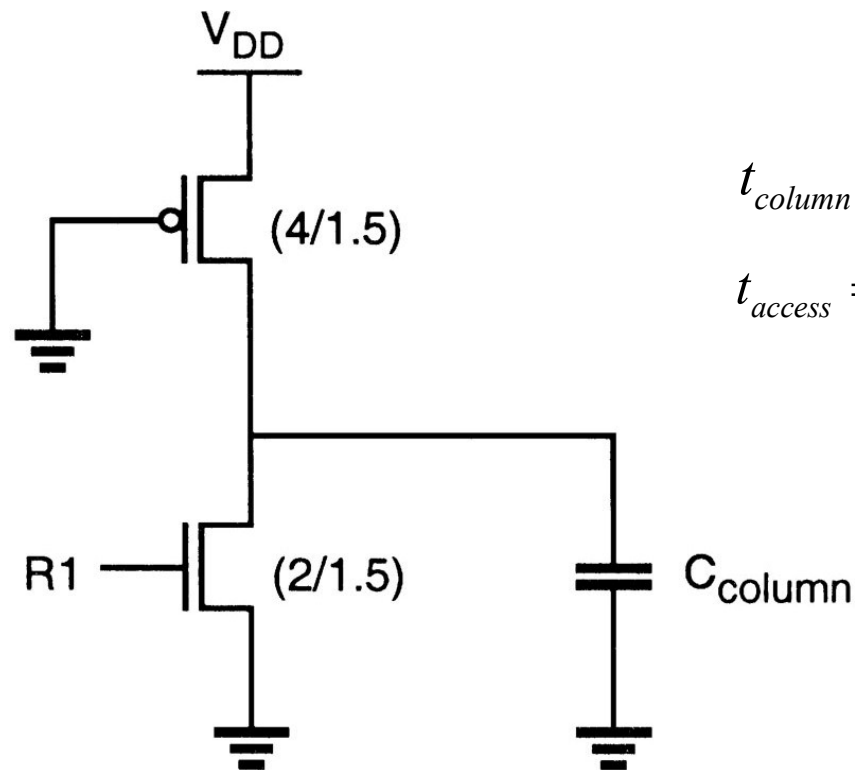Example 10.1(4)

- To calculate column access time, consider the worst-case signal propagation delay τ_{PHL} for below inverter




$$t_{\text{column}} = 18ns \quad (\text{using eq. 6.18: } t_{\text{PHL}})$$


$$t_{\text{access}} = t_{\text{row}} + t_{\text{column}} = 38.5ns$$

 10.5 Flash Memory

- ◆ One transistor with floating gate
- ◆ Memory cell can have two states (two threshold)
- ◆ Electron accumulated at the floating gate → higher threshold → "1" state
- ◆ Electron removed from the floating gate → lower threshold → "0" state




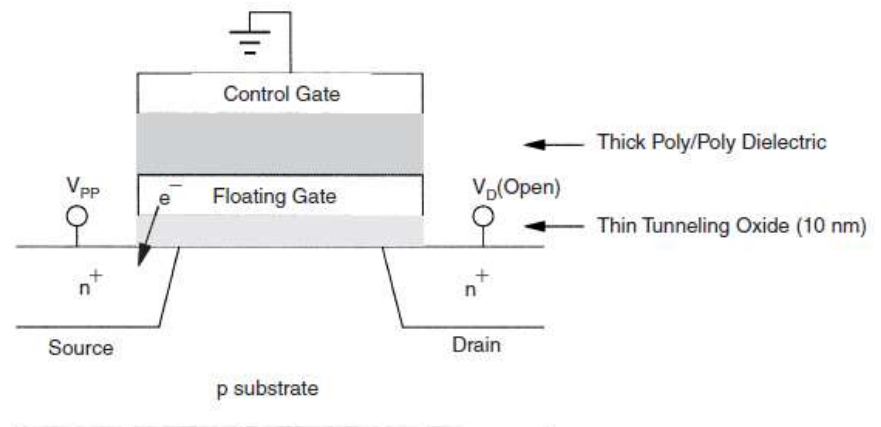Hot electron injection mechanism
(Data programming)



Fowler-Nordheim tunneling mechanism
(Data erasing)

Equivalent Capacitive-Coupling Circuit

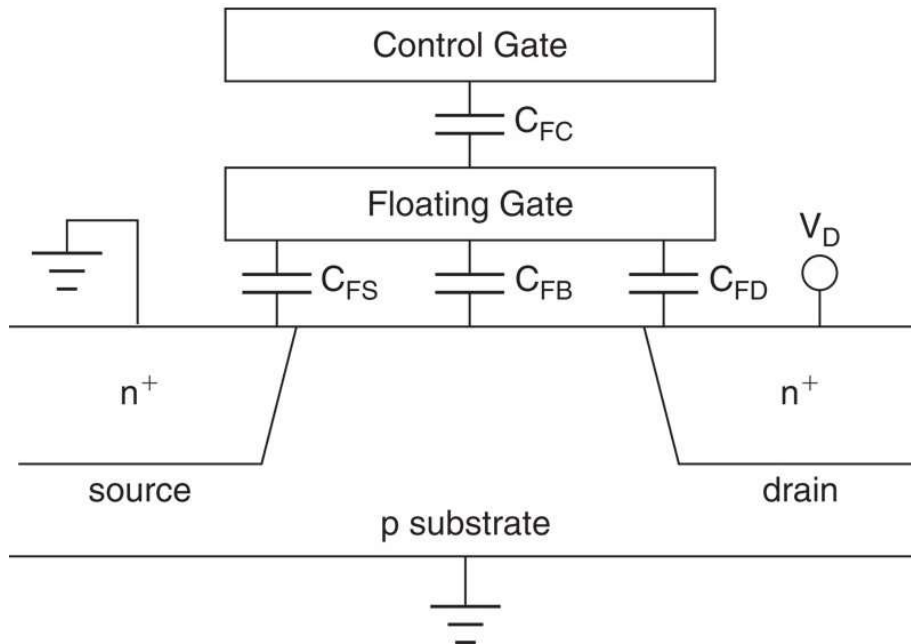

Q_{FC} : charge stored at floating gate

C_{total} : total cap.

C_{FC} : cap. between floating and control gate

C_{FS} , C_{FB} and C_{FD} : cap. between floating gate and source, bulk and drain

V_{CG} and V_D : voltage at control gate and drain

$V_T(FG)$: threshold voltage to turn on the floating gate transistor

- V_{FG} by capacitive coupling after V_{CG} & V_D applied

$$V_{FG} = \frac{Q_{FG}}{C_{total}} + \frac{C_{FC}}{C_{total}} V_{CG} + \frac{C_{FD}}{C_{total}} V_D$$

$$C_{total} = C_{FC} + C_{FS} + C_{FB} + C_{FD}$$


- min. V_{CG} to turn on the control gate transistor

$$V_T(CG) = \frac{C_{total}}{C_{FC}} V_T(FG) - \frac{Q_{FG}}{C_{FC}} - \frac{C_{FD}}{C_{FC}} V_D$$

$$\Delta V_T(CG) = -\frac{\Delta Q_{FG}}{C_{FC}}$$


I-V Characteristic of Flash Memory

 - ◆ Low and high threshold voltages for control gate voltage



NOR Flash Memory Cell

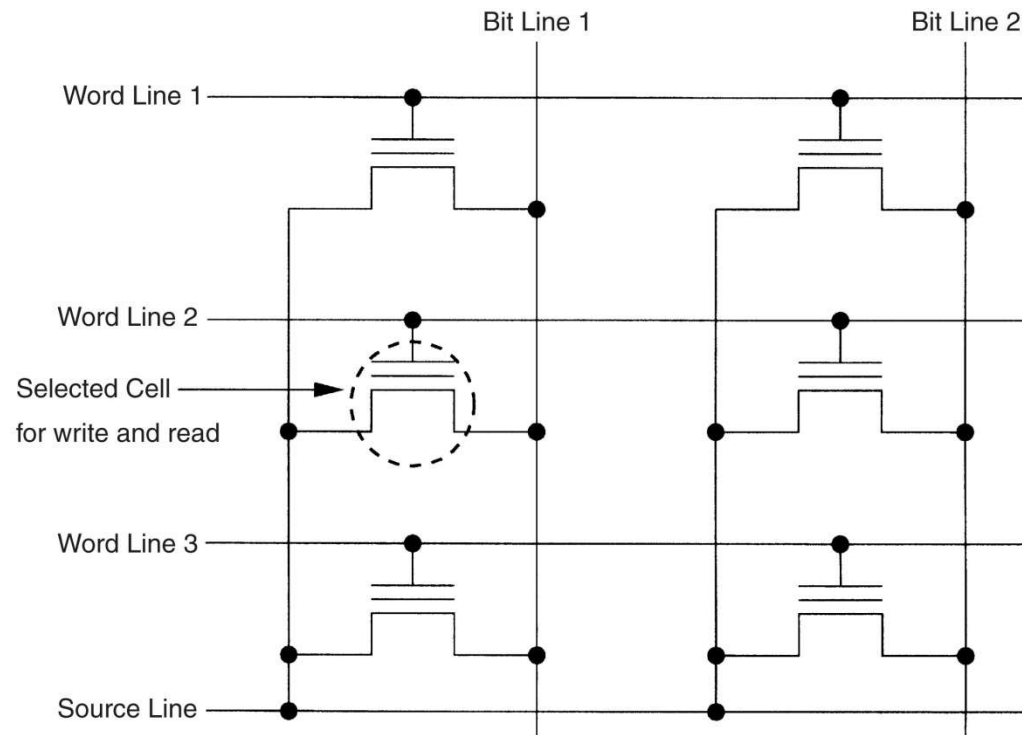- ◆ Bias conditions and configuration of NOR Cells




- ◆ F-N tunneling mechanism for erase operation
- ◆ Hot-electron injection mechanism for programming operation

Bias Conditions of NOR Cell


Signal	Operation		
	Erase	Programming	Read
Bit line 1	Open	6V	1V
Bit line 2	Open	0V	0V
Source line	12V	0V	0V
Word line 1	0V	0V	0V
Word line 2	0V	12V	5V
Word line 3	0V	0V	0V

NAND Flash Memory Cell

 ◆ Cross-section view and configuration of NAND cells



 - ◆ F-N tunneling mechanism for erase
- ◆ F-N tunneling mechanism for program
- ◆ Slower programming and read speed but smaller area than NOR cell structure



Bias Conditions of NAND Cell


Signal	Operation		
	Erase	Programming	Read
Bit line 1	Open	0V	1V
Bit line 2	Open	0V	1V
Select line 1	Open	5V	5V
Word line 1	0V	10V	5V
Word line 2	0V	10V	5V
Word line 3	0V	10V	5V
Word line 4	0V	10V	5V
Word line 5	0V	20V	0V
Word line 6	0V	10V	5V
Word line 7	0V	10V	5V
Word line 8	0V	10V	5V
Select line 2	Open	0V	5V
Source line	Open	0V	0V
p-well 2	20V	0V	0V
n-sub	20V	0V	0V

Comparison between NOR and NAND

	NOR	NAND
Erase method	F-N tunneling	F-N tunneling
Programming method	Hot electron injection	F-N tunneling
Erase speed	Slow	Fast
Program speed	Fast	Slow
Read speed	Fast	Slow
Cell size	Large	Small
Scalability	Difficult	Easy
Application	Embedded system	Mass storage

Multilevel Cell Concept

 - ◆ Effective memory density can be improved
- ◆ Possible state number limited by
 - Available charge range
 - Accuracy of programming and read operations
 - Disturbance of state over time




Threshold voltage distribution of 2bits/cell storage

Flash Memory Circuit


- ◆ On-chip charge pump used to generate programming voltage
- ◆ Chain of diode and cap. to charge or discharge each half cycle
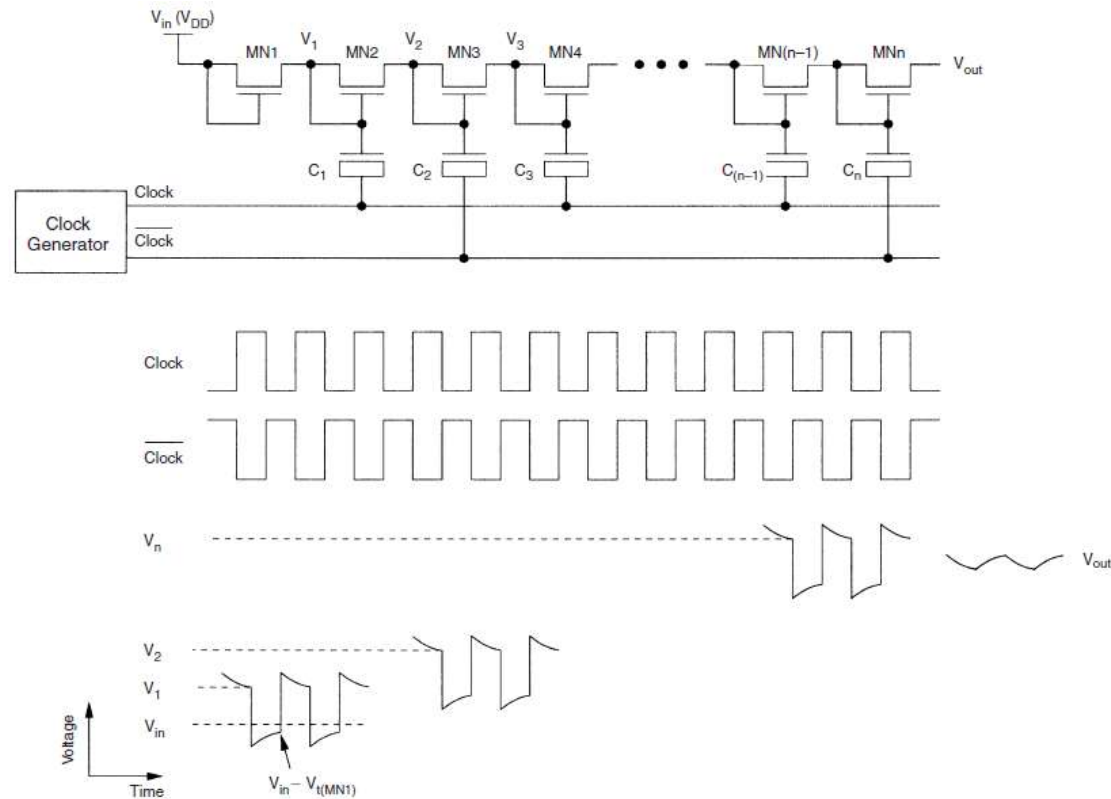
$$V_{out} = V_{in} + (\gamma V_{DD} - V_T(MN1)) + \dots + (\gamma V_{DD} - V_T(MNn))$$



 10.6 Ferroelectric Random Access Memory


- ◆ Hysteresis characteristic of a ferroelectric cap.



- ◆ Total charge varies as function of applied voltage

Structure and Operation of FRAM

- ◆ Similar to DRAM except plate line

 

Problems of FRAM

- ◆ Step-sensing scheme cause reliability issues
 - Pulse sensing scheme also used with read speed penalty
- ◆ Fatigue
 - Capacitance charge gradually degraded with repeated use
- ◆ Imprint
 - Ferroelectric cap tends to stay at one state preferably when state maintained for a long time