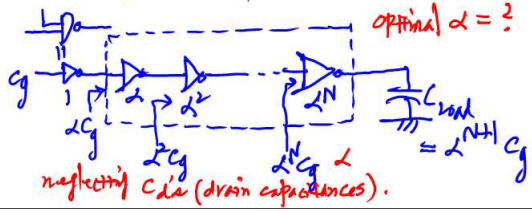


### Super Buffer Design & Analysis

input → How to drive a large load? putting a super buffer for large  $C_L$ .

Textbook (Rang et al.) page 297



$$\alpha^{N+1} C_g = C_{load}$$

$$(N+1) \ln \alpha = \ln \frac{C_{load}}{C_g}$$

$$\Rightarrow N+1 = \frac{\ln \frac{C_{load}}{C_g}}{\ln \alpha}$$

Total delay  $\tau_{total} = (N+1) (\tau_0 \alpha) \leftarrow \tau_0$

$$= \tau_0 \alpha \cdot \frac{\ln \frac{C_{load}}{C_g}}{\ln \alpha}$$

$$\frac{\partial \tau_{total}}{\partial \alpha} = \tau_0 \ln \left( \frac{C_{load}}{C_g} \right) \ln \alpha - \tau_0 \alpha \cdot \frac{1}{\alpha} \frac{1}{\ln \alpha} = 0$$

$$\ln \alpha - 1 = 0 \Rightarrow \alpha^* = e$$

2-718

