
Adiabatic circuits for low power and PLL(Phase Locked Loop) for high speed communications

2019. 10. 17

Soongsil University
School of Electronic Engineering
Prof. Yong Moon

Outline

- 1. Introduction**
- 2. Low Power Technology**
- 3. Adiabatic Circuits**
- 4. PLL basics**
- 5. Digital Approaches**
- 6. Other Issues**


Introduction

- Low power becomes major design goal
 - Battery life for portable system
 - Cooling cost in non-battery powered system
 - Charge loss of conventional static CMOS
 - Leakage power is growing
 - Applications without refueling the energy
- Moore's paper
 - Reliability, cost, complexity, yield
 - And Heat problem → power

Introduction

- Power, Applications and considerations
 - 1-10W: most of applications
 - Cost, performance, package
 - 0.1-1W : mobile, cellular
 - battery, performance, package, cost
 - $10\mu\text{W}$ - $100\mu\text{W}$: sensor
 - battery, replacement cost
- Variability problem
 - FFHH vs. TTTH
 - Power : 1.6x
 - Leakage power : 8x

Low Power Technology Hierarchy

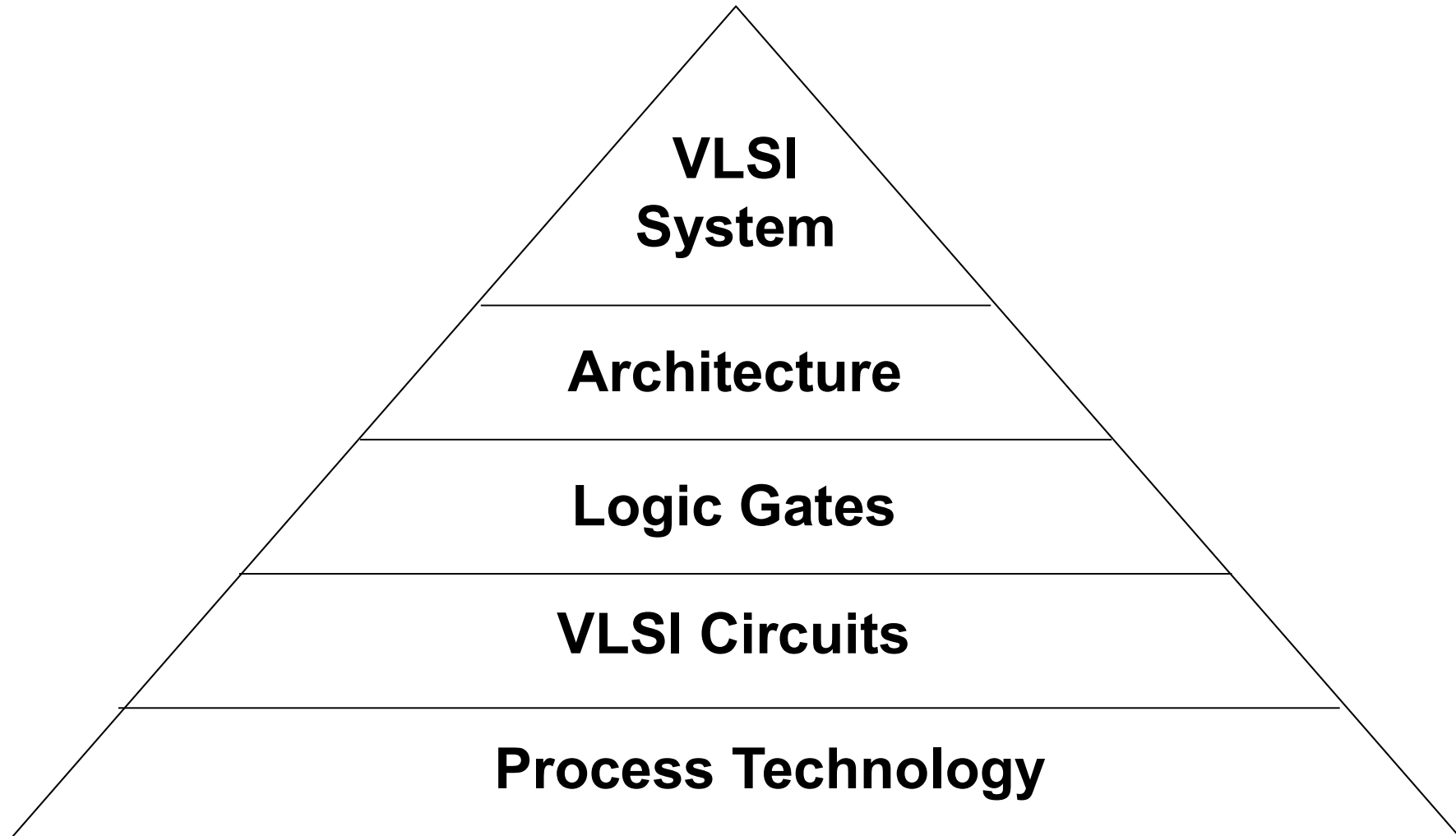



LP System Architecture

- Low power architecture choices
 - Algorithms
 - Partitioning
 - HW/SW
 - system-level: analog, digital
 - Pipelining
 - Bus, memory
 - DVFS(Dynamic voltage frequency scaling)
 - Multi-VDD design
 - Power gating
 - Clock gating

LP Transistor Level Work

- Leakage reducing techniques
 - Lowering operating voltage
 - Power gating
 - Dual threshold voltage
 - Cell sizing
 - Non-minimum size gate lengths
 - Substrate biasing
 - Stacking transistor
- Reduce gap between automated and custom design



Concept of Adiabatic Circuit

  

$$E_{Total} = qV_{dd} = CV_{dd}^2$$

$$E_C = CV_{dd}^2 / 2$$

$$E_R = CV_{dd}^2 / 2 \text{ (heat)}$$

  


$$E_{diss} = I^2 RT = \left(\frac{CV_{dd}}{T}\right)^2 RT = \left(\frac{RC}{T}\right) CV_{dd}^2$$

if $RC \ll T$ then $E_{diss} \rightarrow 0$

Returning delivered charge

Using AC supply clock



Basic Operation of Adiabatic Circuits

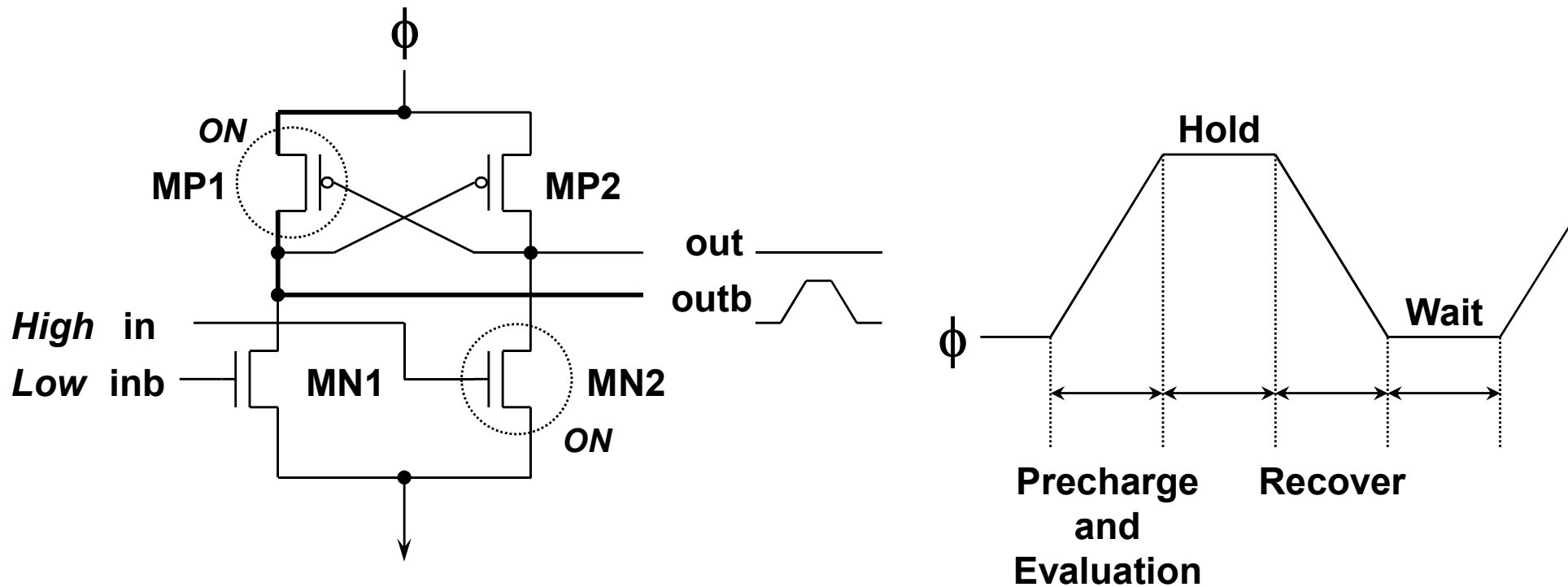

- ECRL(Efficient Charge Recovery Logic)
- Asymptotic energy loss : $E_{ECRL} = C|V_{TP}|^2$



Circuit Construction

(Inverter Chain)

 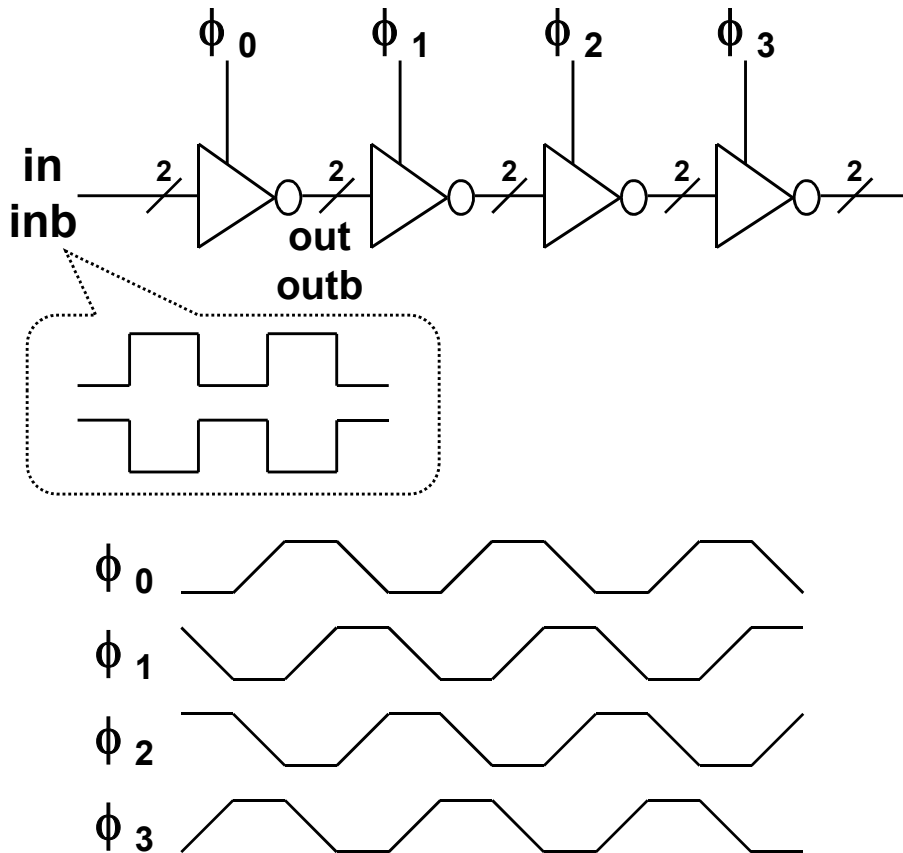


Gate Design

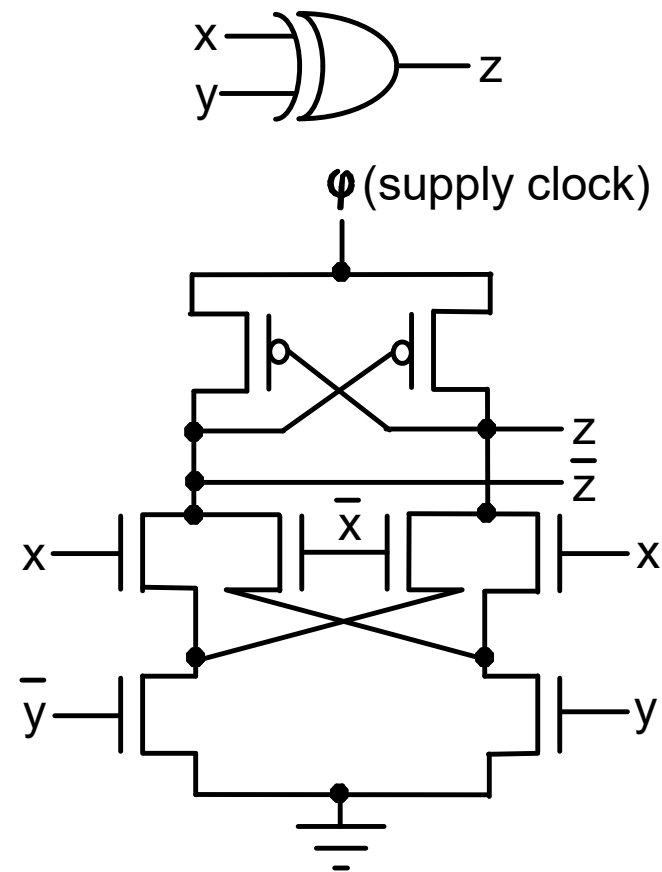 
- Same construction as CVSL(Cascode Voltage Switching Logic)




PG Logic for Adder

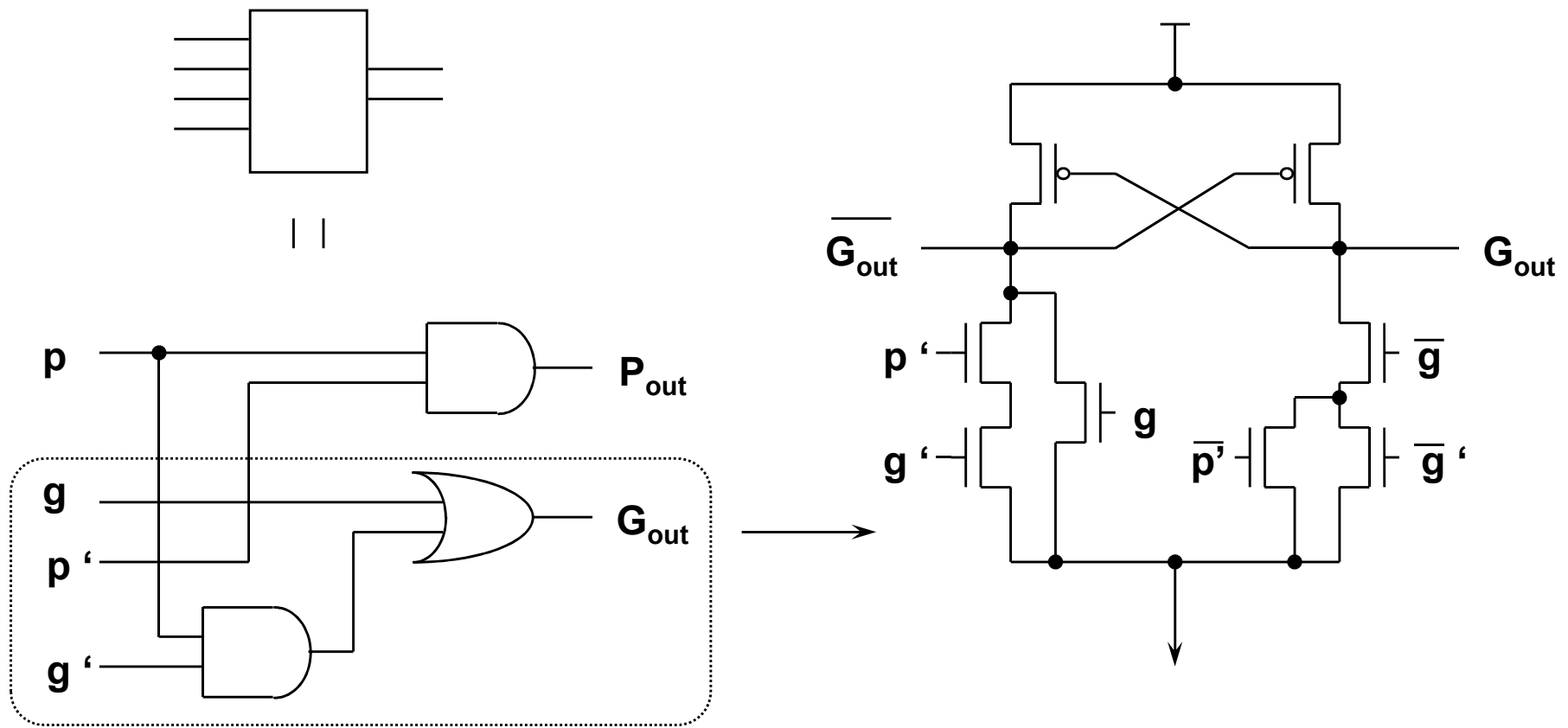

Interface Circuits


 


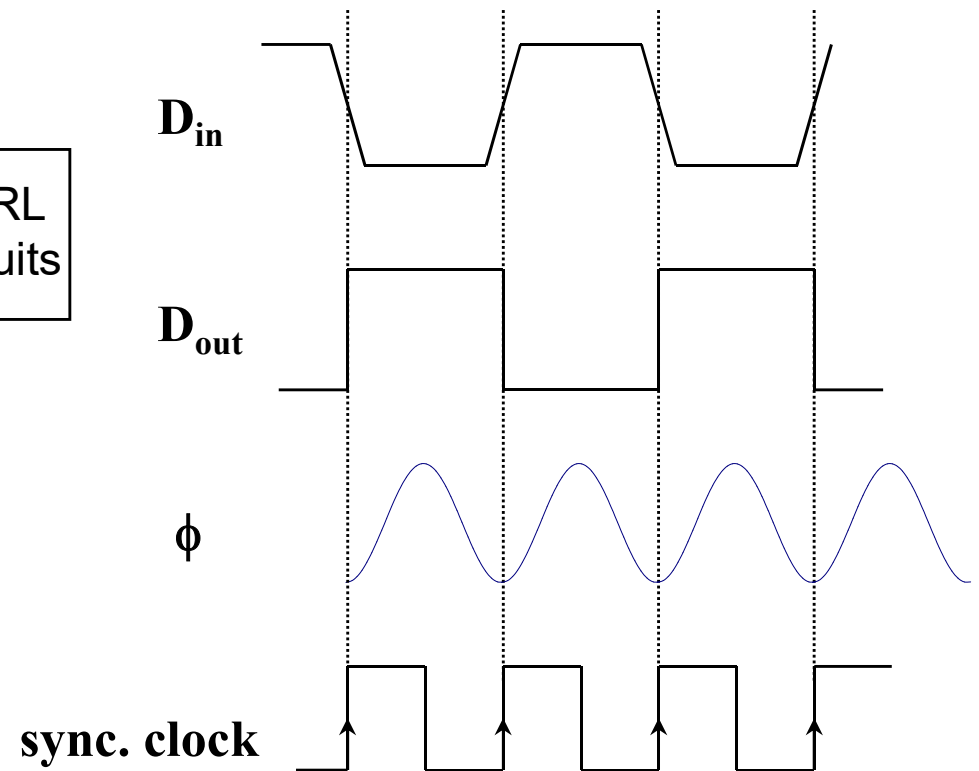**Rising edge-triggered
D-type Flip-Flop**




Principles of Clock Circuit

- LC resonant circuit

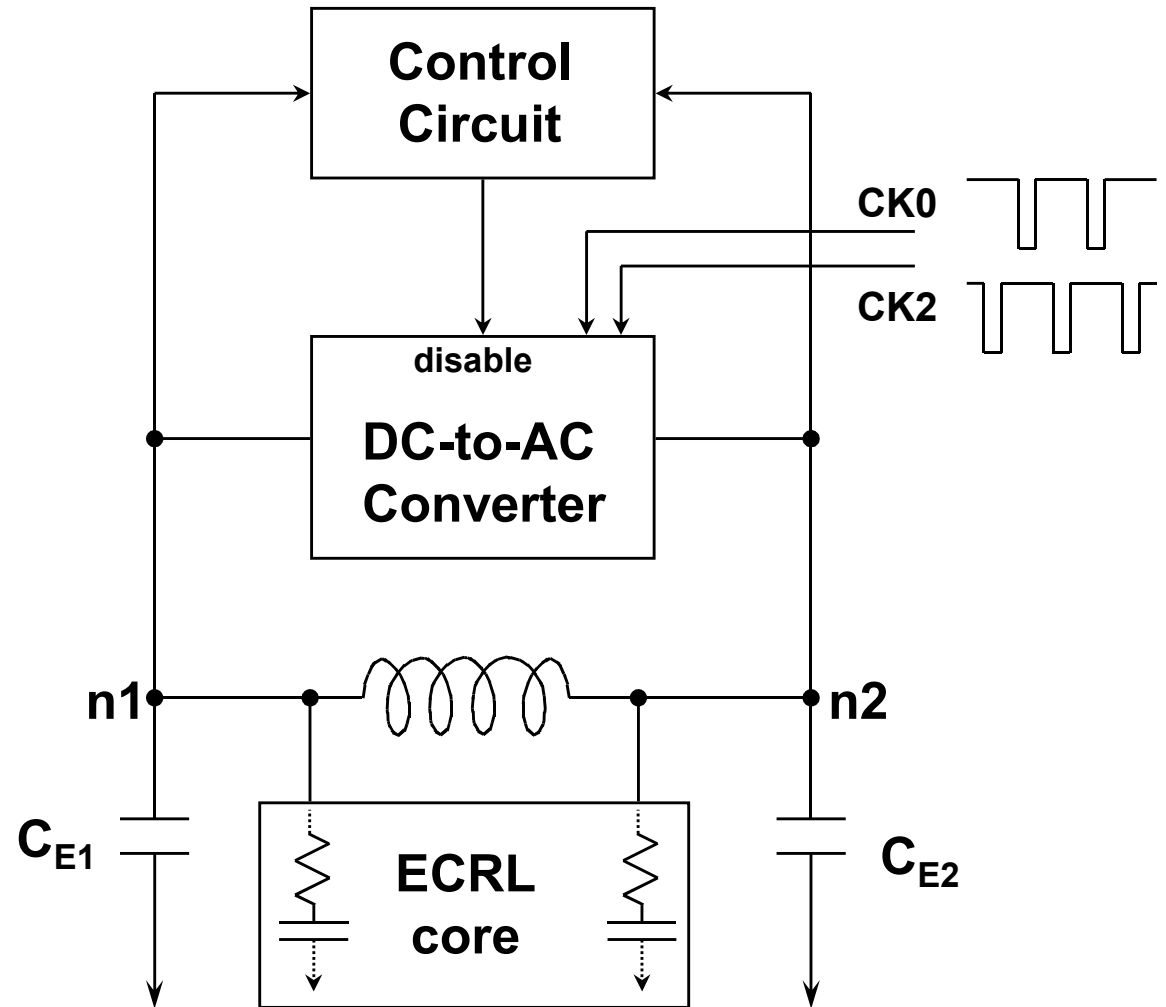 

Supply Clock Generator

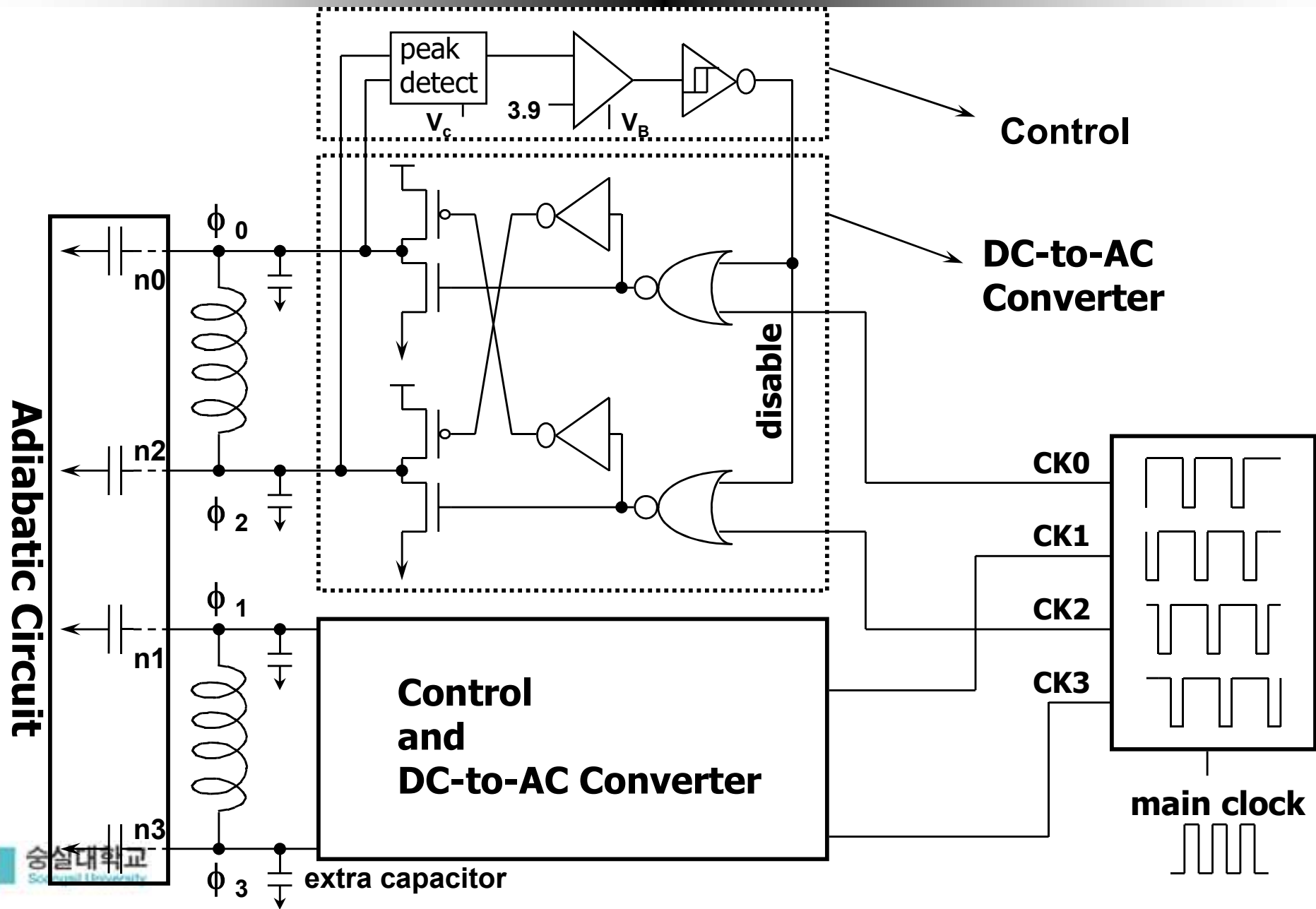

Energy Efficiency

(16-bit ECRL CLA operating at 10MHz)

Block	Sub-block	Power [uW]			
ECRL core	16-bit adder	258	258	1178	
DC-to-AC Converter	NOR gate	27	365		
	Inverter	60			
	MOS switches	278			
Control Circuit	Peak Detector	50	555		
	Comparator	264			
	Schmitt Trigger	241			
Conventional CMOS					1430



$$\text{Conversion Efficiency} = 258 / (258 + 365) = 41\%$$

$$\text{Power Gain over CMOS} = 1 - (258 + 365) / 1430 = 56\%$$

$$\begin{aligned} \text{Power Gain over CMOS with Common Block} \\ = 1 - 1178 / 1430 = 18\% \end{aligned}$$



2-Phase Clocked Adiabatic Static CMOS Logic

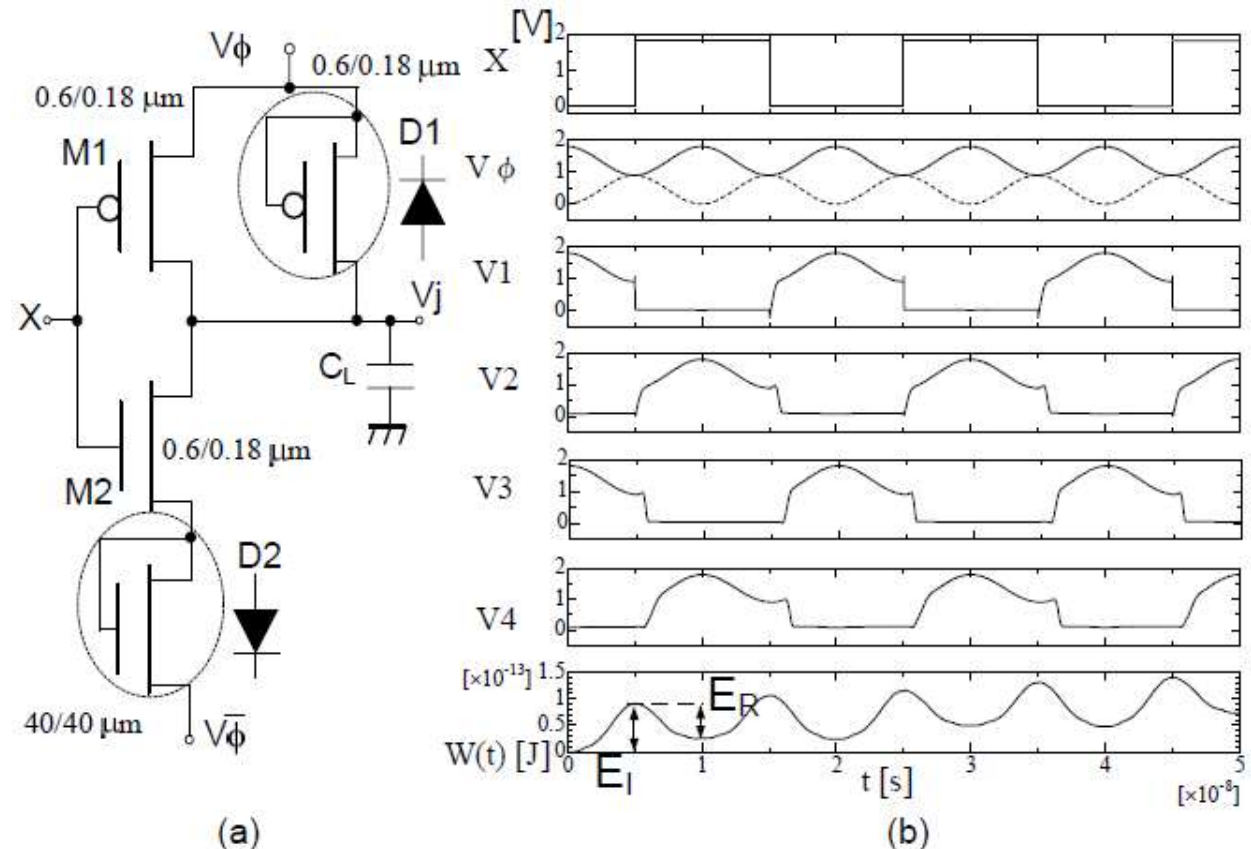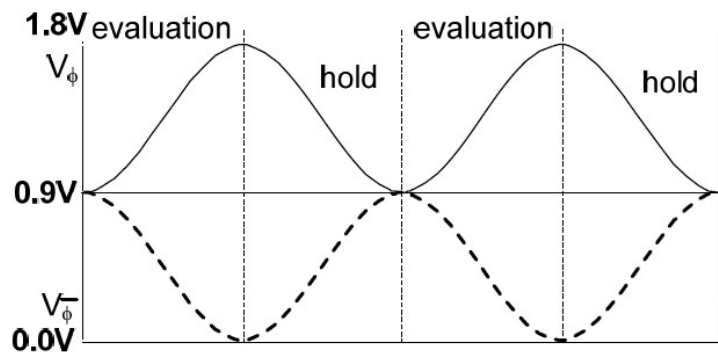- 2010, Gifu University, Japan
 - 2 complementary split-level sinusoidal power supply clocks (V_{dd})



Power Clock Generator

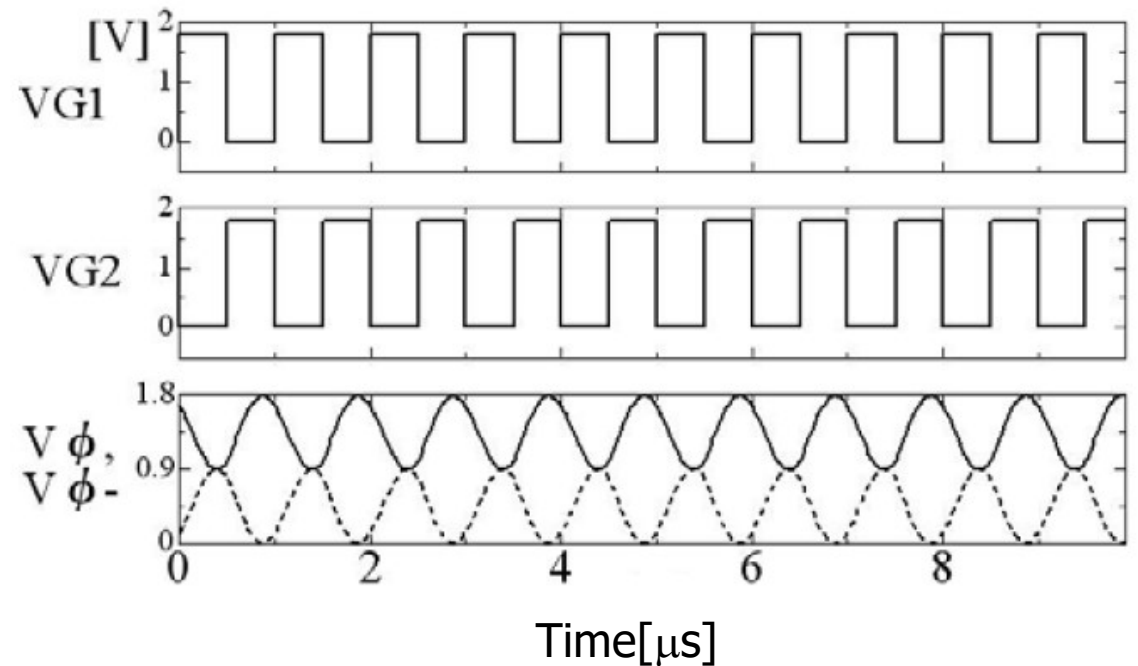 - Simple LC resonant oscillator
- M1, M2 compensate resistive loss
- Voltage regulator with $0.75V_{dd}$ and $0.25V_{dd}$ are used



Some Remarks

- Pros
 - Ultra low power dissipation
 - High Fan-out
- Cons
 - Need supply clocks generation
 - C balancing
 - Low operating speed
- Applications
 - RFID, smart cards, sensors
 - Security blocks


PLL(Phase Locked Loop)

- Definition

- An oscillator whose phase, and thus frequency is locked to an input signal

- Basic operation

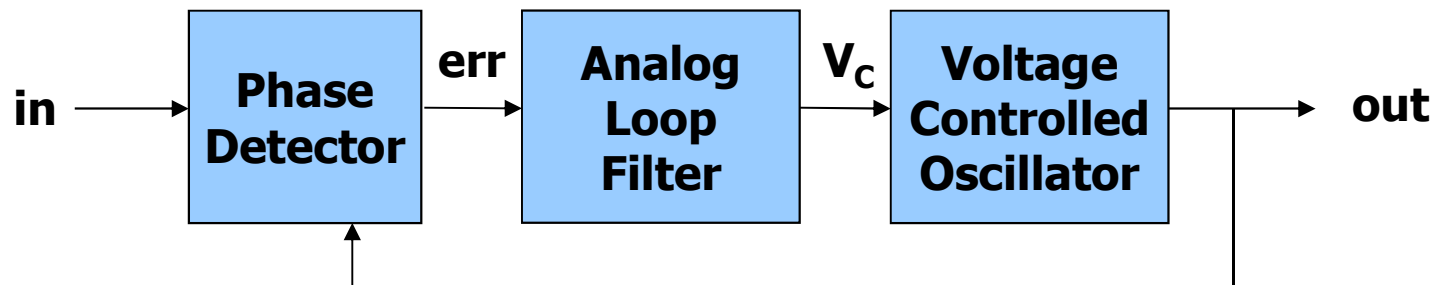- The phase detector
 - compares the phases (input signal, internally generated signal)
 - developing a voltage proportional to the phase difference
- Analog loop filter → smooths PFD signal
- The voltage is applied to the VCO to reduce the phase difference




- Analogy

- Voltage level filtering (low pass filter) vs. Time level filtering

Applications (1)

- Jitter reduction

 - Signals often experience timing jitter as they travel through a communication channel
- Retrieved from a storage medium




- Frequency multiplication

- Multiplies input by a factor of M
- Frequency multiplications at microprocessors

- Frequency Synthesis

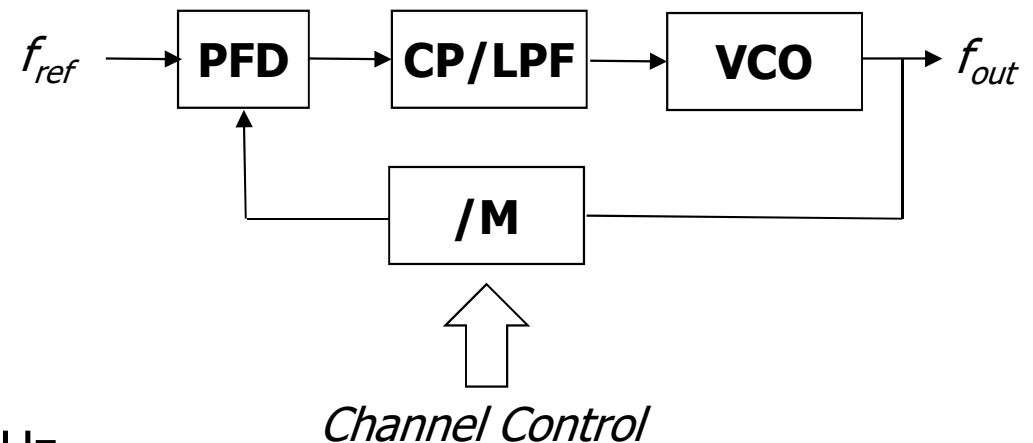
- Accurate periodic waveform
- Frequency vary in very fine steps
- Wireless transceivers
 - 900MHz~925MHz in steps of 200KHz



Applications (2)


- Skew suppression

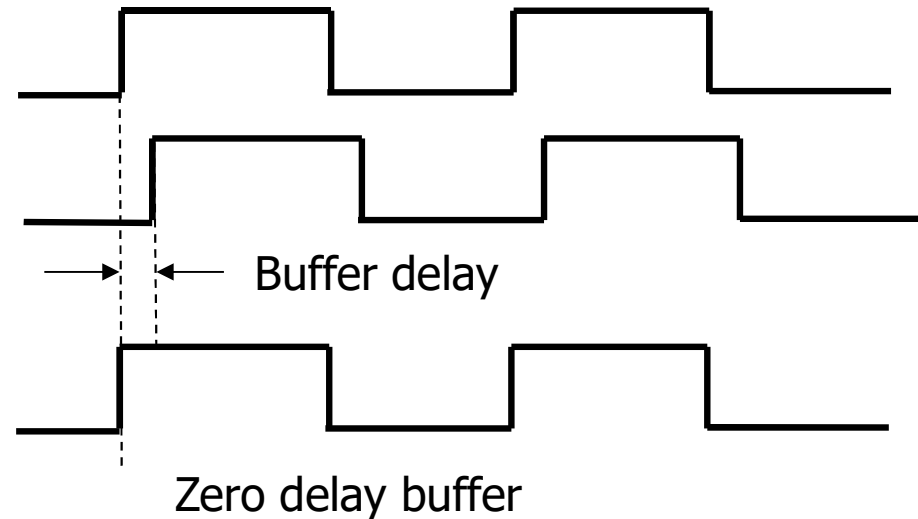- Remove the clock buffer delay at digital systems





- Clock Recovery

 - Data is transmitted without any additional timing reference
- The timing information must be recovered from the data at the receive end



2nd order System

- Linear model of type I PLL

 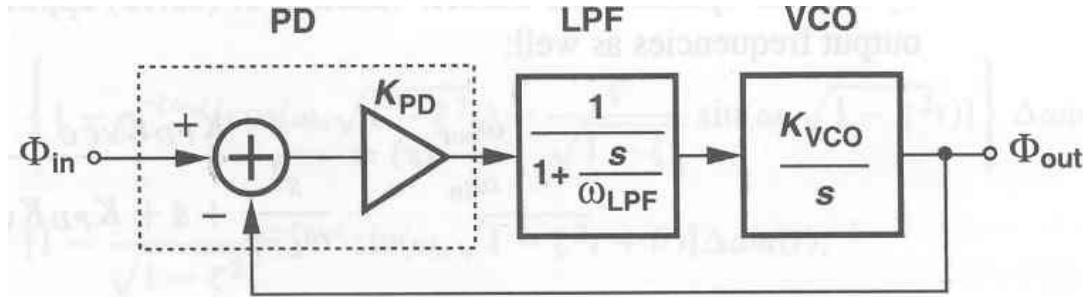

- 1st order LPF, PD(subtractor with amplification), ...
- Open-loop transfer function

$$H(s)|_{\text{open}} = \frac{\Phi_{\text{out}}(s)}{\Phi_{\text{in}}(s)}|_{\text{open}} = K_{PD} \frac{1}{1 + \frac{s}{\omega_{LPF}}} \frac{K_{VCO}}{s}$$

- Close-loop transfer function

$$H(s)|_{\text{closed}} = \frac{K_{PD}K_{VCO}}{\frac{s^2}{\omega_{LPF}} + s + K_{PD}K_{VCO}}$$

Loop Dynamics

- 2nd order transfer function and damping factor

$$H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$$\omega_n = \sqrt{\omega_{LPF} K_{PD} K_{VCO}}$$

$$\zeta = \frac{1}{2} \sqrt{\frac{\omega_{LPF}}{K_{PD} K_{VCO}}}$$

- Two poles


$$s_{1,2} = -\zeta\omega_n \pm \sqrt{(\zeta^2 - 1)\omega_n^2} = (-\zeta \pm \sqrt{\zeta^2 - 1})\omega_n$$

- Real pole : overdamped ($\zeta > 1$)
- Complex pole and response to an input frequency step

$$\omega_{out}(t) = [1 - \frac{1}{\sqrt{1-\zeta^2}} e^{-\zeta\omega_n t} \sin(\omega_n \sqrt{1-\zeta^2} t + \theta)] \Delta\omega u(t)$$

$$\theta = \sin^{-1} \sqrt{1-\zeta^2}$$

 
$$\zeta\omega_n = \frac{1}{2} \omega_{LPF} = \frac{1}{\tau_{decay}}$$



Damping Factor & Stability


- Underdamped response

 - $\zeta=0.707$:
maximally flat response
- $\zeta=0.707\sim 1$
generally used



- Bode plot

 - Mostly unstable
- Direct relationship among variables
- Loop gain increase \rightarrow settling behavior degrades



Voltage Controlled Oscillator

- Parameters to consider
 - Tuning range
 - MIN ~ MAX frequency *vs.* input frequency range
 - Covers the process, temperature and supply variations
 - Jitter
 - Timing accuracy
 - Phase noise
 - Spectral purity
 - Supply and substrate noise rejection
 - Input/output linearity
- Other considerations
 - Single-ended *vs.* differential
 - Duty cycle




PFD and Charge Pump

- **PFD & Charge Pump**

- Produce a signal current proportional to the difference in phase or frequency between two input signals
- Design Issues
 - Gain & Linearity
 - Dead zone
 - Mismatch between sourcing and sinking current
 - Mismatch between UP and DOWN switching time
 - UP/DOWN current programmable
 - Leakage current
 - Maximize voltage compliance

Common Circuits

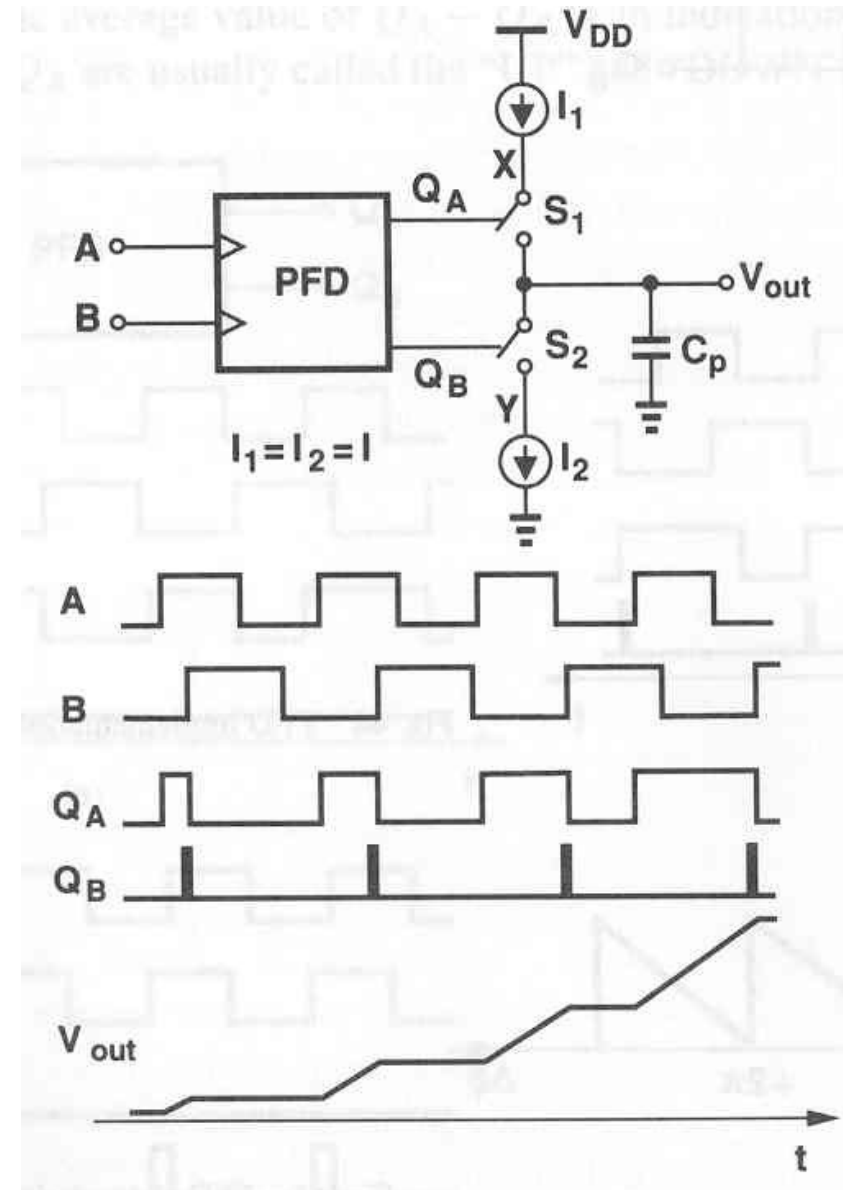  
- PFD output
 - Difference amplification → LPF
 - Drive 3-state "charge pump"






CP & Dead Zone

- Charge pump

 - Infinite DC gain
- Offset, mismatch
- Time difference $\rightarrow 0$: gain reduced
- Input/output difference < dead zone
 - Error occurs
- Sideband of VCO



Mismatch in current

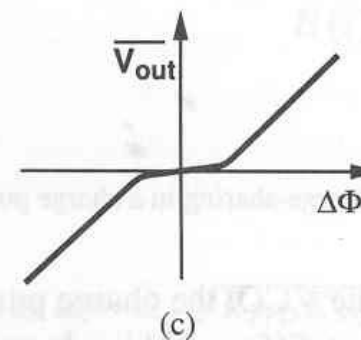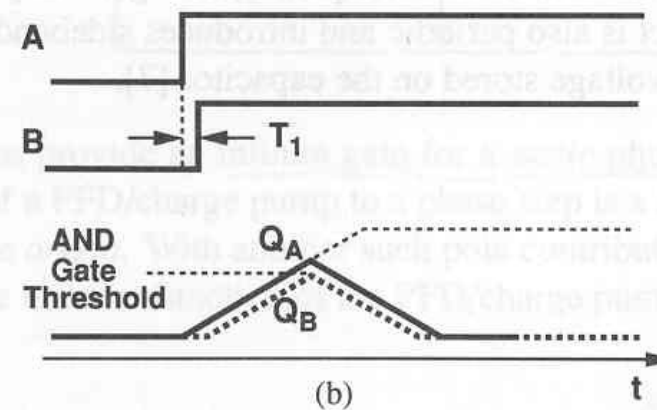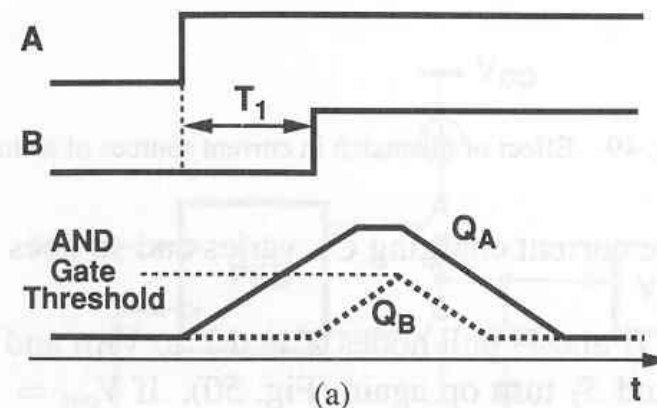


Loop Filter & Loop Bandwidth

- Loop Filter

- Design Tradeoffs

- The narrower the loop BW
→ the lower reference spurs, but the longer the lock time
 - The wider the loop BW → the phase noise of VCO is limited

- Loop Bandwidth and phase margin

 

- Loop BW $< \frac{F_{PFD}}{10}$

- Phase Margin $> 50^\circ$

for $\phi_{PM} = 60^\circ$

$$R_2 = \frac{N\omega_p}{K_{pd}K_{VCO}}, \quad C_2 = \frac{4}{R_2\omega_p}$$

$$C_1 = \frac{1}{4R_2\omega_p}$$

$$\rightarrow \omega_p \approx \frac{K_{pd}K_{VCO}}{N} \frac{R_2C_2}{C_1 + C_2}$$

Noise in PLLs

- Jitters
 - Period experiences small changes, Deviating from their ideal points
 - slow jitter and fast jitter
- All the loop components may contribute output phase noise, θ_o .
 - The noise in θ_o should be suppressed.
- Two important cases
 - Input signal contains noise: Bandwidth should be low
 - VCO introduces noise : dominant, Bandwidth should be large


$$\frac{\theta_o(s)}{\theta_i(s)} = \frac{\frac{I_P}{2\pi C}(RCs + 1)K_{VCO}}{s^2 + \frac{I_P}{2\pi}K_{VCO}Rs + \frac{I_P}{2\pi C}K_{VCO}} = H(s) \quad \frac{\theta_o(s)}{\theta_{VCO}(s)} = \frac{s^2}{s^2 + \frac{I_P}{2\pi}K_{VCO}Rs + \frac{I_P}{2\pi C}K_{VCO}} = H(s)$$

- Increasing the bandwidth of the PLL can lower the contribution of the VCO phase noise

All-Digital PLL

- Demand for digitization of PLL
 - Integrated on IC as a key circuit
 - Elimination of externally attached components
 - No need for adjustment
- Advantages
 - Testability, Programmability, Stability
 - Portability over different processes
 - Reduce the system turn around time
 - Fast lock time
- Disadvantages
 - Need high frequency clock source, low jitter performance
 - Lower frequency range : ADC, counter, ...


Analog PLL vs. Digital PLL

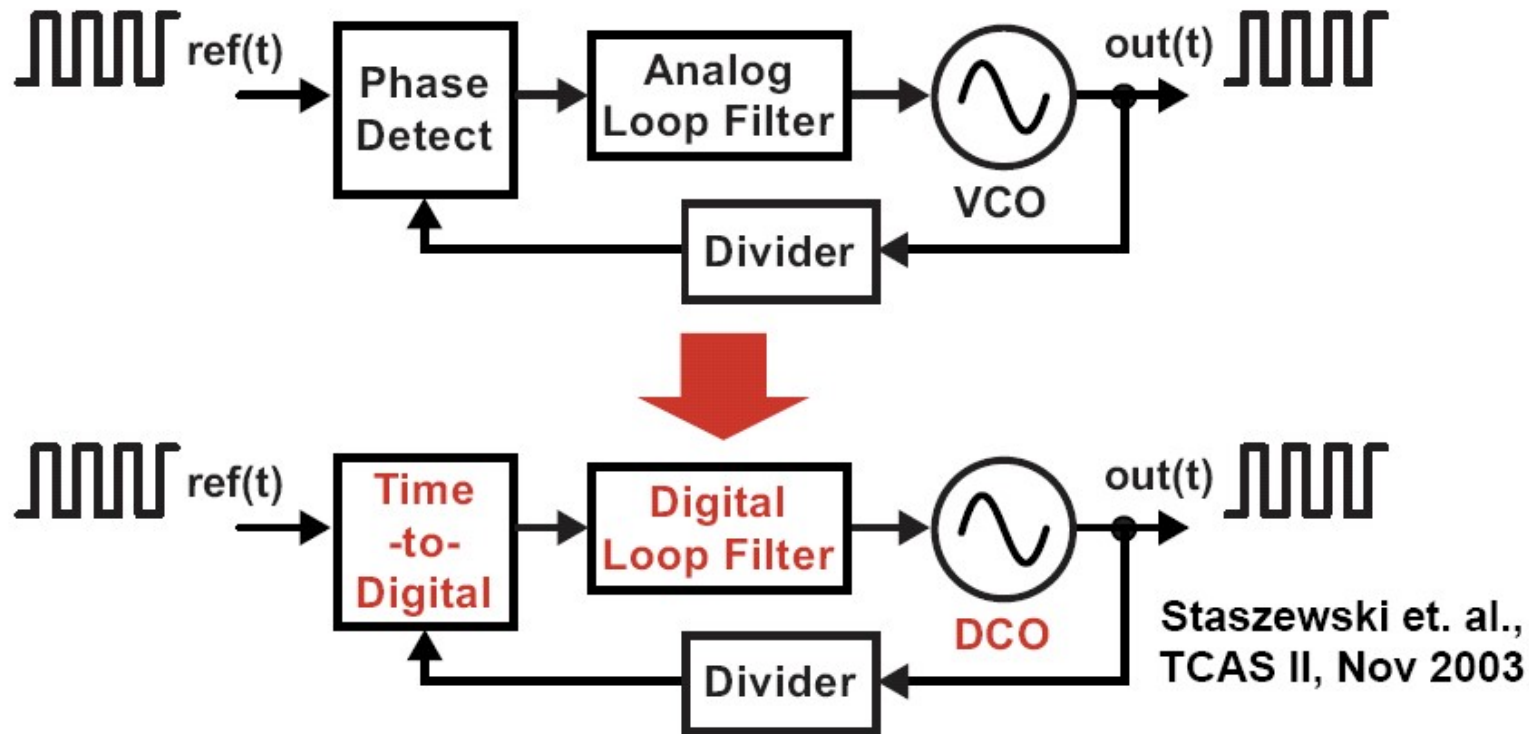

- Digital loop filter
 - Compact area, Leakage insensitive
- Challenges
 - DCO: Digitally Controlled Oscillator
 - TDC: Time-to-Digital Converter


DCO(Digitally-Controlled Oscillator)

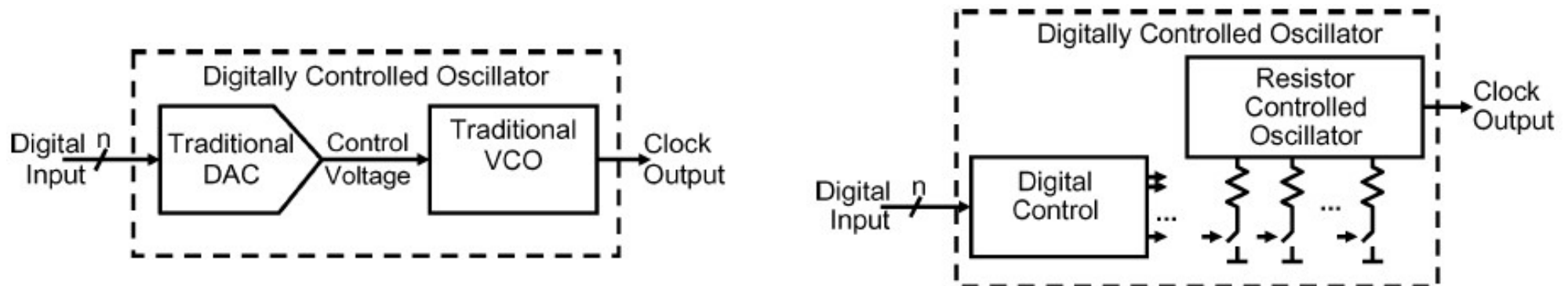- **The most critical component**
- **Challenges**
 - Noise performance, PVT variation
 - Tuning range and the mechanism for tuning
- **2 main approaches**
 - Paring a DAC and a VCO
 - Digitally controlling a physical parameters




Injection-Locked 16b DCO

- ISSCC 2016, U. of Illinois & Xilinx

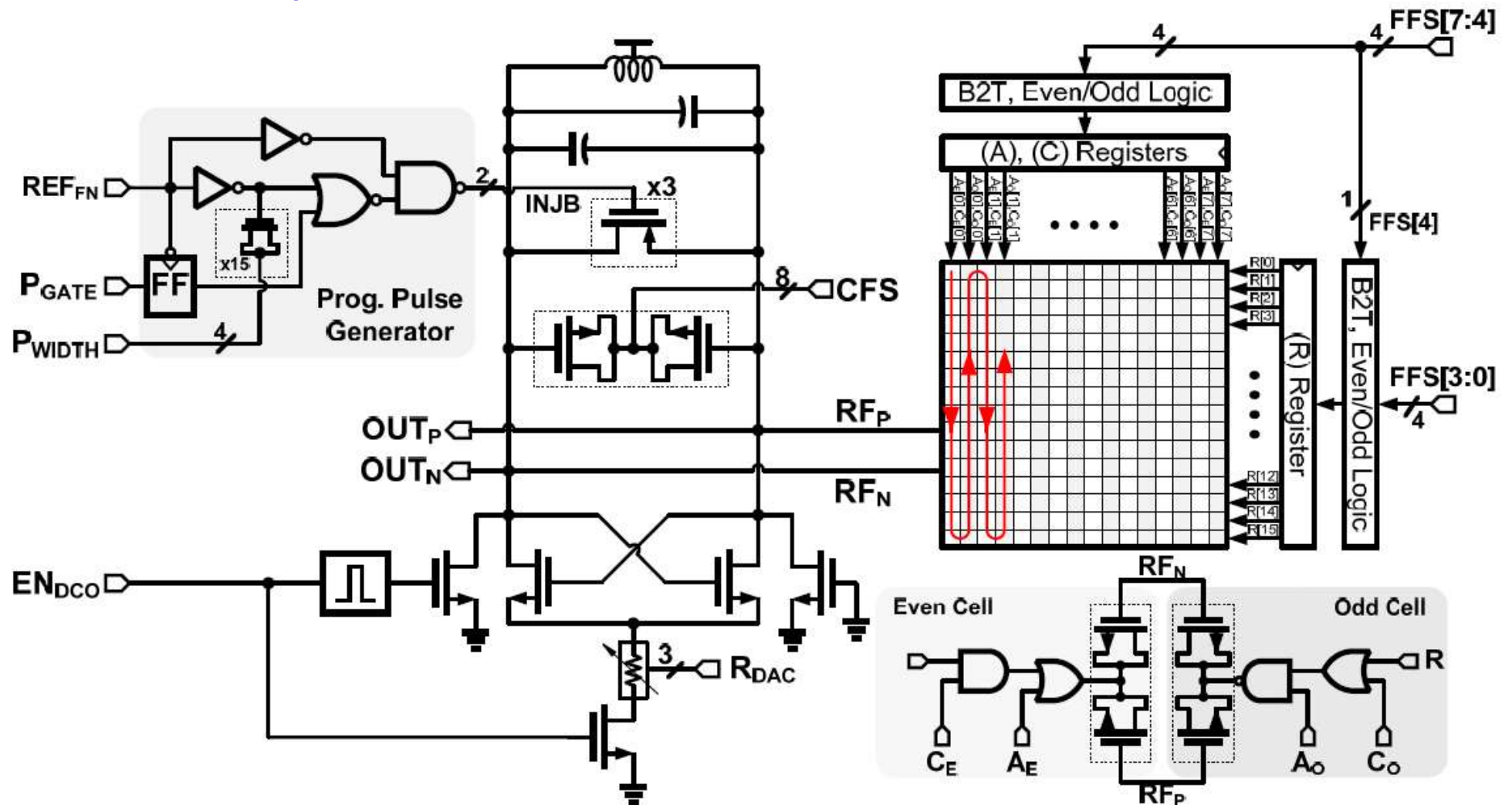

Conventional TDC





- Use linear delay element

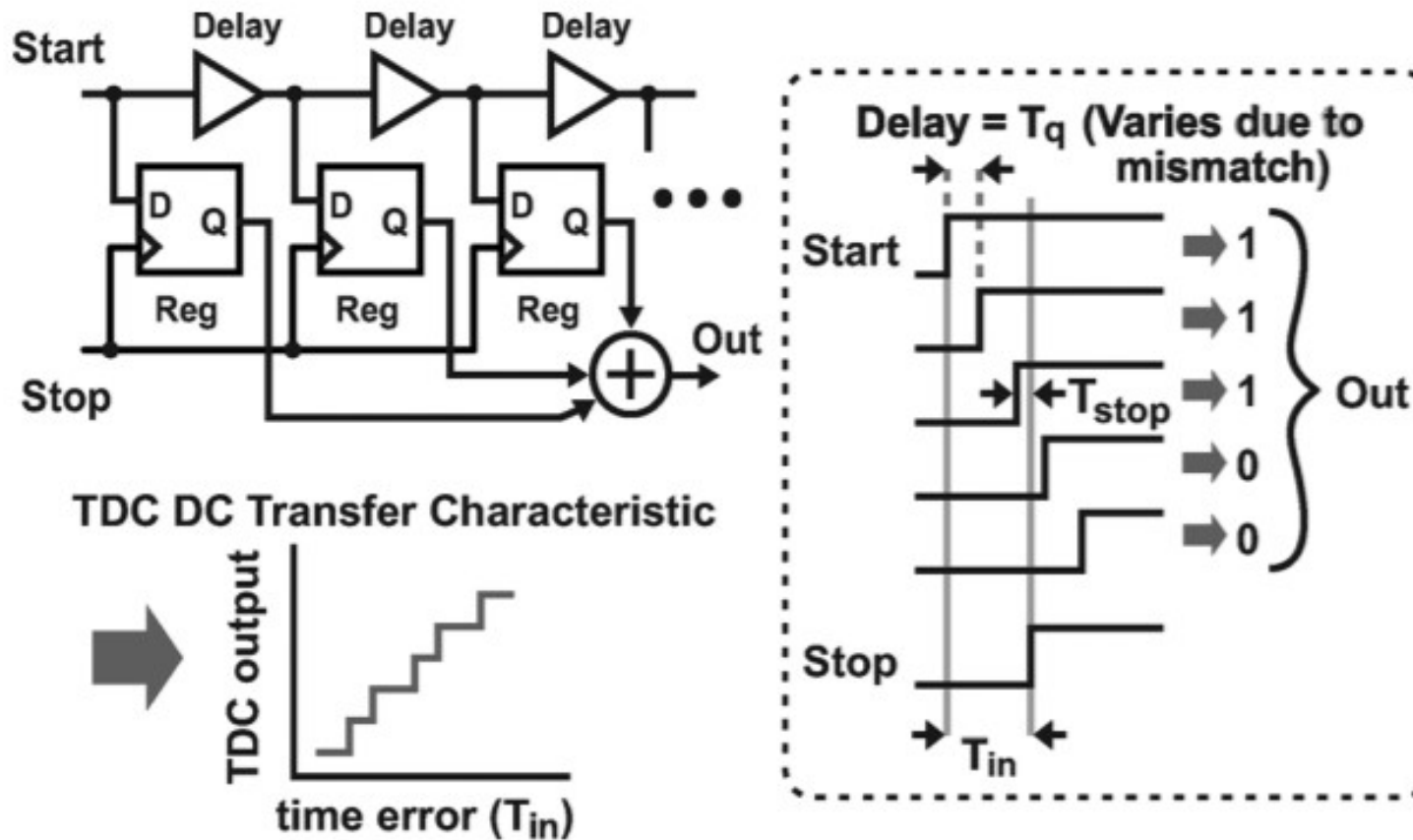

JSSC
2009

Improved TDC

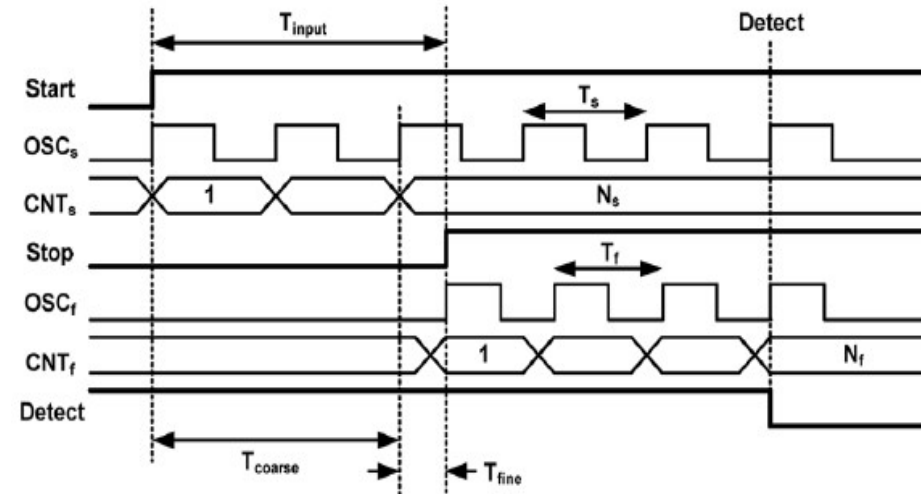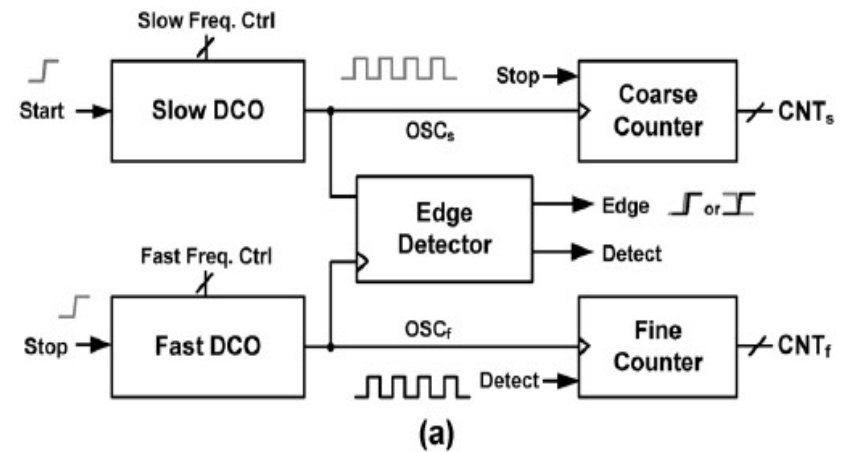  - Vernier delay line, 2-stage with time-amplifier (2008 JSSC)
- Cyclic TDC (2011 JSSC)




CDR(Clock and Data Recovery)

- Needs
 - Optical communication
 - Backplane routing
 - Chip-to-chip interconnection
- Random data processing
 - Synchronous operation : data sensing
 - Receivers must generate clock : retimed
 - D-flipflop: data retiming, decision circuit
- Clock conditions
 - Frequency equal to the data
 - Phase relationship with respect to data
 - Small jitter

Simple CDR Circuit

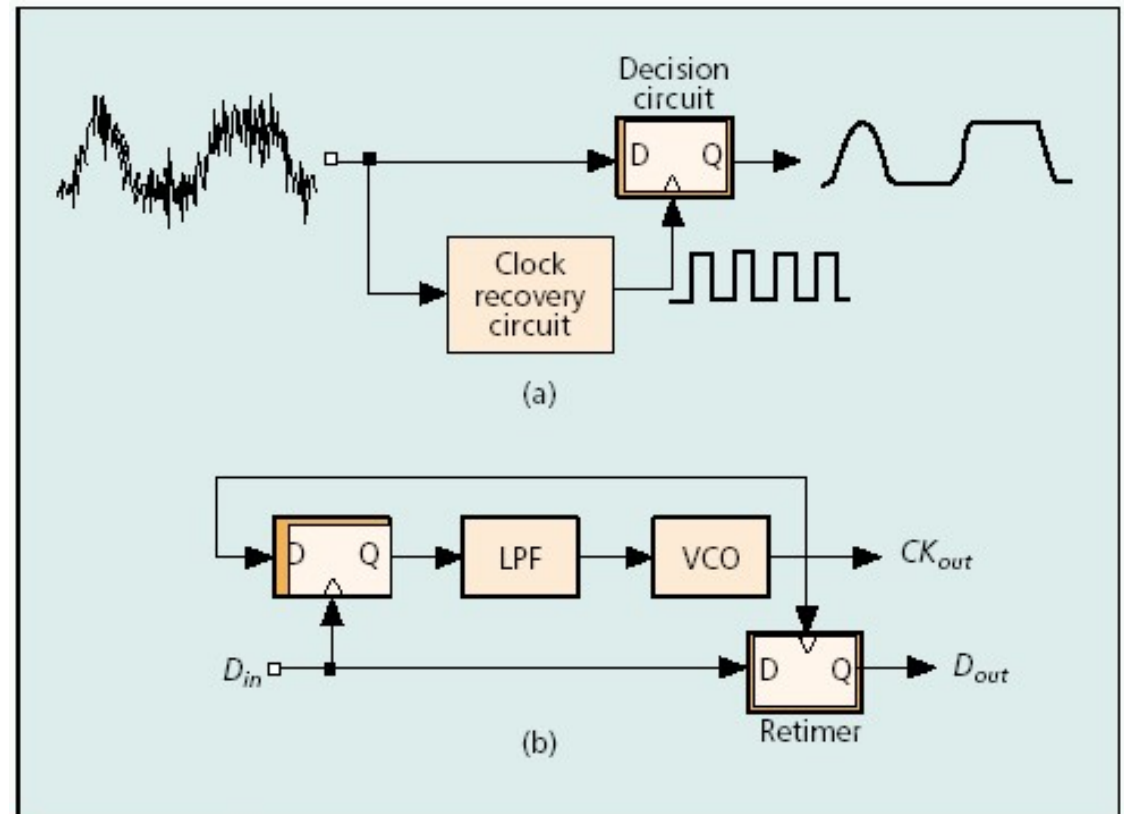- Structure
 - DFF as Phase Detector
 - Recovered clock
($CK_{out} \leftrightarrow D_{in}$)
- Drawbacks
 - Full digital output PD
 - Large phase offset for data retiming
(D-to-Q, CK-to-Q)
 - Feedthrough of data
(to VCO output)
- PD needs skew avoiding
 - Sample the data by the clock



■ Figure 1. a) The role of a CDR circuit in retiming data; b) an example of CDR implementation.

IEEE spectrum

PLL Characteristics

- Specification & Performance
 - Frequency range
 - Loop Bandwidth
 - Jitter
 - cycle-to-cycle jitter, peak-to-peak jitter
 - histogram, eye-diagram, PPM
 - By thermal noise, supply noise and substrate noise
 - Lock time
 - Damping factor
 - Power consumption
 - Area
 - Synthesizable (for digital PLL)
 - Silicon proven (for Analog PLL)

Layout Issues

- **Dummy layout**
 - Density affects the characteristics of transistors
 - Dummy cell/pattern for low density portions
- **Symmetry**
 - Minimize process variation: VCO, ...
 - Differential signal
- **Separation**
 - Geographical separation is best, guard
 - Substrate noise should be minimized: Substrate contacts, bypass C
- **Supply**
 - Different supply, independent supply for clock buffer
 - Capacitors between supply and ground
 - On-chip capacitor array, large capacitor is better
 - Use metal plane for supply

Other Considerations

- VCO

- Guard

- Every transistor : supply and ground
 - Every delay cell : ground guard
 - All VCO

- Interconnection

- The same line length and width
 - Elimination of 90 degree interconnection

- Geography

- The same cell direction(orientation) for every delay cell
 - Symmetrical cell layout

- ETC

- ESD, Bias line routing, cross-talk
 - Stuffing option, corner simulation, di/dt, wire-to-wire C